

## PHASE II Cadence

### Table of contents

|  |    |
|--|----|
| Cadence Parameters .....                                       | 3  |
| Final Parameters after Resizing for 3 (or 2) Multipliers. .... | 3  |
| Cadence Layout.....  | 3  |
| Minimize the size of Inverter 1 .....                          | 6  |
| Inverter 4 and 3-input-NAND .....                              | 7  |
| Inverter 2 .....   | 9  |
| LVS Results.....   | 9  |
| Inverter1 + Inverter 2.....                                    | 11 |
| LVS Results .....  | 12 |
| Inverter 3 .....   | 12 |
| LVS Results .....  | 13 |
| Predecoder NAND .....  | 13 |
| LVS Results .....  | 14 |
| Inverter 4 .....   | 15 |
| LVS Results .....  | 15 |
| Inverter1 + Inverter 2 + Predecoder NAND .....                 | 16 |
| LVS Results .....  | 17 |
| Thinner 3-input NAND .....                                     | 18 |
| Final Thinner 3-input NAND Gate .....                          | 19 |
| Inverter1 + Inverter 2 + Thin Predecoder NAND .....            | 20 |
| LVS Results .....  | 21 |
| Schematic.....   | 21 |
| LVS Results .....  | 23 |
| Schematic.....   | 23 |
| Predecoder+Postdecoder +SRAM.....                              | 24 |
| Schematic.....   | 24 |
| LVS Results .....  | 25 |
| Rewiring SRAM Cell .....                                       | 25 |
| LVS Results .....  | 26 |
| LVS Results (For Decoder with Re-wired SRAM Cell).....         | 27 |
| Predecoder+Postdecoder+Array of Re-wired SRAM Cells .....      | 27 |
| LVS Results .....  | 28 |
| Minimizing Inverter 4 .....                                    | 29 |
| LVS Results .....  | 30 |
| Minimizing Postdecoder NAND Gate .....                         | 31 |
| Minimizing the Whole Postdecoder .....                         | 32 |
| LVS Results .....  | 32 |
| LVS Results Match .....  | 33 |
| Minimizing the Inverter 3.....                                 | 33 |
| LVS Results .....  | 33 |
| LVS Results Match .....  | 34 |
| Minimizing the Inverter 2.....                                 | 35 |

|  |    |
|--|----|
| LVS Results .....  | 36 |
| Minimizing the Whole Predecoder .....                        | 36 |
| LVS Results .....  | 37 |
| Minimizing Predecoder+Postdecoder+SRAM Array .....           | 37 |
| LVS Results .....  | 38 |
| Array of SRAM Cells (4x32 SRAM Cells) .....                  | 39 |
| Schematics .....   | 39 |
| Layout .....   | 39 |
| LVS Results .....  | 40 |
| SRAM Array (32x32).....                                      | 41 |
| LVS Results .....  | 42 |
| Post Decoder Array (32 Instants) .....                       | 45 |
| LVS Results .....  | 46 |
| LVS Window Screen from Labs .....                            | 47 |
| 32x32 SRAM Cells + 32-Postdecoder Array .....                | 47 |
| LVS Results .....  | 48 |
| Predecoder Symbol.....                                       | 52 |
| LVS Results .....  | 53 |
| Predecoder Final.....  | 53 |
| LVS Results .....  | 54 |
| 2 Predecoder.....  | 54 |
| LVS Results .....  | 55 |
| Predecoder Array (16 Instants).....                          | 56 |
| LVS Results .....  | 57 |
| 16-Predecoder + 32-Postdecoder + 32x32-SRAM.....             | 57 |
| LVS Results .....  | 60 |
| LVS (mysteriously) Failed .....                              | 60 |
| Predecoder (8 Instants).....                                 | 62 |
| LVS Results .....  | 63 |
| Minimizing Distance between Predecoder and Postdecoder ..... | 63 |
| LVS Failed Error Again.....                                  | 64 |
| 16-Postdecoder + 64-Predecoder.....                          | 65 |
| LVS Results .....  | 66 |
| Wire Branching Examples .....                                | 67 |

## Cadence Parameters

The widths for PMOS and NMOS are listed below.


pwidth = 0.7200 2.64 1.5 5.4 1.44 5.34  
 nwidth = 0.3600 1.32 2.22 2.7 2.16 2.64

## Final Parameters after Resizing for 3 (or 2) Multipliers.

pmos  
 0.72 2.64 1.5 5.4 1.44 5.40  
 nmos  
 0.36 1.32 2.22 2.76 2.16 2.70

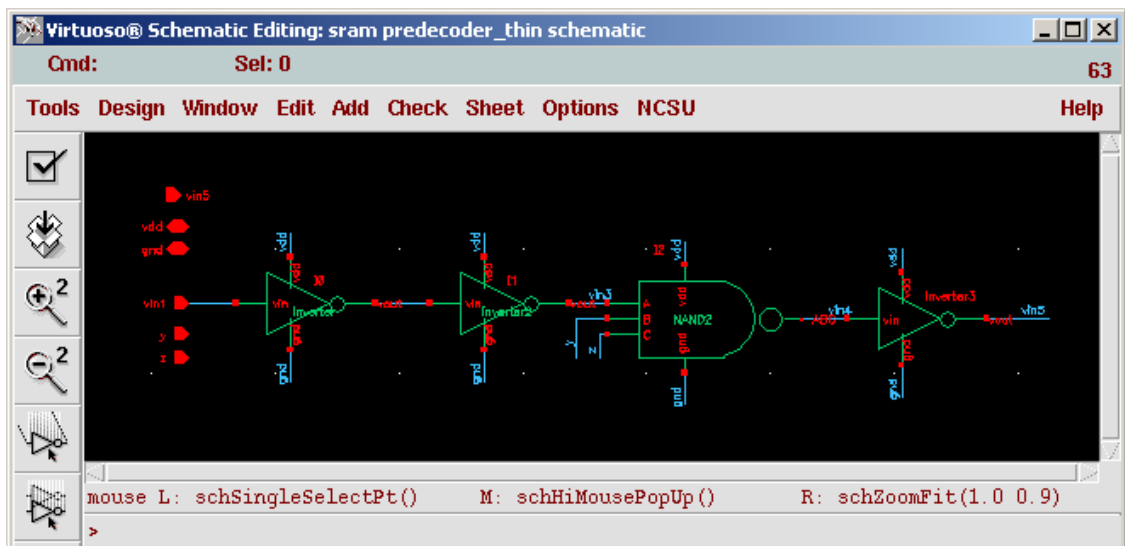
## Cadence Layout

The goal of this part is to built a decoder with the logic of not-not-nand-not-nand-not. The first 3-input-nand gate has a branch factor of 4, and the second 3-input-nand gate has a branch factor of 8.




## Inverter 1 – First Inverter

(Minimum Sized, pmos/nmos=0.72/0.36)

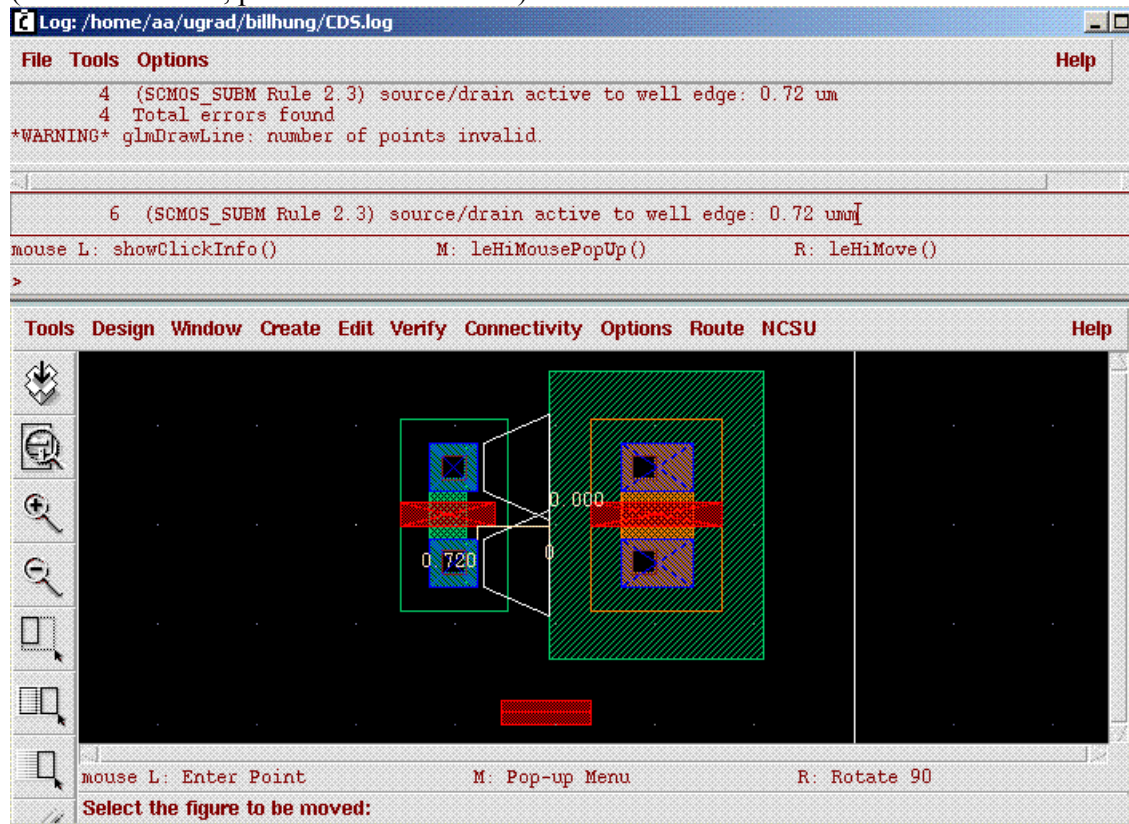

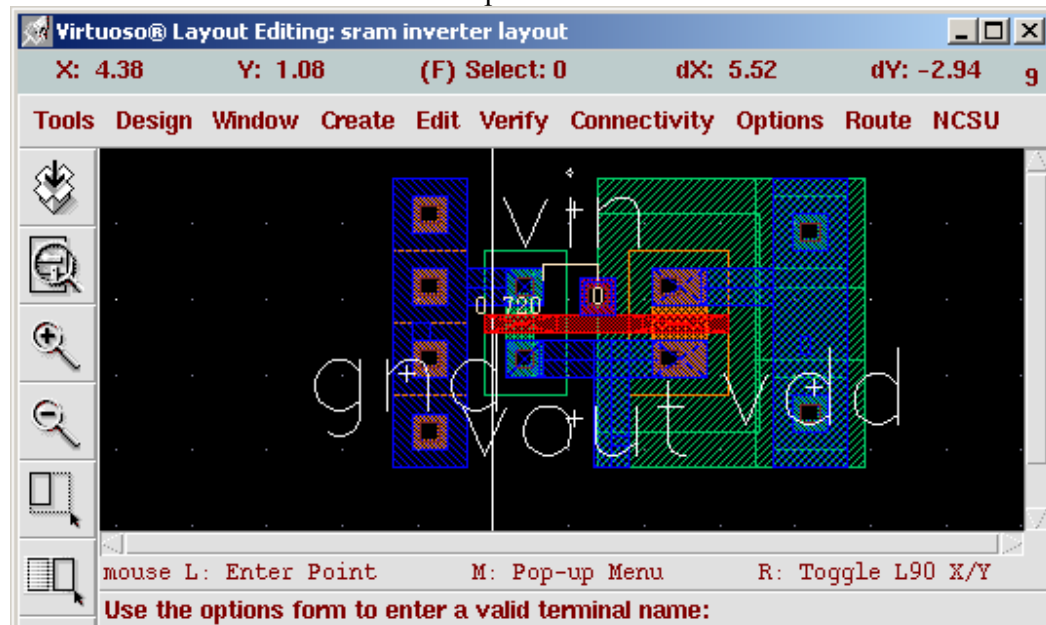6 lambda between nmos-contacts and pmos-nwell.



Testing LVS with minimum sized inverter.

DRC -&gt; Total errors found: 0

Extract -&gt; Total errors found: 0



Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |


The net-lists match.

LVS->Pass **GREAT**

## Minimize the size of Inverter 1

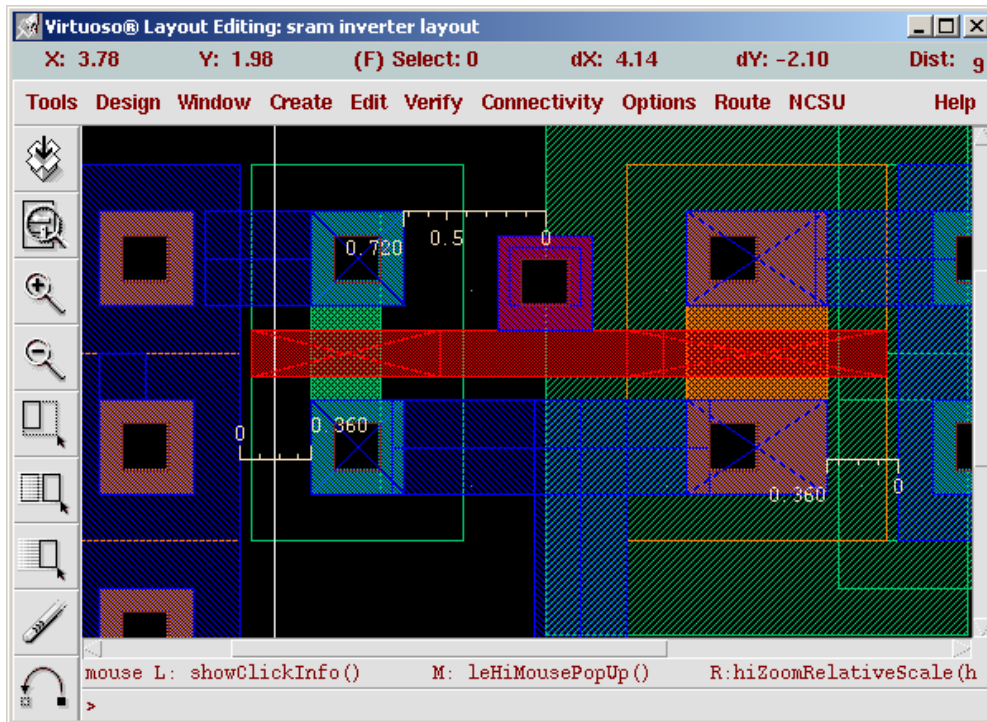

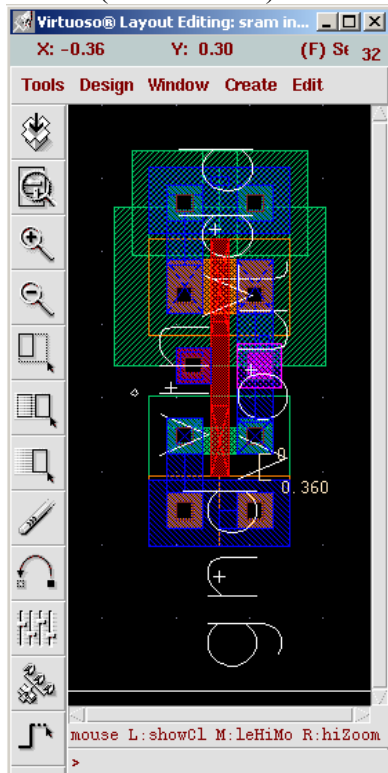
metal1=3 lambda, nmos-contact to pmos-nwell=6 lambda. The ntaps and ptaps are currently placed on the left and right sides. The inverter 4 (the biggest one) and 3-input nand 2 (the last nand) will determine the locations of the ntap and ptap.




Inverter 1 final layout
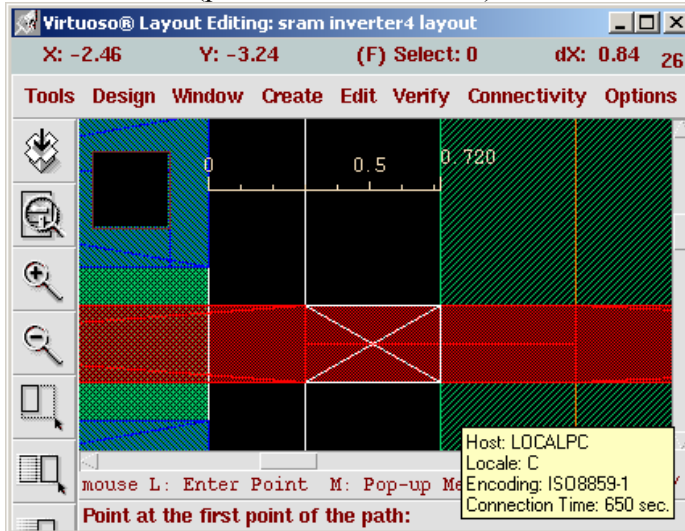
## Inverter 4 and 3-input-NAND


– Last Inverter (pmos/nmos=5.34/2.64) and Last NAND (pmos/nmos=1.44/2.16)



Nmos and pmos 6 lambda apart.

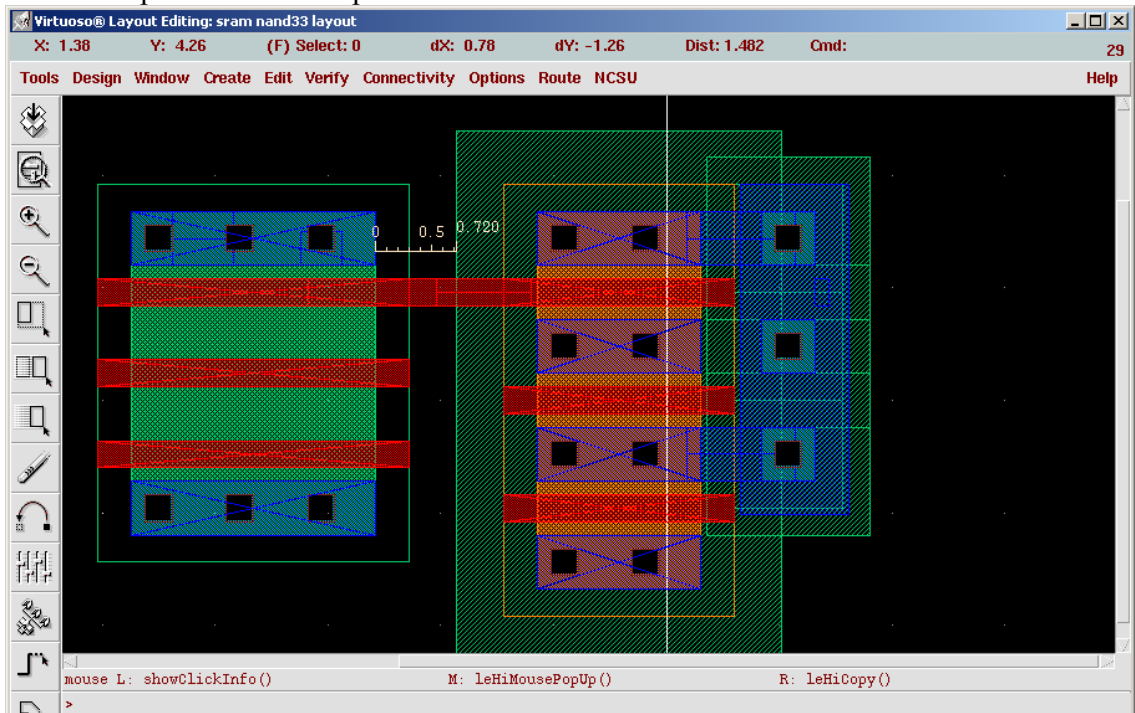

Last 3-input-NAND Gate

 


2-input NAND Gate




## Inverter 2

(pmos/nmos=2.64/1.32)

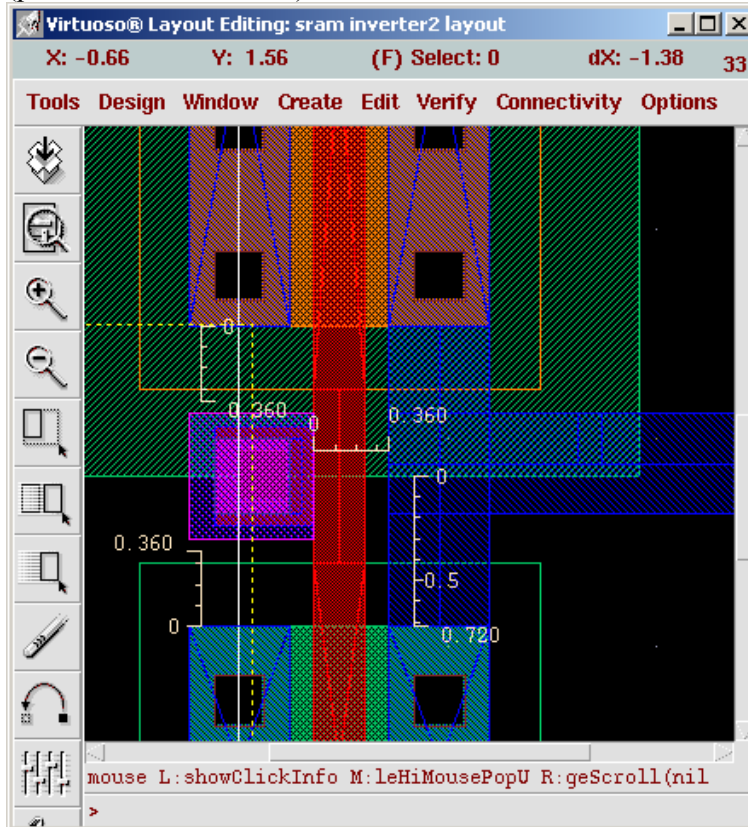

 Adding M1-M2 contact, 3 lambda metal1 spacing, 6 lambda pmos-nmos spacing.



Metal2 spacing 4 lambda.

## LVS Results


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


| count |           |
|-------|-----------|
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

The net-lists match.

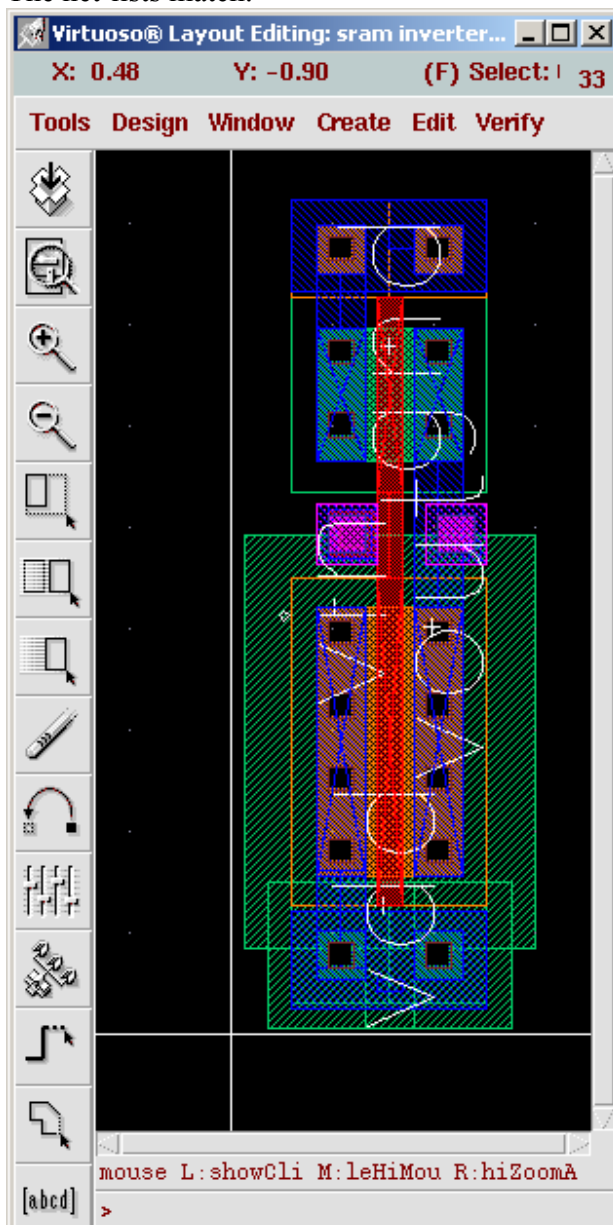


Inverter 2 final layout. The cell was flipped to share the vdd and gnd.

## Inverter1 + Inverter 2

 

DRC, Extract, LVS pass

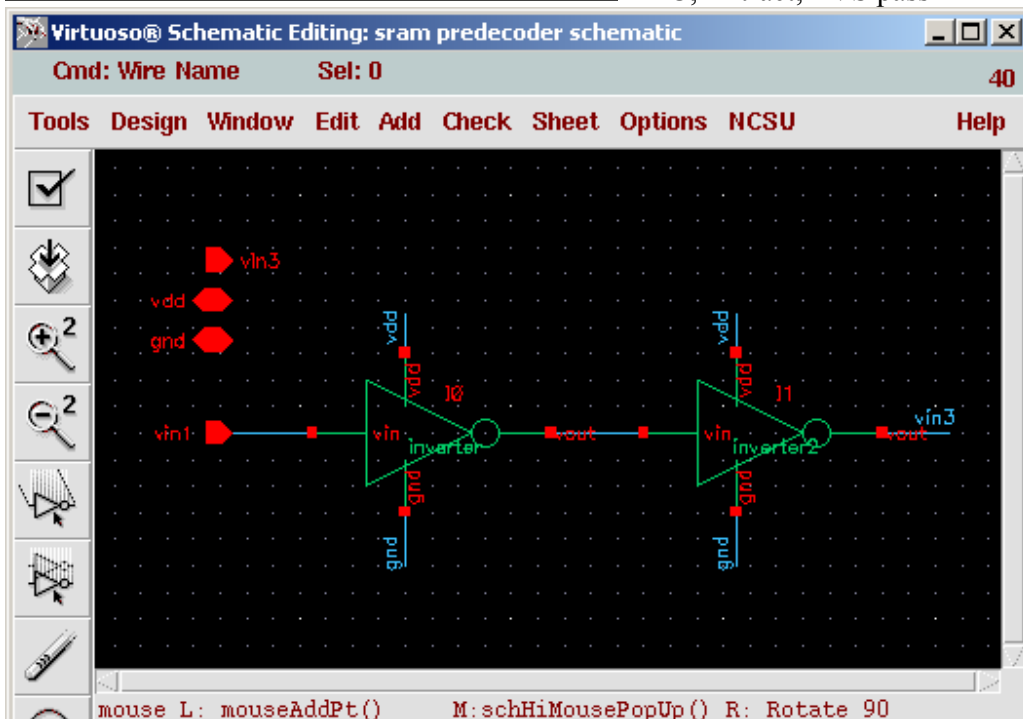

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

The net-lists match.

## Inverter 3

(pmos/nmos=5.4/2.7)

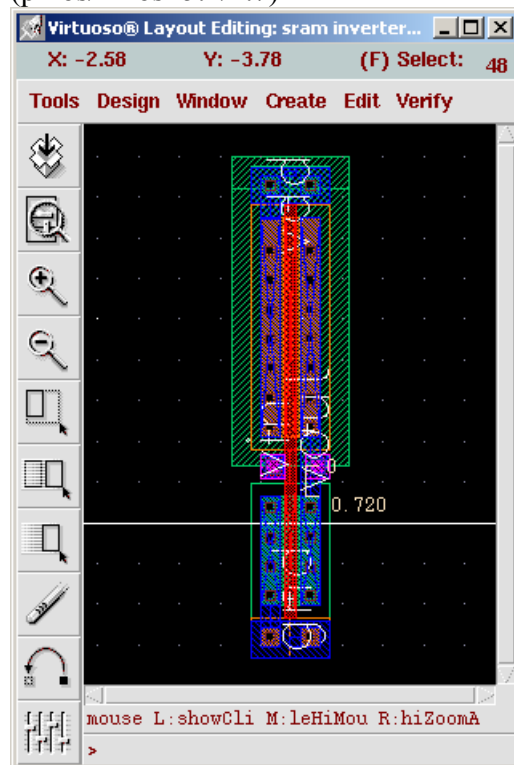

DRC, Extract, LVS Pass

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

The net-lists match.

## Predecoder NAND

(pmos/nmos=1.5/2.22)

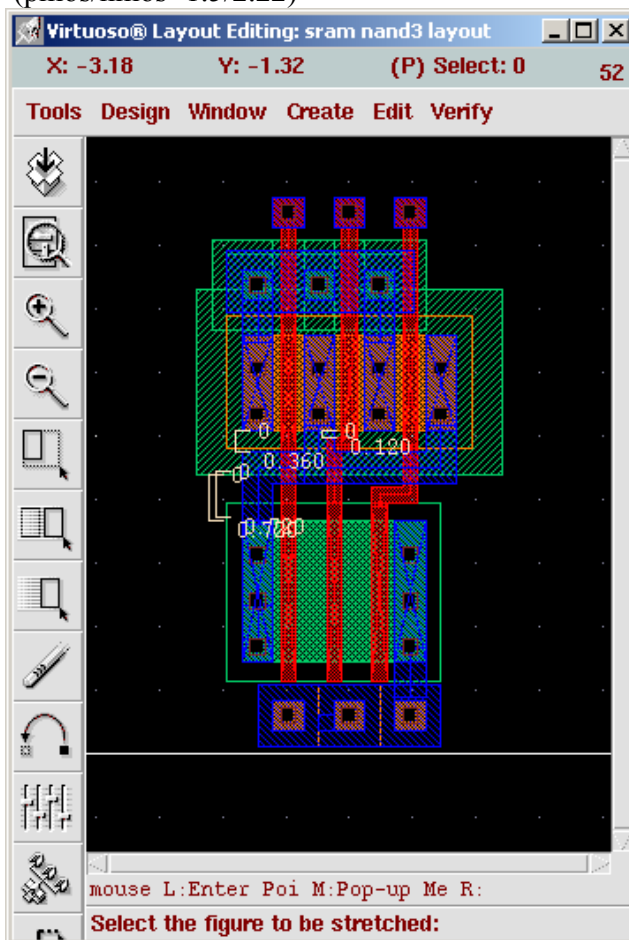

3-input NAND

**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 10    | nets      |
| 6     | terminals |
| 5     | pmos      |
| 5     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 10    | nets      |
| 6     | terminals |
| 5     | pmos      |
| 5     | nmos      |


Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin1 |
| 4 | vin4 |
| 5 | y    |
| 6 | z    |

The net-lists match.

## Inverter 4

(pmos/nmos=5.34/2.64)

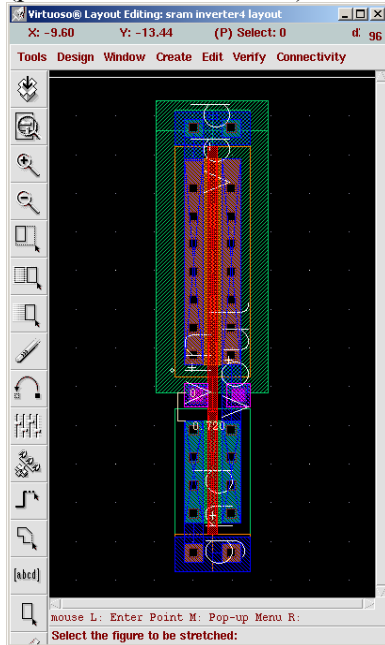

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist


|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

The net-lists match.
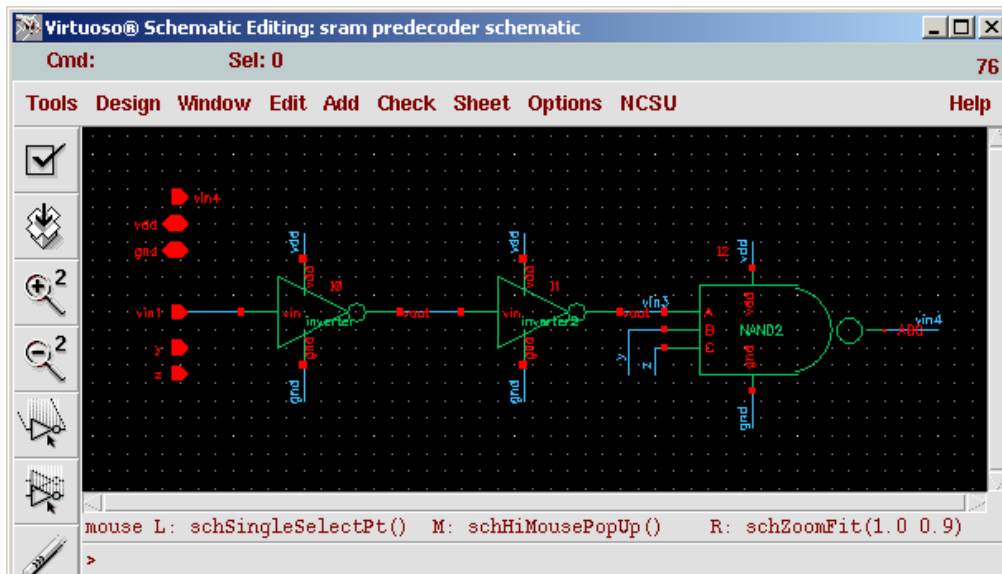
## Inverter1 + Inverter 2 + Predecoder NAND



Schematic

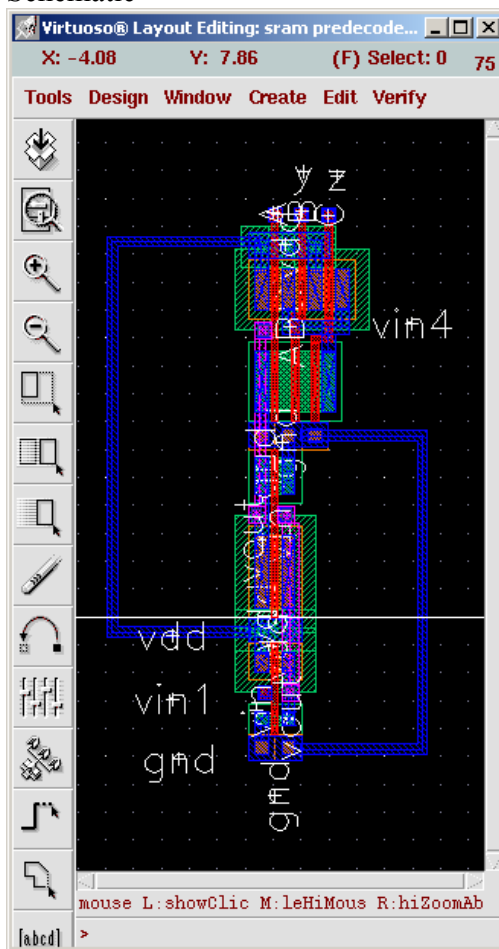

Final Layout



**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 10    | nets      |
| 6     | terminals |
| 5     | pmos      |
| 5     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


| count |           |
|-------|-----------|
| 10    | nets      |
| 6     | terminals |
| 5     | pmos      |
| 5     | nmos      |

Terminal correspondence points


|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin1 |
| 4 | vin4 |
| 5 | y    |
| 6 | z    |

The net-lists match.


## Thinner 3-input NAND

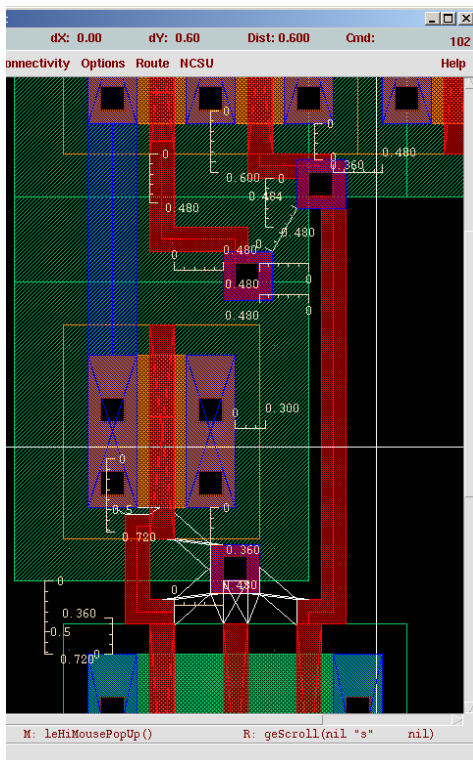

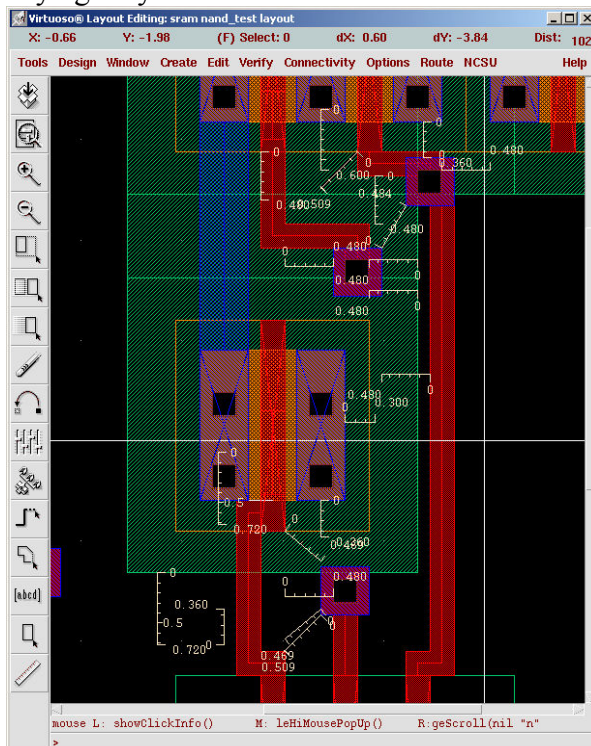
Trying very hard to make a thinner NAND Gate



Getting with some wiring troubles

 

 The M1\_M2 contact placed here has no DRC error, but the M2 from the output contact needs to go down, and the contact from the poly wants to go down. So this won't work.



### Final Thinner 3-input NAND Gate

Before-> Horizontal=3.30um, vertical=6.78um  
Now-> Horizontal=3.12 um , vertical=11.46umz

Fat NAND versus Thin NAND  
176.94um<sup>2</sup> versus 87.984um<sup>2</sup>  
Thin NAND won


#### Calculation

Fat

$$6 \times (3.36 - 2.88) \times 1.92 \times 32 = 176.94$$

Thin

$$2.88 \times 6 \times (11.48 - 6.78) = 87.984$$

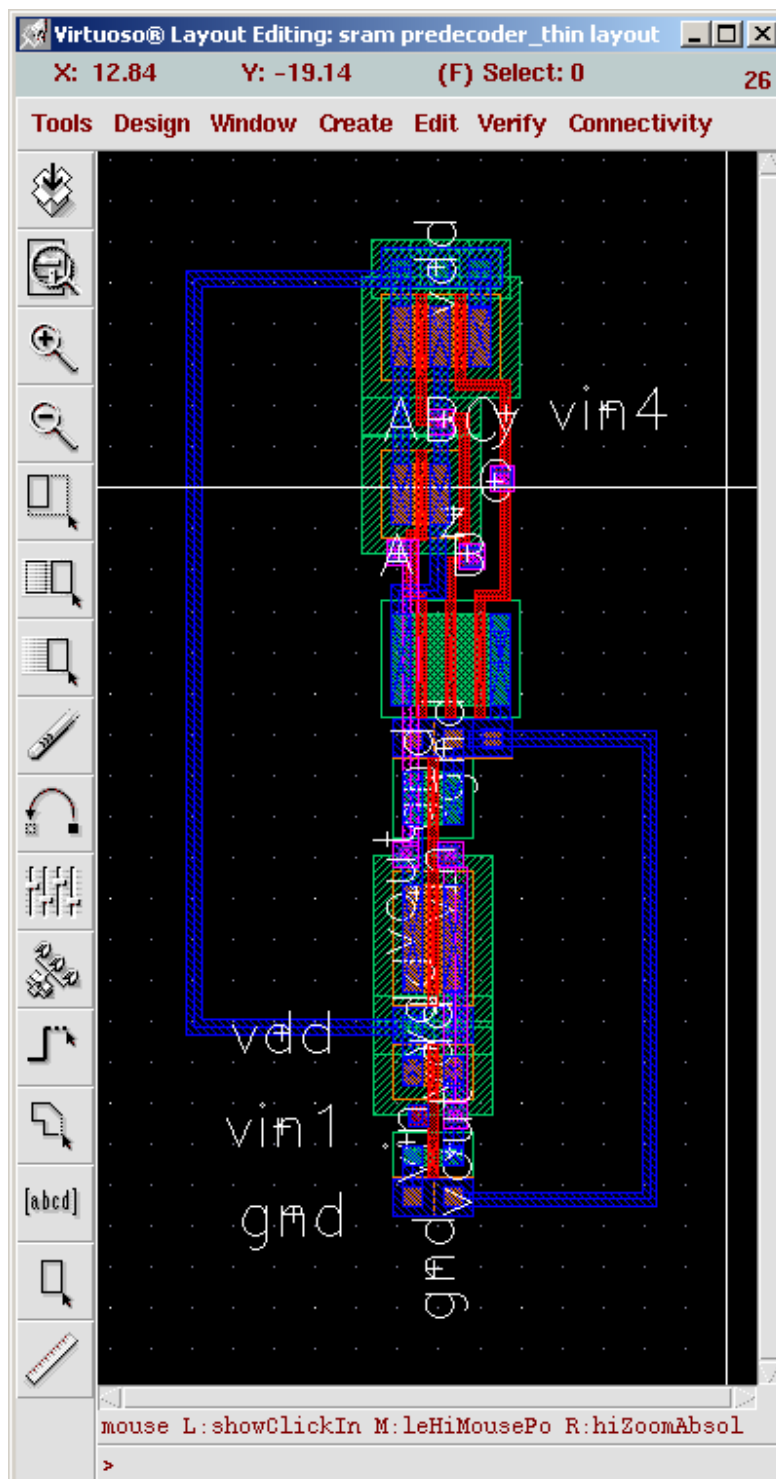**Inverter1 + Inverter 2 + Thin Predecoder NAND**

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 8     | nets      |
| 6     | terminals |
| 3     | pmos      |
| 3     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


| count |           |
|-------|-----------|
| 8     | nets      |
| 6     | terminals |
| 3     | pmos      |
| 3     | nmos      |

Terminal correspondence points


|   |     |
|---|-----|
| 1 | A   |
| 2 | ABC |
| 3 | B   |
| 4 | C   |
| 5 | gnd |
| 6 | vdd |

The net-lists match.

## Schematic

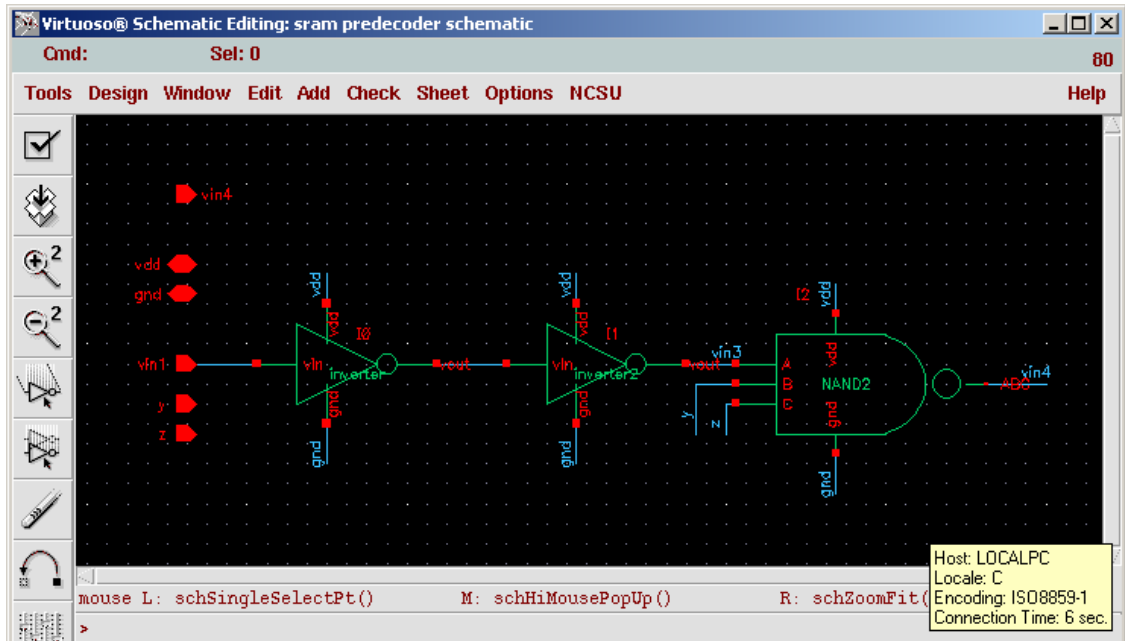

## Final Predecoder

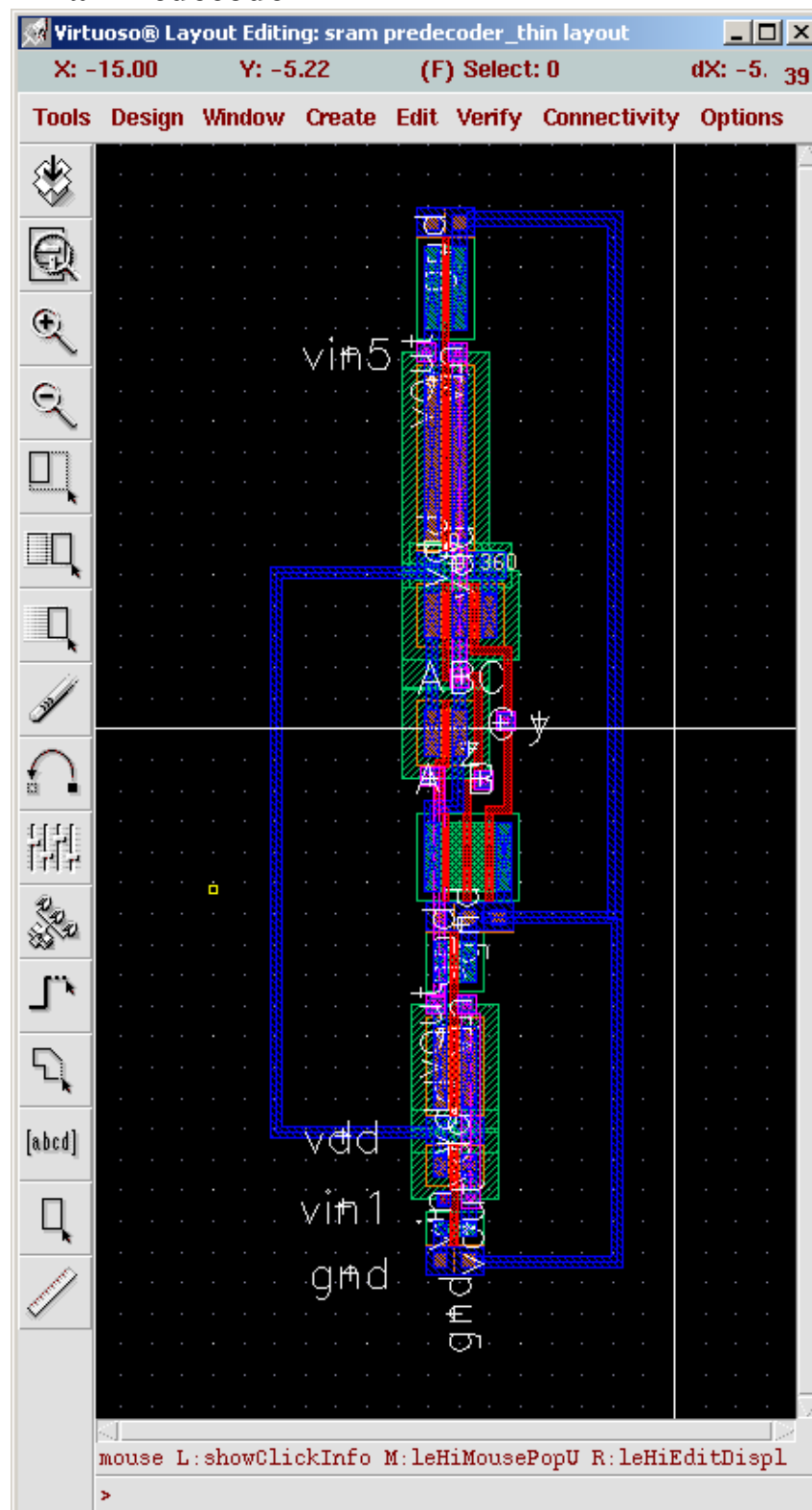

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 11    | nets      |
| 6     | terminals |
| 6     | pmos      |
| 6     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


| count |           |
|-------|-----------|
| 11    | nets      |
| 6     | terminals |
| 6     | pmos      |
| 6     | nmos      |

Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin1 |
| 4 | vin5 |
| 5 | y    |
| 6 | z    |


The net-lists match.

## Schematic

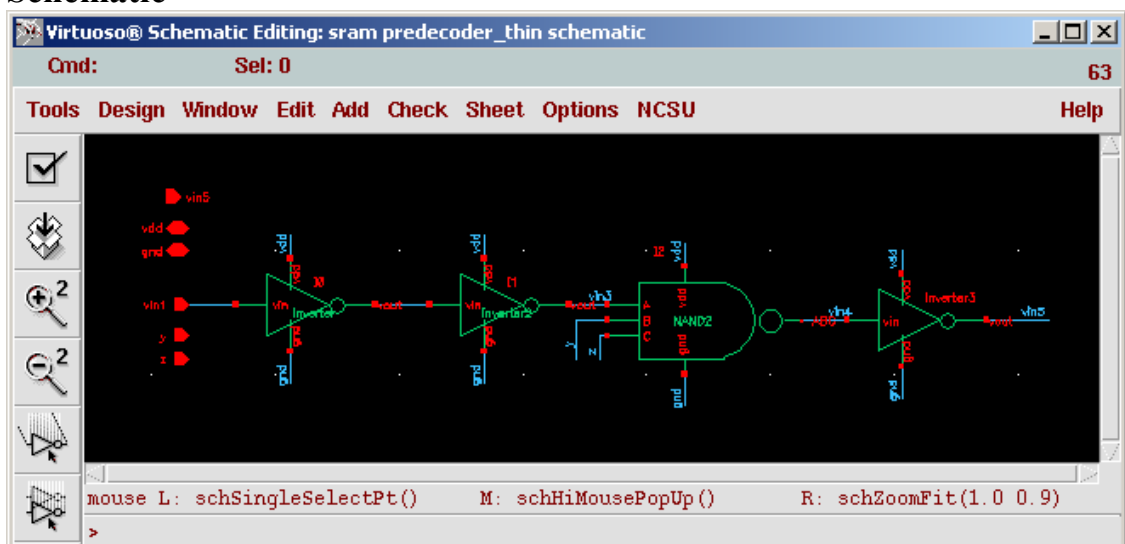




### Predecoder+Postdecoder +SRAM

 

The metal 1 (blue) wires are gnd and vdd. These wires will be re-wired for final layout.

## Schematic

 



## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 21    | nets      |
| 0     | terminals |
| 12    | pmos      |
| 14    | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 21    | nets      |
| 9     | terminals |
| 12    | pmos      |
| 14    | nmos      |

4 net-list ambiguities were resolved by random selection.


The net-lists match.

## Rewiring SRAM Cell

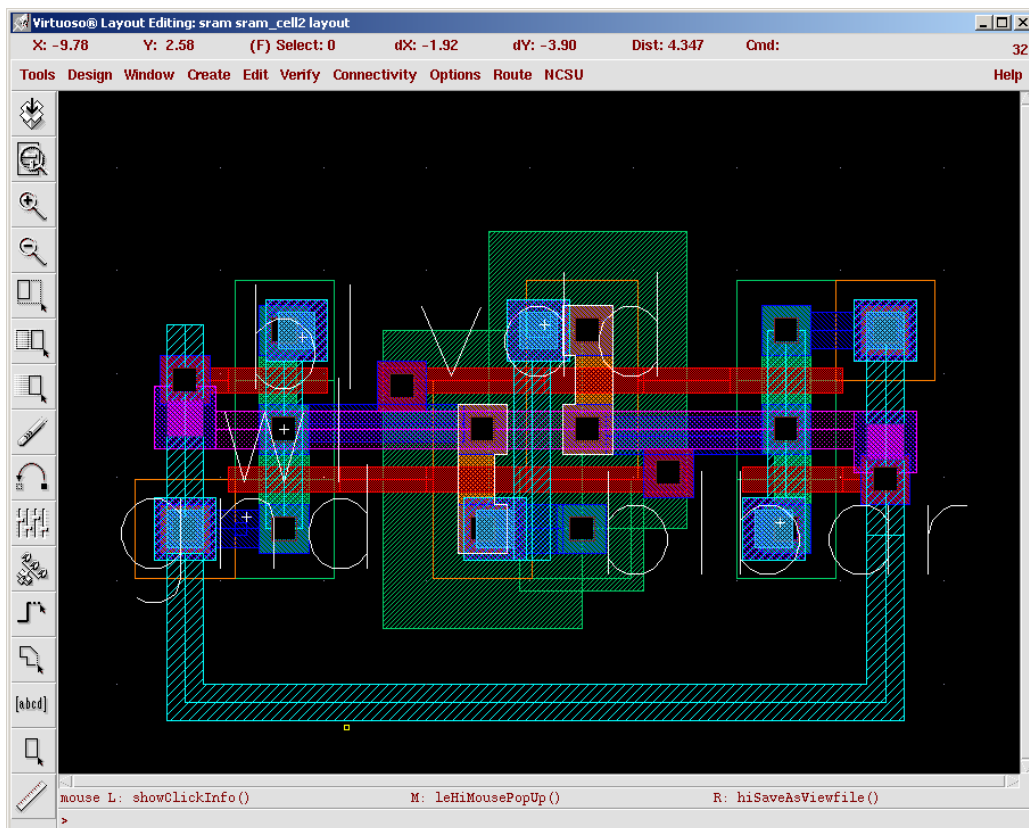

Rewired the SRAM cell changing metal 2 to metal 3, metal 3 to metal 2.

## Schematic

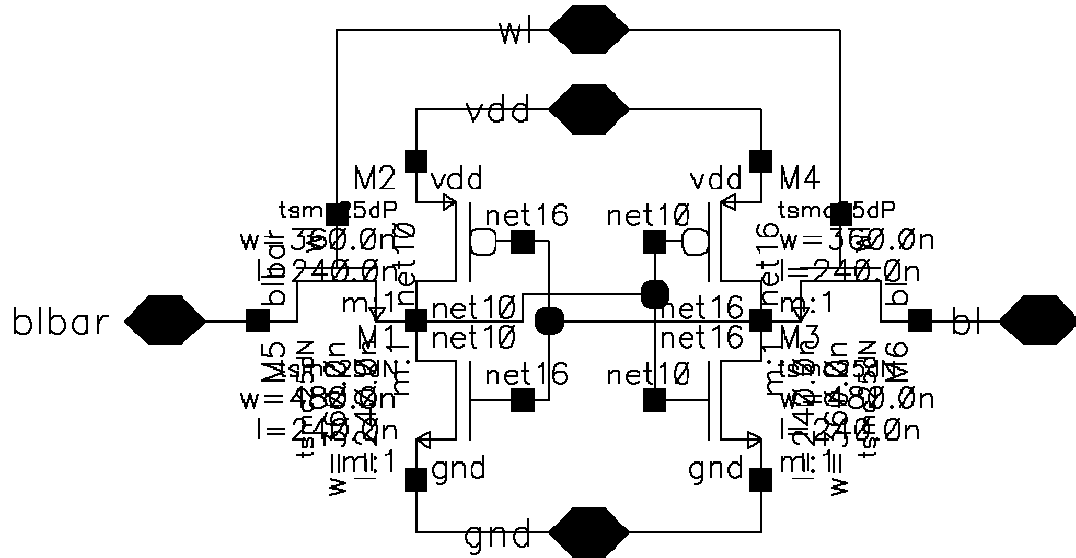

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 7     | nets      |
| 5     | terminals |
| 2     | pmos      |
| 4     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 7     | nets      |
| 5     | terminals |
| 2     | pmos      |
| 4     | nmos      |

Terminal correspondence points

|   |       |
|---|-------|
| 1 | bl    |
| 2 | blbar |
| 3 | gnd   |
| 4 | vdd   |
| 5 | wl    |

The net-lists match.

## LVS Results (For Decoder with Re-wired SRAM Cell)

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 21    | nets      |
| 0     | terminals |
| 12    | pmos      |
| 14    | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 21    | nets      |
| 9     | terminals |
| 12    | pmos      |
| 14    | nmos      |


4 net-list ambiguities were resolved by random selection.

The net-lists match.
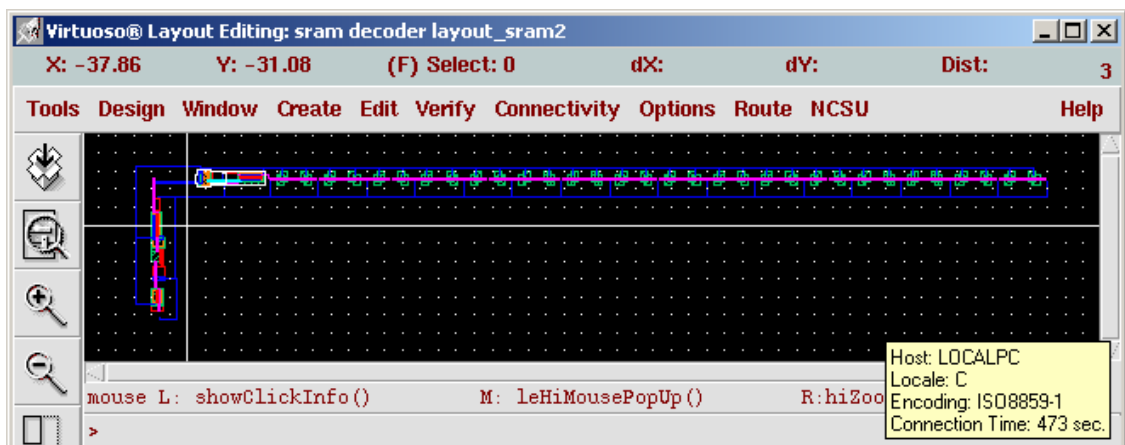
## Predecoder+Postdecoder+Array of Re-wired SRAM Cells



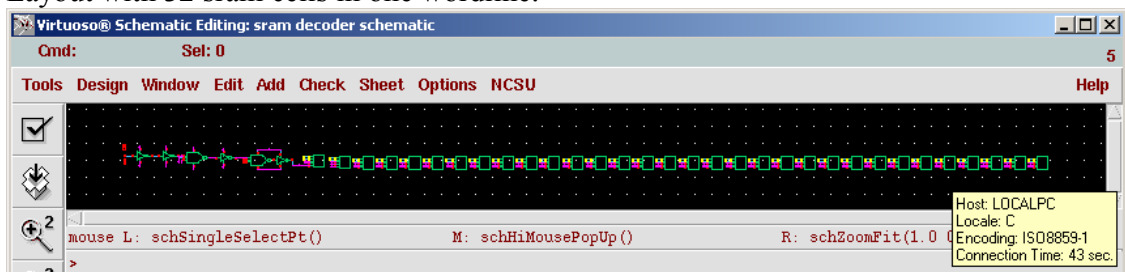Layout with 32 sram cells in one wordline.



Schematic with 32 sram cells

**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 145   | nets      |
| 0     | terminals |
| 74    | pmos      |
| 138   | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 145   | nets      |
| 7     | terminals |
| 74    | pmos      |
| 138   | nmos      |

35 net-list ambiguities were resolved by random selection.


The net-lists match.

One Wordline HSPICE Extraction

one\_wordline\_final\_extraction.sp
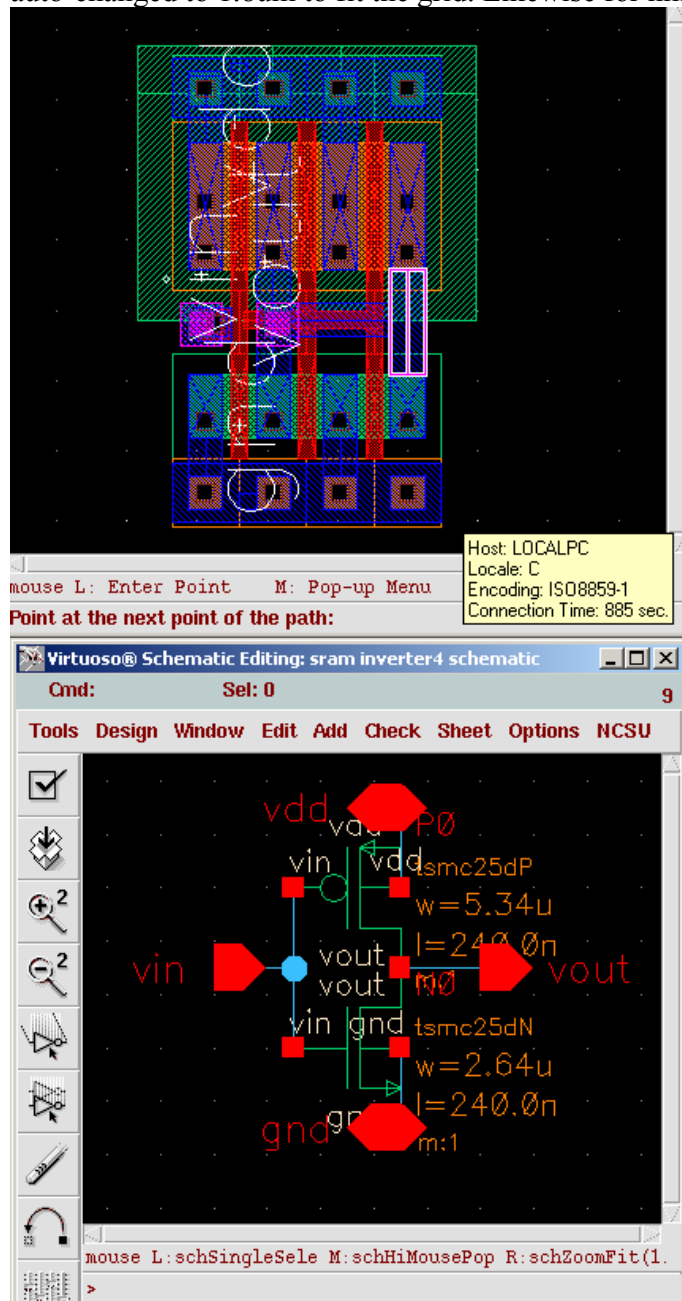
## Minimizing Inverter 4

Changed multiplier of 1 to multiplier of 3. Width changed from 5.34um to 1.78um. Then auto-changed to 1.8um to fit the grid. Likewise for nmos.



pmos

$$5.34/3 = 1.78 \rightarrow 1.8\mu\text{m}$$

nmos

$$2.64/3 = 0.88 \rightarrow 0.9\mu\text{m}$$

**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 3     | pmos      |
| 3     | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin  |
| 4 | vout |

The net-lists match.

 



## Minimizing Postdecoder NAND Gate

wanted to make the poly goes through the nmos instead of the pmos

But the poly are too close to the actives. So this doesn't work. (left, up)

Then I tried to put the contacts between pmos and nmos, but that makes the nand gate much longer. So this also doesn't work (left, down)

  At the end, the original nand gate design was used. (right)



## Minimizing the Whole Postdecoder

### LVS Results

audit.out:

I /IO/P0

? Combined device: Transistor width mismatch: layout 5.40 um, schematic 5.34 um

I /IO/N0


? Combined device: Transistor width mismatch: layout 2.70 um, schematic 2.64 um

Because using 3 multipliers, there are round-offs of half a lambda. I solved this problem by changing the schematics of inverter 4.

Inverter 4 schematic changes

Pmos 5.34->5.40

Nmos 2.64-> 2.70

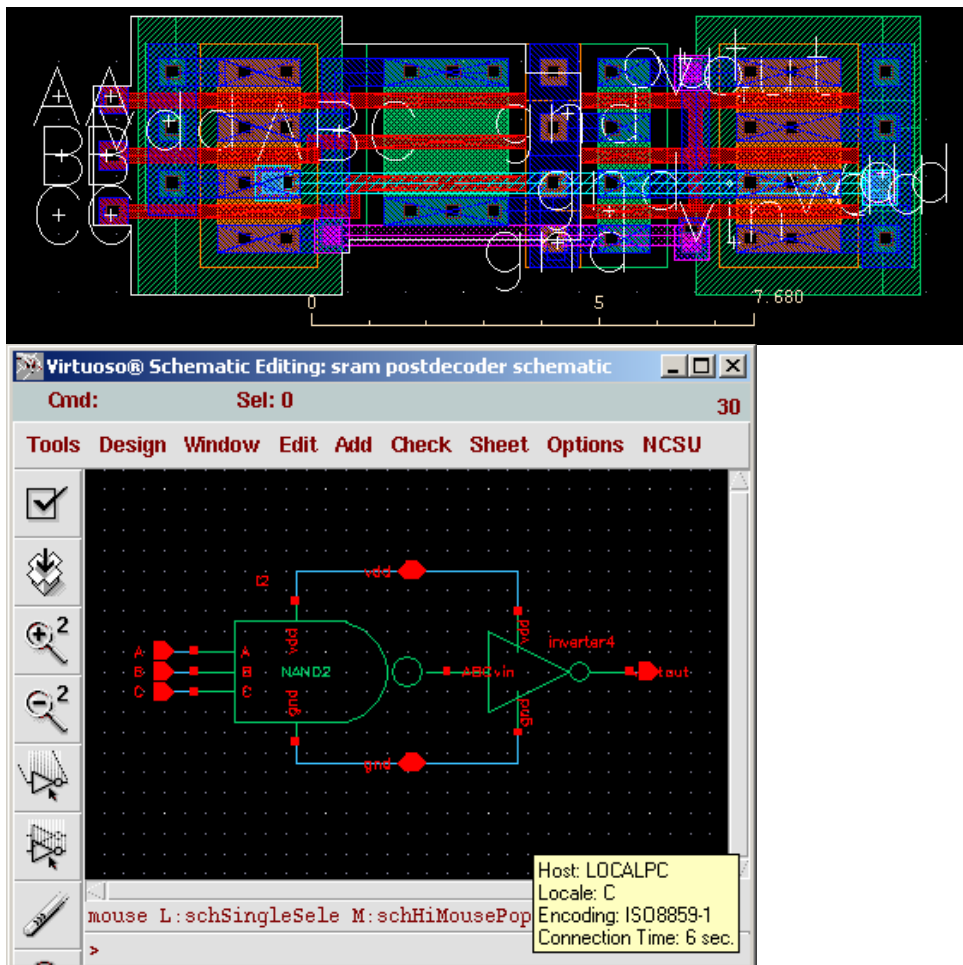



**LVS Results Match**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 9     | nets      |
| 6     | terminals |
| 6     | pmos      |
| 6     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 9     | nets      |
| 6     | terminals |
| 4     | pmos      |
| 4     | nmos      |

Terminal correspondence points

|   |     |
|---|-----|
| 1 | A   |
| 2 | B   |
| 3 | C   |
| 4 | gnd |
| 5 | out |
| 6 | vdd |

The net-lists match.

**Minimizing the Inverter 3**

Pmos  $5.4/-2=2.7\mu\text{m} \rightarrow 2.7\mu\text{m}$

Nmos  $2.7/2=1.35 \rightarrow 1.38\mu\text{m}$

**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 2     | pmos      |
| 2     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin  |
| 4 | vout |


The net-lists match logically but have mismatched parameters.

I / N0

? Combined device: Transistor width mismatch: layout 2.76 um, schematic 2.70 um

Changing the schematic to solve this half a lambda problem.

Nmos 2.7->2.76um

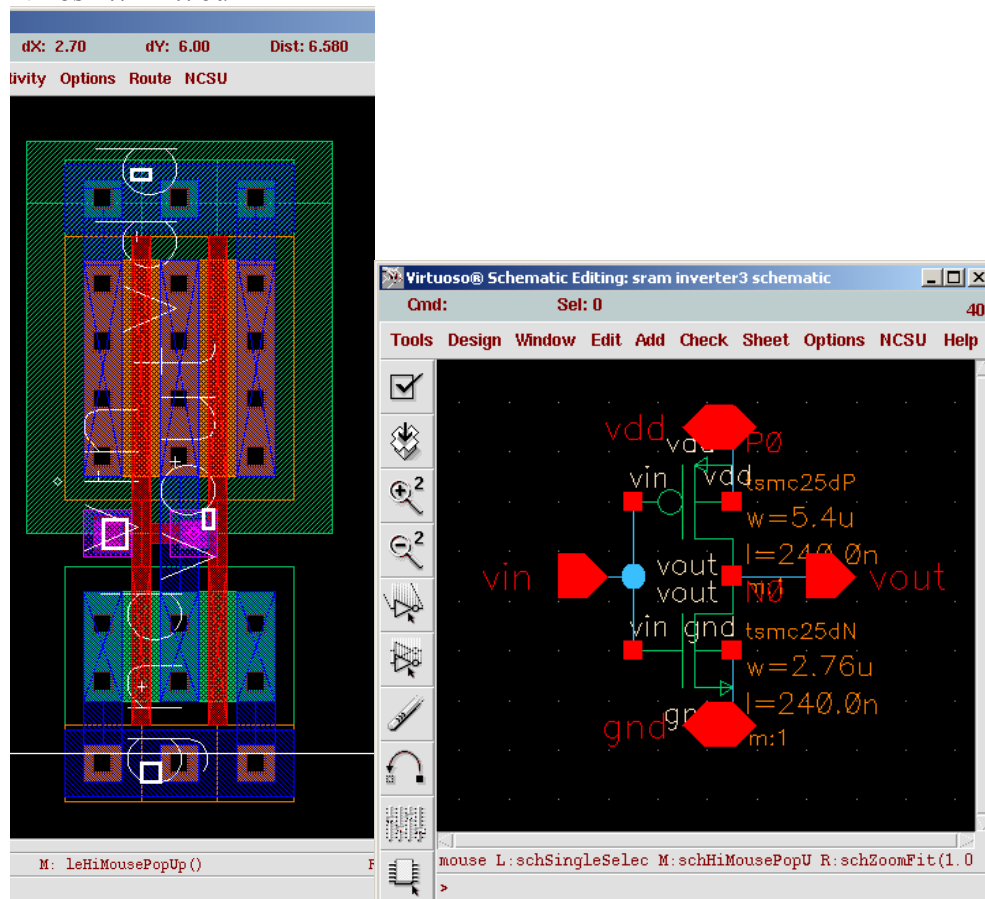

## LVS Results Match

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 2     | pmos      |
| 2     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Terminal correspondence points


|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin  |
| 4 | vout |

The net-lists match.
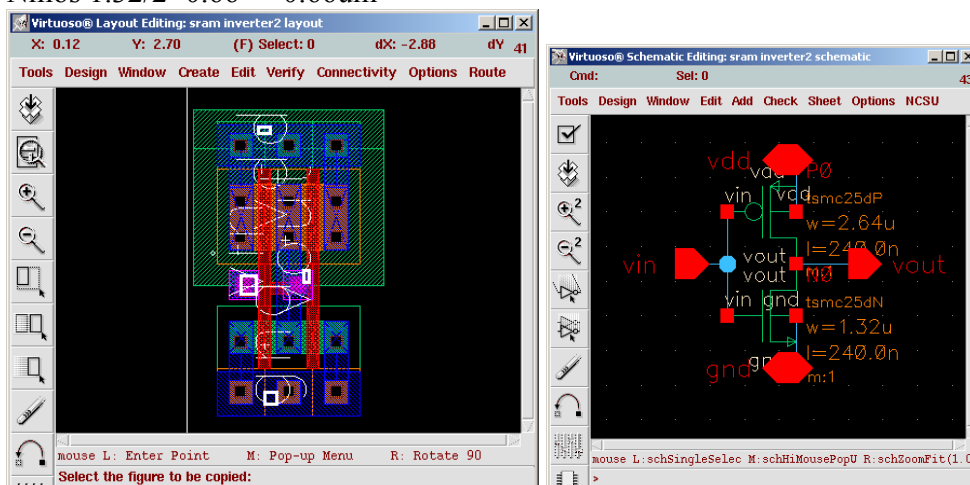
## Minimizing the Inverter 2

Pmos  $2.64/2=1.32\mu\text{m} \rightarrow 1.32\mu\text{m}$

Nmos  $1.32/2=0.66 \rightarrow 0.66\mu\text{m}$



Schematic values were not changed.

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 2     | pmos      |
| 2     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


|       |           |
|-------|-----------|
| count |           |
| 4     | nets      |
| 4     | terminals |
| 1     | pmos      |
| 1     | nmos      |

Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin  |
| 4 | vout |

The net-lists match.

## Minimizing the Whole Predecoder

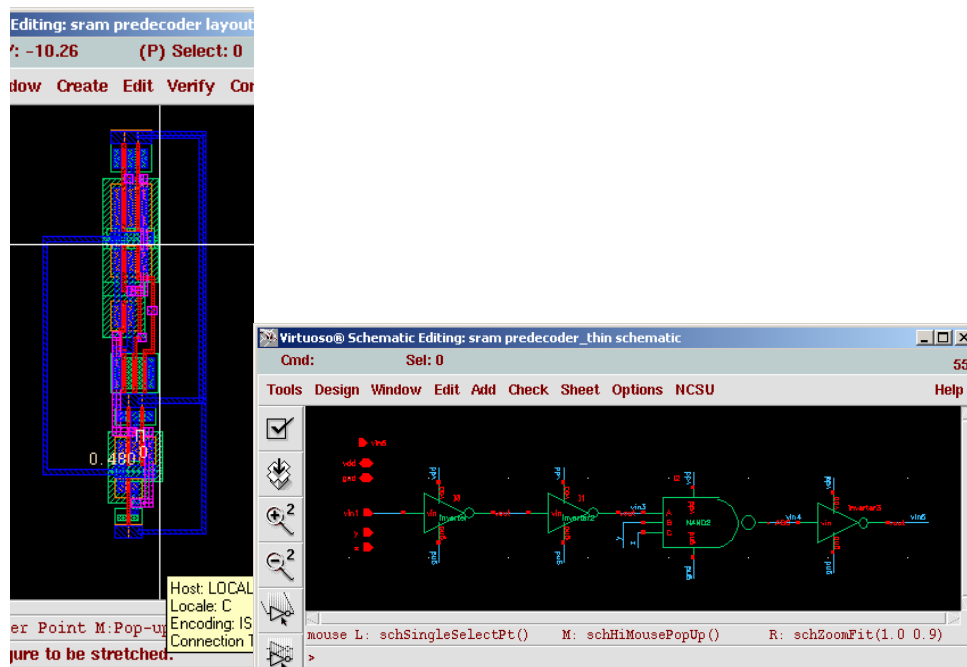

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 11    | nets      |
| 6     | terminals |
| 8     | pmos      |
| 8     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


|       |           |
|-------|-----------|
| count |           |
| 11    | nets      |
| 6     | terminals |
| 6     | pmos      |
| 6     | nmos      |


Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin1 |
| 4 | vin5 |
| 5 | y    |
| 6 | z    |

The net-lists match.
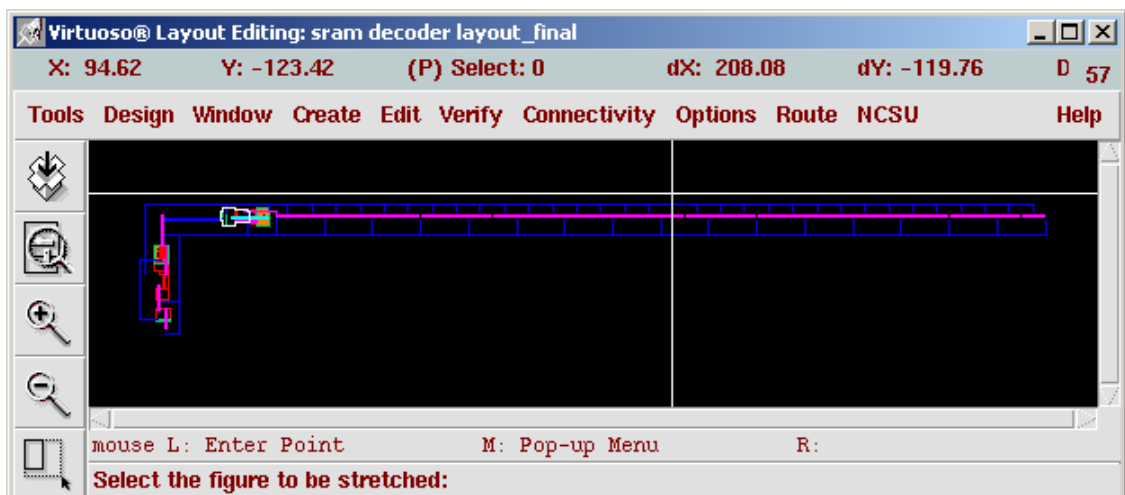
## Minimizing Predecoder+Postdecoder+SRAM Array



 

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 145   | nets      |
| 0     | terminals |
| 78    | pmos      |
| 142   | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 145   | nets      |
| 7     | terminals |
| 74    | pmos      |
| 138   | nmos      |


35 net-list ambiguities were resolved by random selection.

The net-lists match.

|                |           |           |   |
|----------------|-----------|-----------|---|
|                | layout    | schematic |   |
|                | instances |           |   |
| un-matched     | 0         | 0         |   |
| rewired        |           | 0         | 0 |
| size errors    | 0         | 0         |   |
| pruned         | 0         | 0         |   |
| active         | 220       | 212       |   |
| total          | 220       | 212       |   |
|                | nets      |           |   |
| un-matched     | 0         | 0         |   |
| merged         | 0         | 0         |   |
| pruned         | 0         | 0         |   |
| active         | 145       | 145       |   |
| total          | 145       | 145       |   |
|                | terminals |           |   |
| un-matched     | 0         | 0         |   |
| matched but    |           |           |   |
| different type | 0         | 0         |   |
| total          | 0         | 7         |   |


## Array of SRAM Cells (4x32 SRAM Cells)

### Schematics


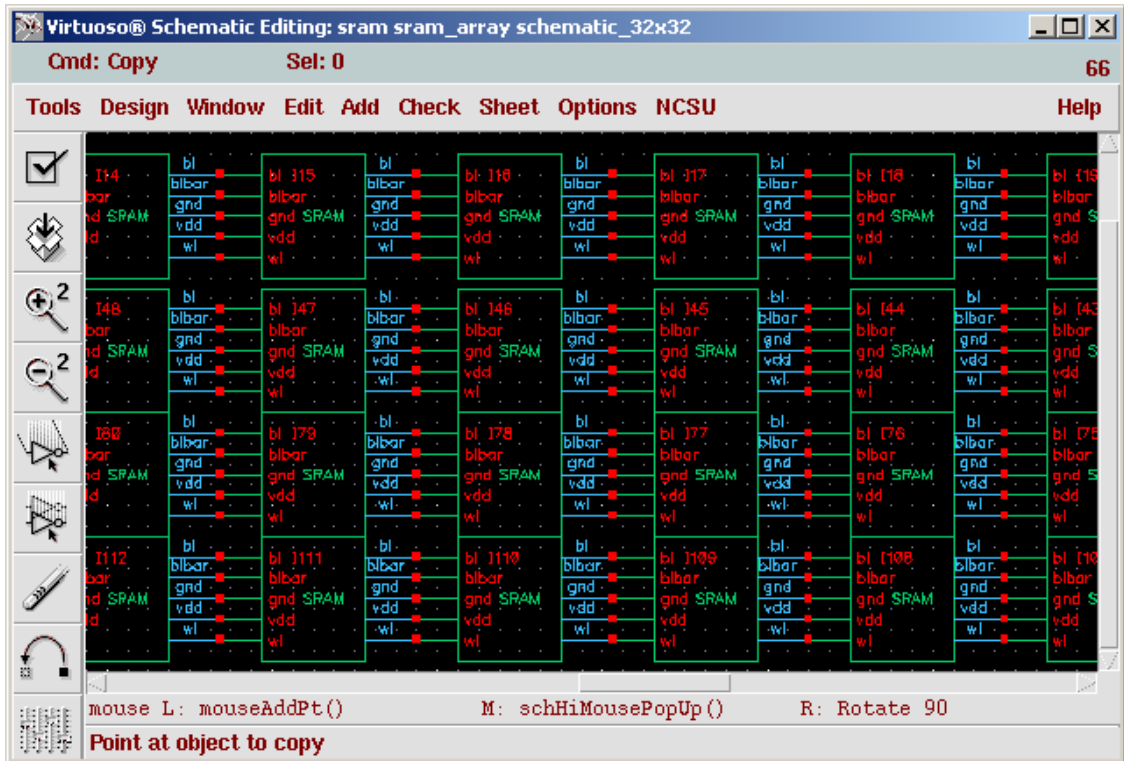


4 rows of 32 SRAM Cells Schematics.

### Layout

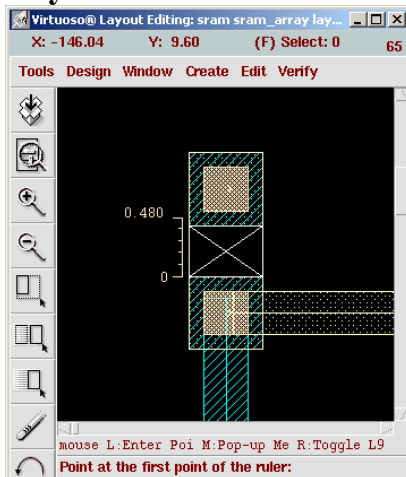

Metal 4 spacing, 4 lambda.

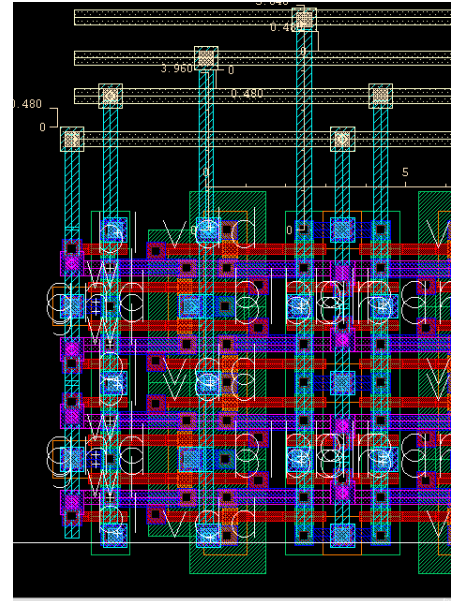 

(left) Connecting the gnd, bl, vdd, blbar through horizontal metal 4 layers.  
 (right) LVS passed 4x32 SRAM cells.

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 264   | nets      |
| 0     | terminals |
| 256   | pmos      |
| 512   | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 264   | nets      |
| 4     | terminals |
| 256   | pmos      |
| 512   | nmos      |


134 net-list ambiguities were resolved by random selection.

The net-lists match.



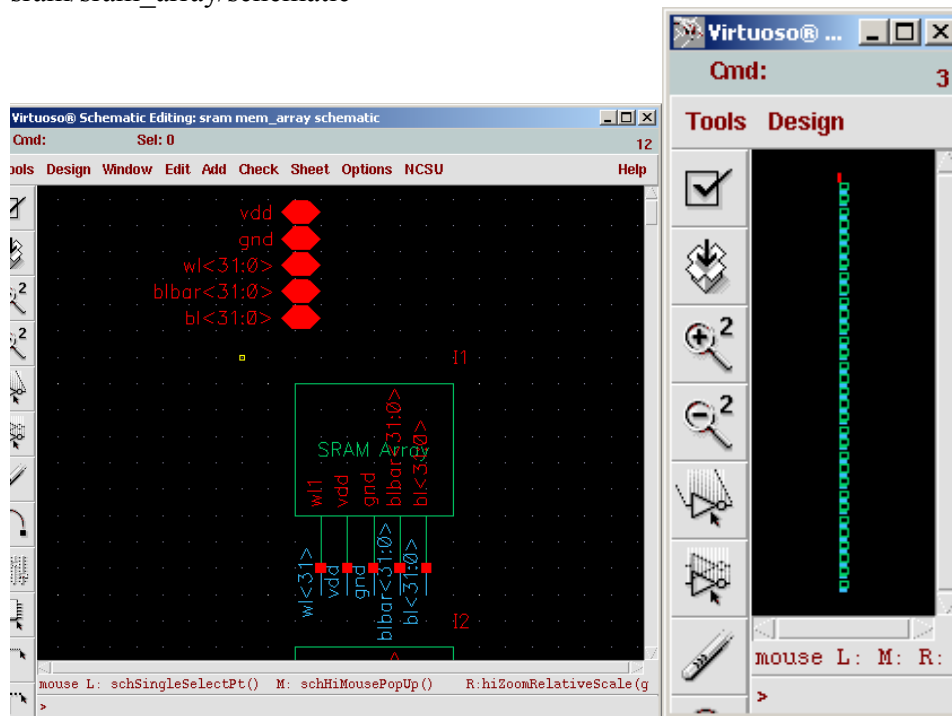
## SRAM Array (32x32)

Schematic= sram/mem\_array/schematic. Each symbol is an instantiation of sram/sram\_array/schematic



Layout = sram/sram\_array/layout\_row.

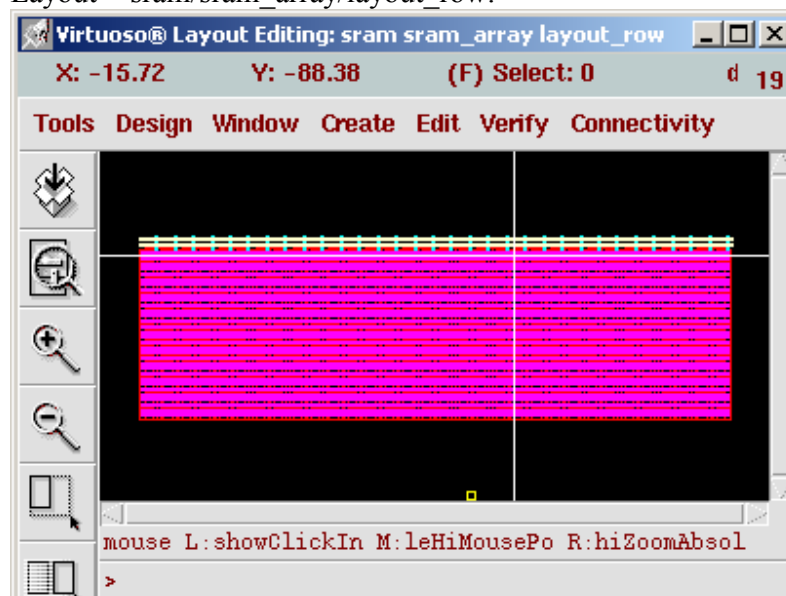

DRC pass. Extract pass.

**LVS Results**

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 2146  | nets      |
| 98    | terminals |
| 2048  | pmos      |
| 4096  | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 2146  | nets      |
| 98    | terminals |
| 2048  | pmos      |
| 4096  | nmos      |

Terminal correspondence points


|    |           |
|----|-----------|
| 1  | bl<0>     |
| 2  | bl<10>    |
| 3  | bl<11>    |
| 4  | bl<12>    |
| 5  | bl<13>    |
| 6  | bl<14>    |
| 7  | bl<15>    |
| 8  | bl<16>    |
| 9  | bl<17>    |
| 10 | bl<18>    |
| 11 | bl<19>    |
| 12 | bl<1>     |
| 13 | bl<20>    |
| 14 | bl<21>    |
| 15 | bl<22>    |
| 16 | bl<23>    |
| 17 | bl<24>    |
| 18 | bl<25>    |
| 19 | bl<26>    |
| 20 | bl<27>    |
| 21 | bl<28>    |
| 22 | bl<29>    |
| 23 | bl<2>     |
| 24 | bl<30>    |
| 25 | bl<31>    |
| 26 | bl<3>     |
| 27 | bl<4>     |
| 28 | bl<5>     |
| 29 | bl<6>     |
| 30 | bl<7>     |
| 31 | bl<8>     |
| 32 | bl<9>     |
| 33 | blbar<0>  |
| 34 | blbar<10> |

35    blbar<11>  
36    blbar<12>  
37    blbar<13>  
38    blbar<14>  
39    blbar<15>  
40    blbar<16>  
41    blbar<17>  
42    blbar<18>  
43    blbar<19>  
44    blbar<1>  
45    blbar<20>  
46    blbar<21>  
47    blbar<22>  
48    blbar<23>  
49    blbar<24>  
50    blbar<25>  
51    blbar<26>  
52    blbar<27>  
53    blbar<28>  
54    blbar<29>  
55    blbar<2>  
56    blbar<30>  
57    blbar<31>  
58    blbar<3>  
59    blbar<4>  
60    blbar<5>  
61    blbar<6>  
62    blbar<7>  
63    blbar<8>  
64    blbar<9>  
65    gnd  
66    vdd  
67    wl<0>  
68    wl<10>  
69    wl<11>  
70    wl<12>  
71    wl<13>  
72    wl<14>  
73    wl<15>  
74    wl<16>  
75    wl<17>  
76    wl<18>  
77    wl<19>  
78    wl<1>  
79    wl<20>  
80    wl<21>  
81    wl<22>  
82    wl<23>  
83    wl<24>  
84    wl<25>  
85    wl<26>  
86    wl<27>  
87    wl<28>  
88    wl<29>  
89    wl<2>


|    |        |
|----|--------|
| 90 | wl<30> |
| 91 | wl<31> |
| 92 | wl<3>  |
| 93 | wl<4>  |
| 94 | wl<5>  |
| 95 | wl<6>  |
| 96 | wl<7>  |
| 97 | wl<8>  |
| 98 | wl<9>  |

The net-lists match.


## Post Decoder Array (32 Instants)

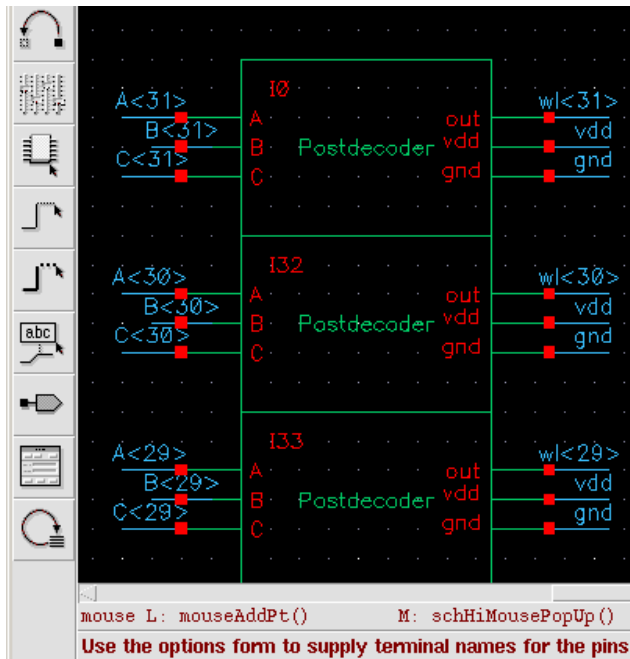

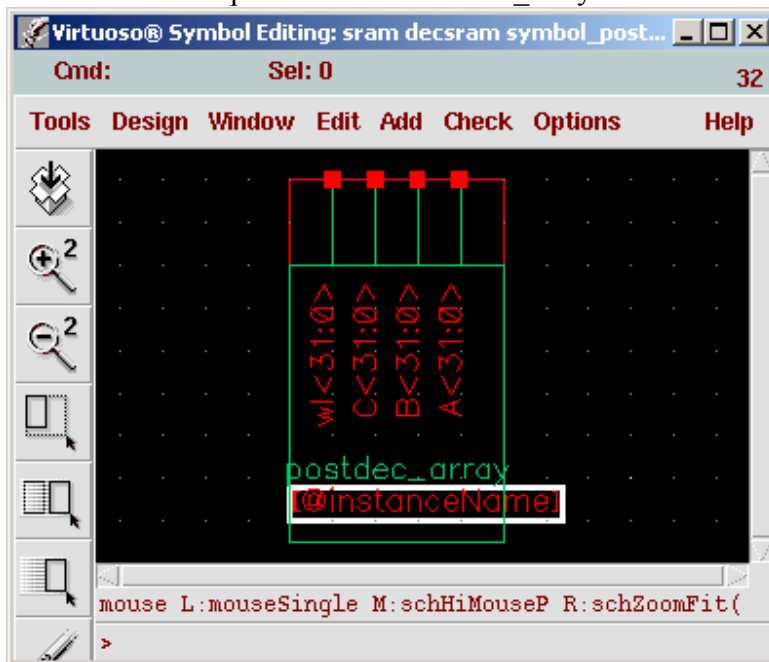Schematic= sram/postdecoder/schematic\_array. Instantiate sram/postdecoder/symbol.



Symbol=Sram/postdecoder/symbol\_array

 

Layout=sram/postdecoder/layout\_array

### LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 226   | nets      |
| 0     | terminals |
| 192   | pmos      |
| 192   | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 226   | nets      |
| 128   | terminals |
| 128   | pmos      |
| 128   | nmos      |

96 net-list ambiguities were resolved by random selection.


The net-lists match.

## LVS Window Screen from Labs

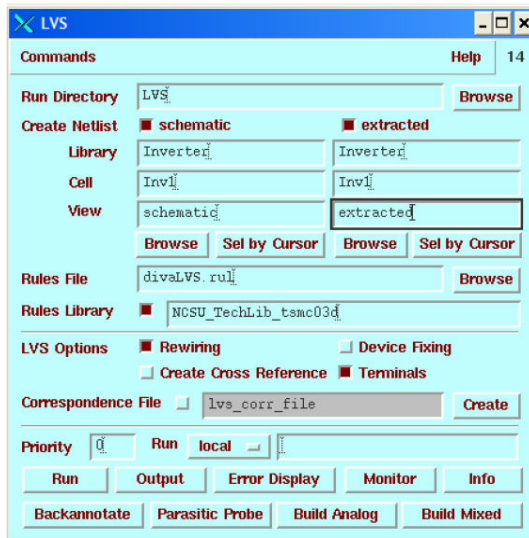

LVS from the lab
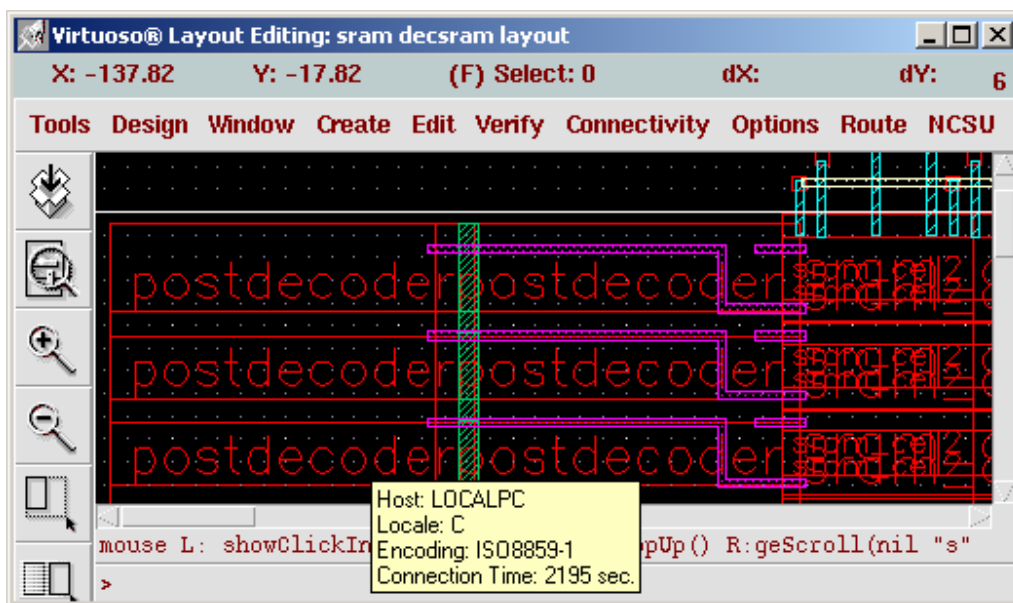
## 32x32 SRAM Cells + 32-Postdecoder Array



Layout = sram/dec\_sram/layout



LVS mysteriously doesn't even generate the report. Let's go back to the postdecoder array and do LVS on that first. (later) the postdecoder array works. But still got this error.

Found the error... I thought

**WARNING** dbSave: Failed to save cellView (decsram extracted). Disc quota exceeded

The error was never found. After 2 hours of finding why LVS failed. I gave up and drew the cell from scratch again. Then I passed LVS.

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 2146  | nets      |
| 98    | terminals |
| 2048  | pmos      |
| 4096  | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 2146  | nets      |
| 98    | terminals |
| 2048  | pmos      |
| 4096  | nmos      |

Terminal correspondence points


|    |        |
|----|--------|
| 1  | bl<0>  |
| 2  | bl<10> |
| 3  | bl<11> |
| 4  | bl<12> |
| 5  | bl<13> |
| 6  | bl<14> |
| 7  | bl<15> |
| 8  | bl<16> |
| 9  | bl<17> |
| 10 | bl<18> |
| 11 | bl<19> |
| 12 | bl<1>  |
| 13 | bl<20> |
| 14 | bl<21> |
| 15 | bl<22> |
| 16 | bl<23> |
| 17 | bl<24> |
| 18 | bl<25> |
| 19 | bl<26> |
| 20 | bl<27> |
| 21 | bl<28> |
| 22 | bl<29> |
| 23 | bl<2>  |
| 24 | bl<30> |
| 25 | bl<31> |
| 26 | bl<3>  |
| 27 | bl<4>  |
| 28 | bl<5>  |
| 29 | bl<6>  |
| 30 | bl<7>  |




|    |           |
|----|-----------|
| 31 | bl<8>     |
| 32 | bl<9>     |
| 33 | blbar<0>  |
| 34 | blbar<10> |
| 35 | blbar<11> |
| 36 | blbar<12> |
| 37 | blbar<13> |
| 38 | blbar<14> |
| 39 | blbar<15> |
| 40 | blbar<16> |
| 41 | blbar<17> |
| 42 | blbar<18> |
| 43 | blbar<19> |
| 44 | blbar<1>  |
| 45 | blbar<20> |
| 46 | blbar<21> |
| 47 | blbar<22> |
| 48 | blbar<23> |
| 49 | blbar<24> |
| 50 | blbar<25> |
| 51 | blbar<26> |
| 52 | blbar<27> |
| 53 | blbar<28> |
| 54 | blbar<29> |
| 55 | blbar<2>  |
| 56 | blbar<30> |
| 57 | blbar<31> |
| 58 | blbar<3>  |
| 59 | blbar<4>  |
| 60 | blbar<5>  |
| 61 | blbar<6>  |
| 62 | blbar<7>  |
| 63 | blbar<8>  |
| 64 | blbar<9>  |
| 65 | gnd       |
| 66 | vdd       |
| 67 | wl<0>     |
| 68 | wl<10>    |
| 69 | wl<11>    |
| 70 | wl<12>    |
| 71 | wl<13>    |
| 72 | wl<14>    |
| 73 | wl<15>    |
| 74 | wl<16>    |
| 75 | wl<17>    |
| 76 | wl<18>    |
| 77 | wl<19>    |
| 78 | wl<1>     |
| 79 | wl<20>    |
| 80 | wl<21>    |
| 81 | wl<22>    |
| 82 | wl<23>    |
| 83 | wl<24>    |
| 84 | wl<25>    |
| 85 | wl<26>    |

|    |        |
|----|--------|
| 86 | wl<27> |
| 87 | wl<28> |
| 88 | wl<29> |
| 89 | wl<2>  |
| 90 | wl<30> |
| 91 | wl<31> |
| 92 | wl<3>  |
| 93 | wl<4>  |
| 94 | wl<5>  |
| 95 | wl<6>  |
| 96 | wl<7>  |
| 97 | wl<8>  |
| 98 | wl<9>  |

The net-lists match.

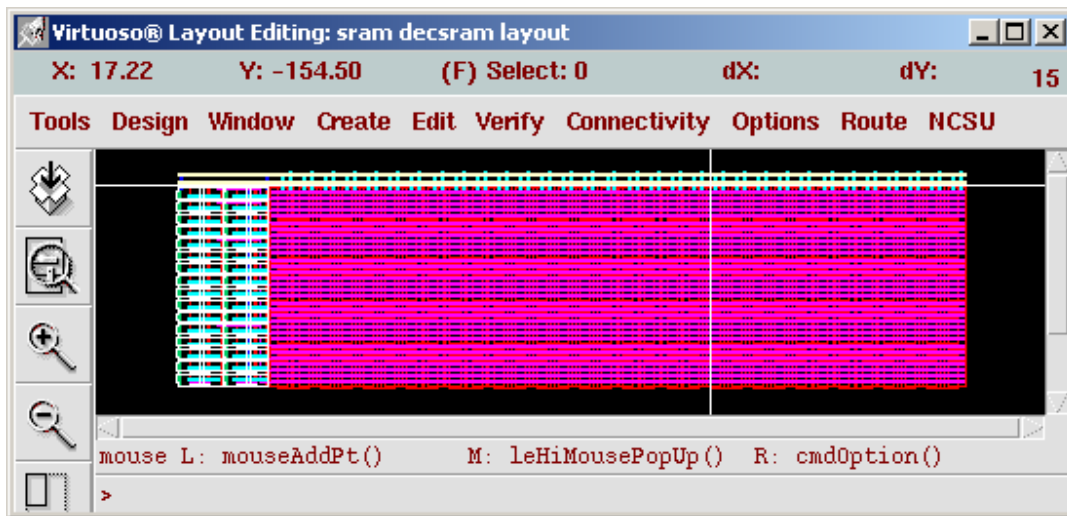


Layout= sram/dec\_sram/layout

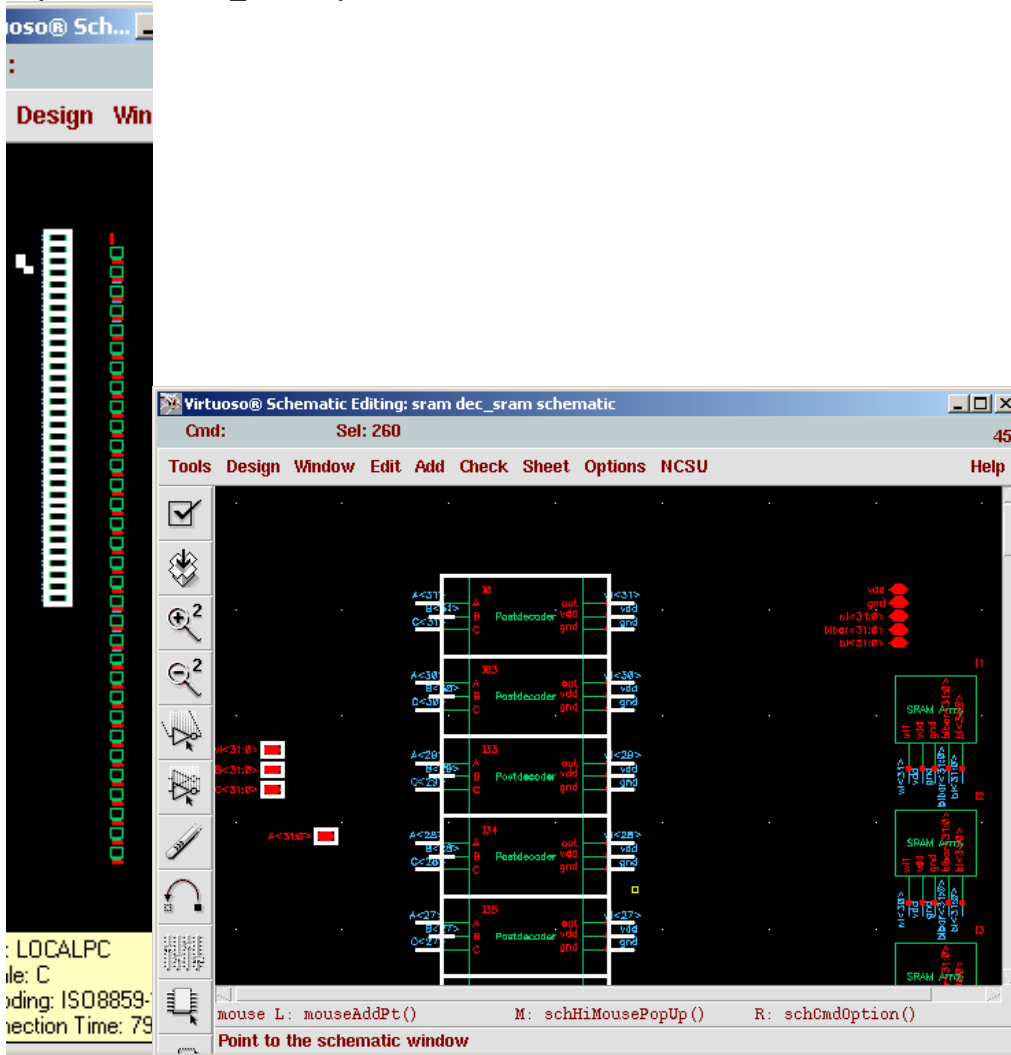


Schematic=sram/sram\_dec/schematic

## Predecoder Symbol

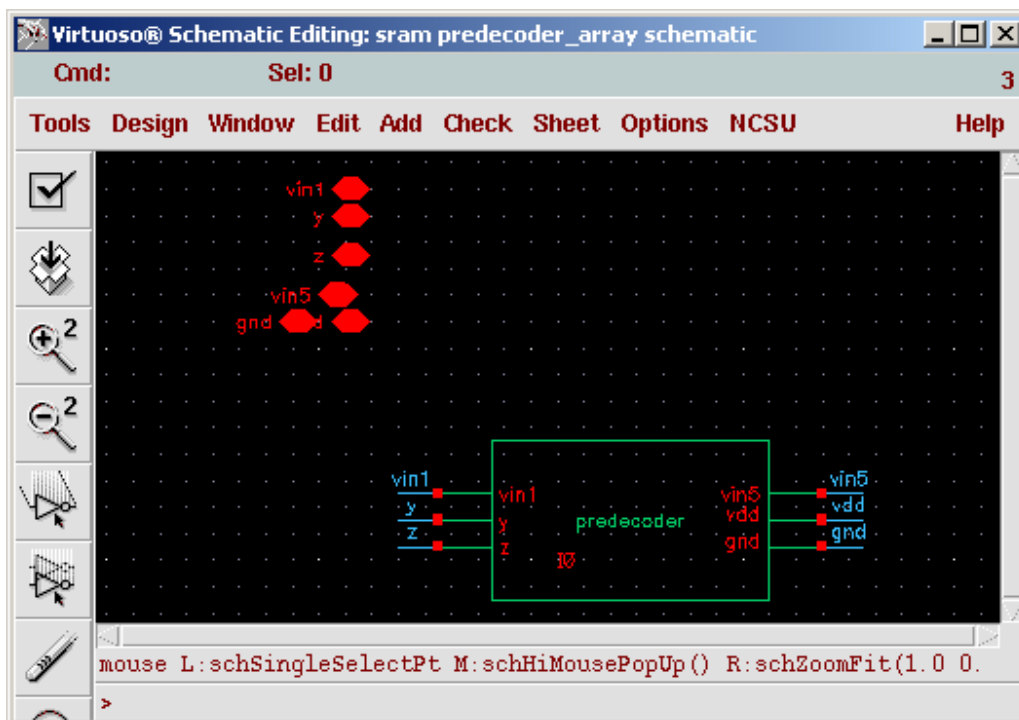

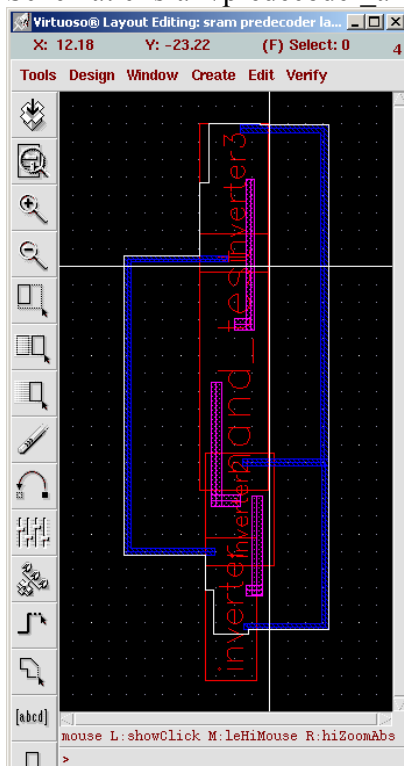Schematic=sram/predecoder\_array/schematic



Layout=sram/predecoder/layout\_final

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 11    | nets      |
| 6     | terminals |
| 8     | pmos      |
| 8     | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist


|       |           |
|-------|-----------|
| count |           |
| 11    | nets      |
| 6     | terminals |
| 6     | pmos      |
| 6     | nmos      |

Terminal correspondence points

|   |      |
|---|------|
| 1 | gnd  |
| 2 | vdd  |
| 3 | vin1 |
| 4 | vin5 |
| 5 | y    |
| 6 | z    |

The net-lists match.

## Predecoder Final

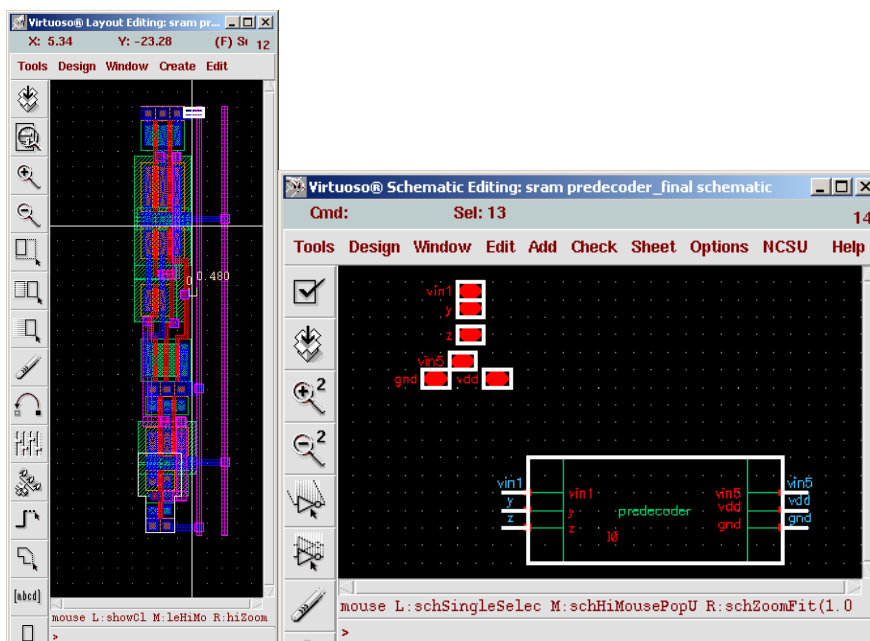

Layout=sram/predecoder\_final/layout, schematic= sram/predecoder\_final/schematic

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 131   | nets      |
| 0     | terminals |
| 64    | pmos      |
| 128   | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 131   | nets      |
| 67    | terminals |
| 64    | pmos      |
| 128   | nmos      |


33 net-list ambiguities were resolved by random selection.

The net-lists match.

## 2 Predecoder

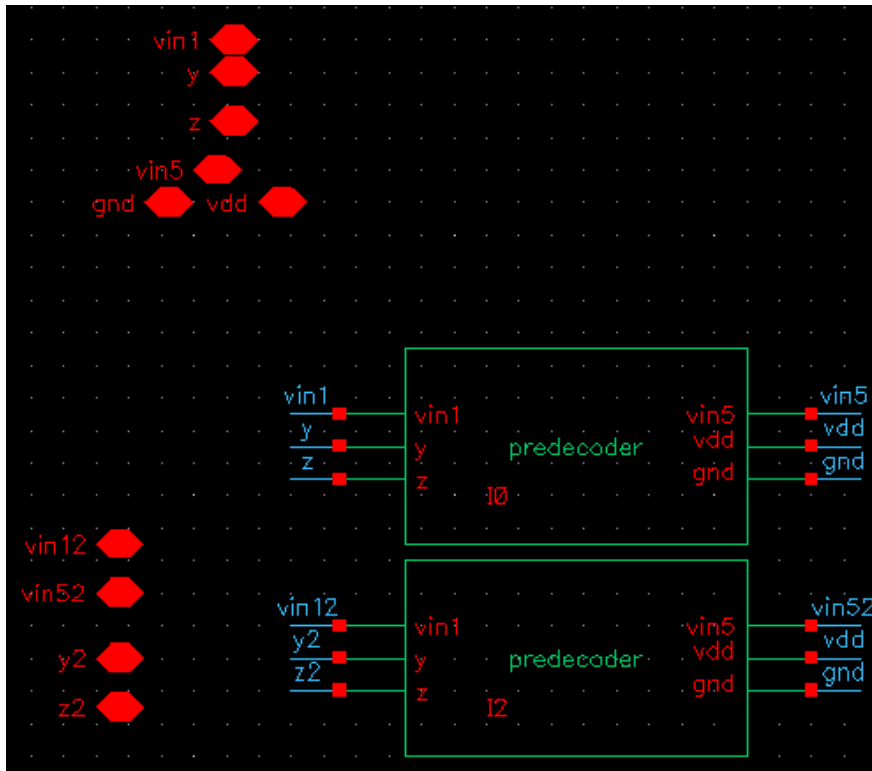

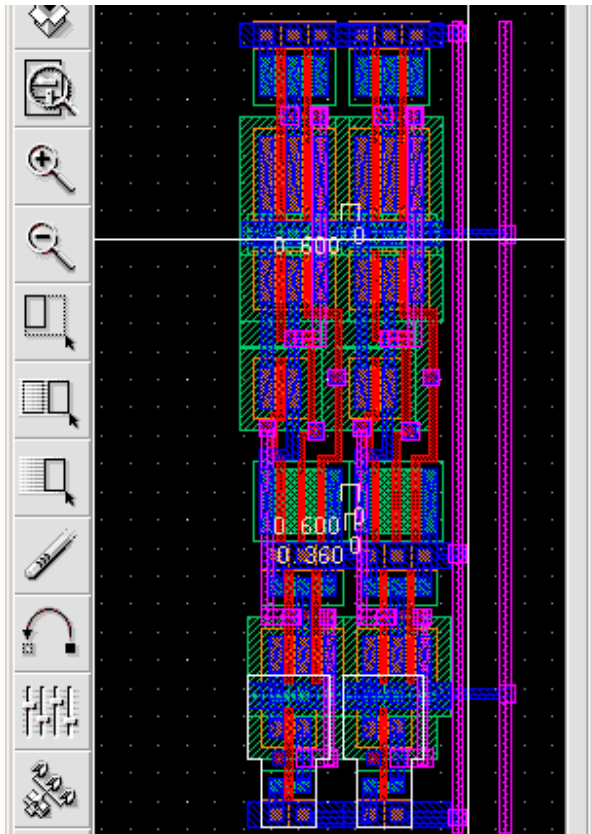Schematic=sram/predecoder\_array/schematic



Layout=sram/predecoder\_array/layout

### LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 20    | nets      |
| 0     | terminals |
| 16    | pmos      |
| 16    | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 20    | nets      |
| 10    | terminals |
| 12    | pmos      |
| 12    | nmos      |


4 net-list ambiguities were resolved by random selection.

The net-lists match.

## Predecoder Array (16 Instants)

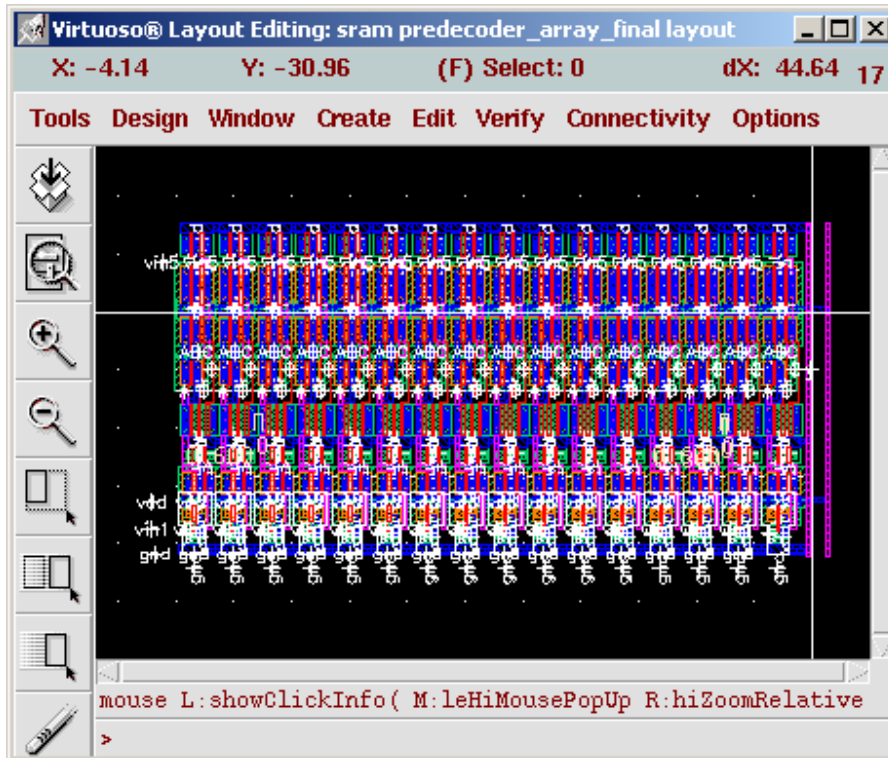

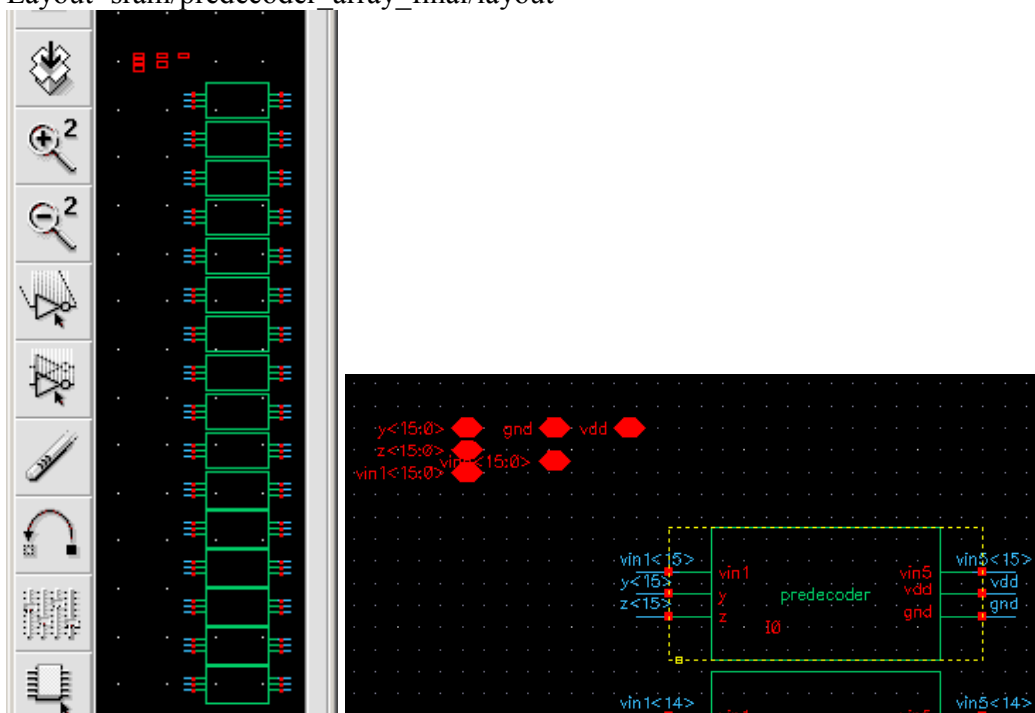Layout=sram/predecoder\_array\_final/layout



Schematic=sram/predecoder\_array\_final/schematic



## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 146   | nets      |
| 0     | terminals |
| 128   | pmos      |
| 128   | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 146   | nets      |
| 66    | terminals |
| 96    | pmos      |
| 96    | nmos      |

32 net-list ambiguities were resolved by random selection.

The net-lists match.

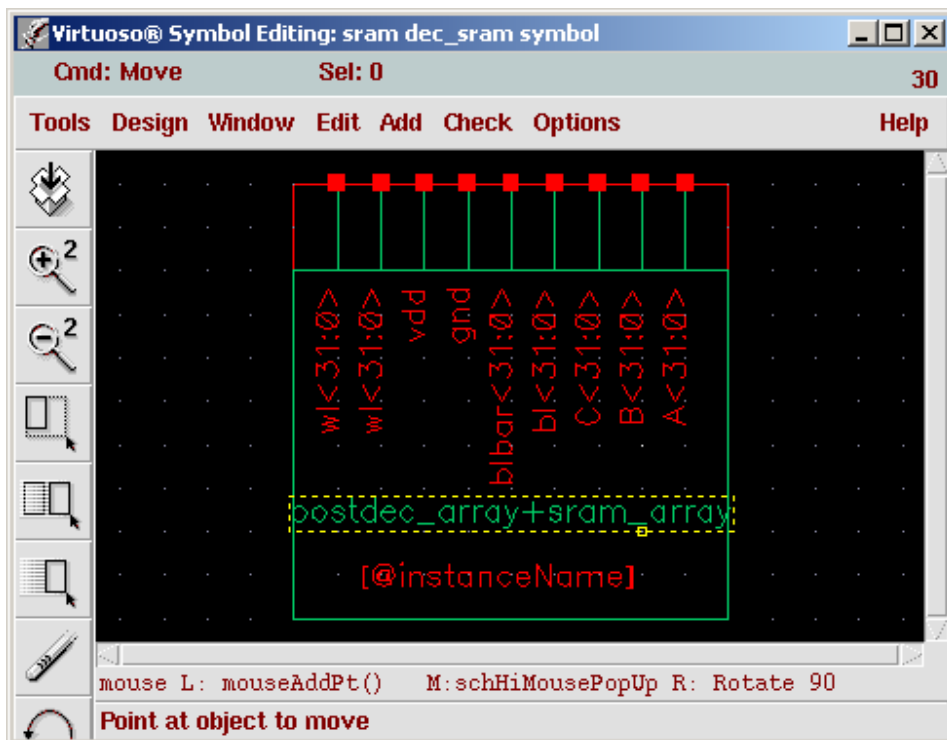
## 16-Predecoder + 32-Postdecoder + 32x32-SRAM




Symbol = sram/dec\_sram/symbol



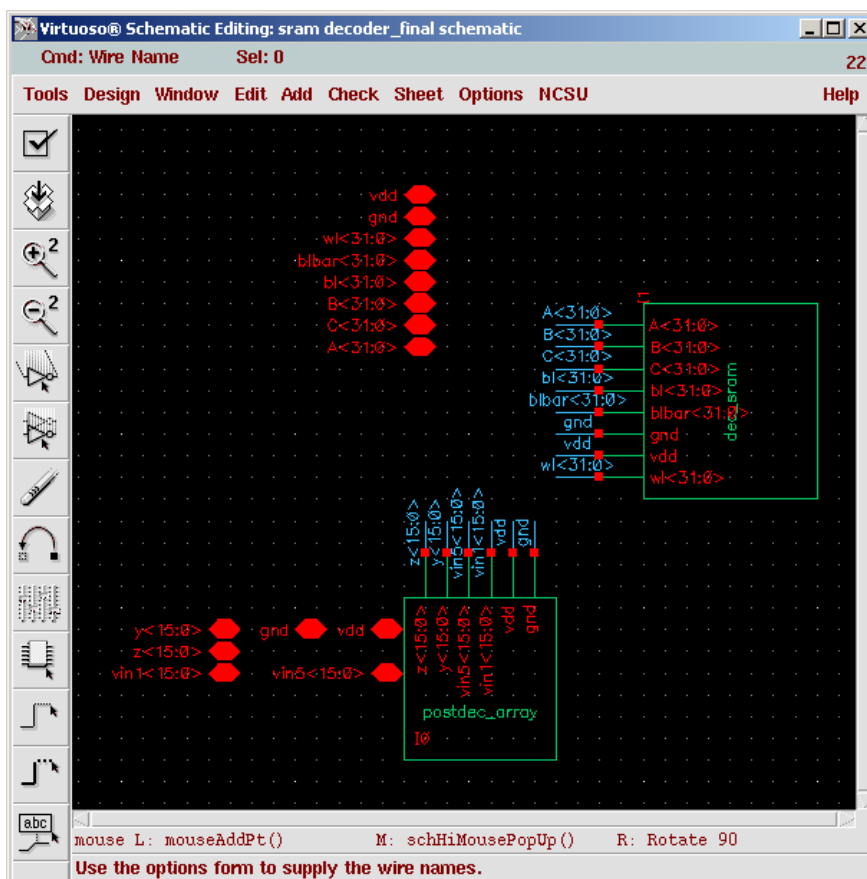Symbol=sram/predecoder\_array\_final/symbol



Schematic=sram/decoder\_final/schematic

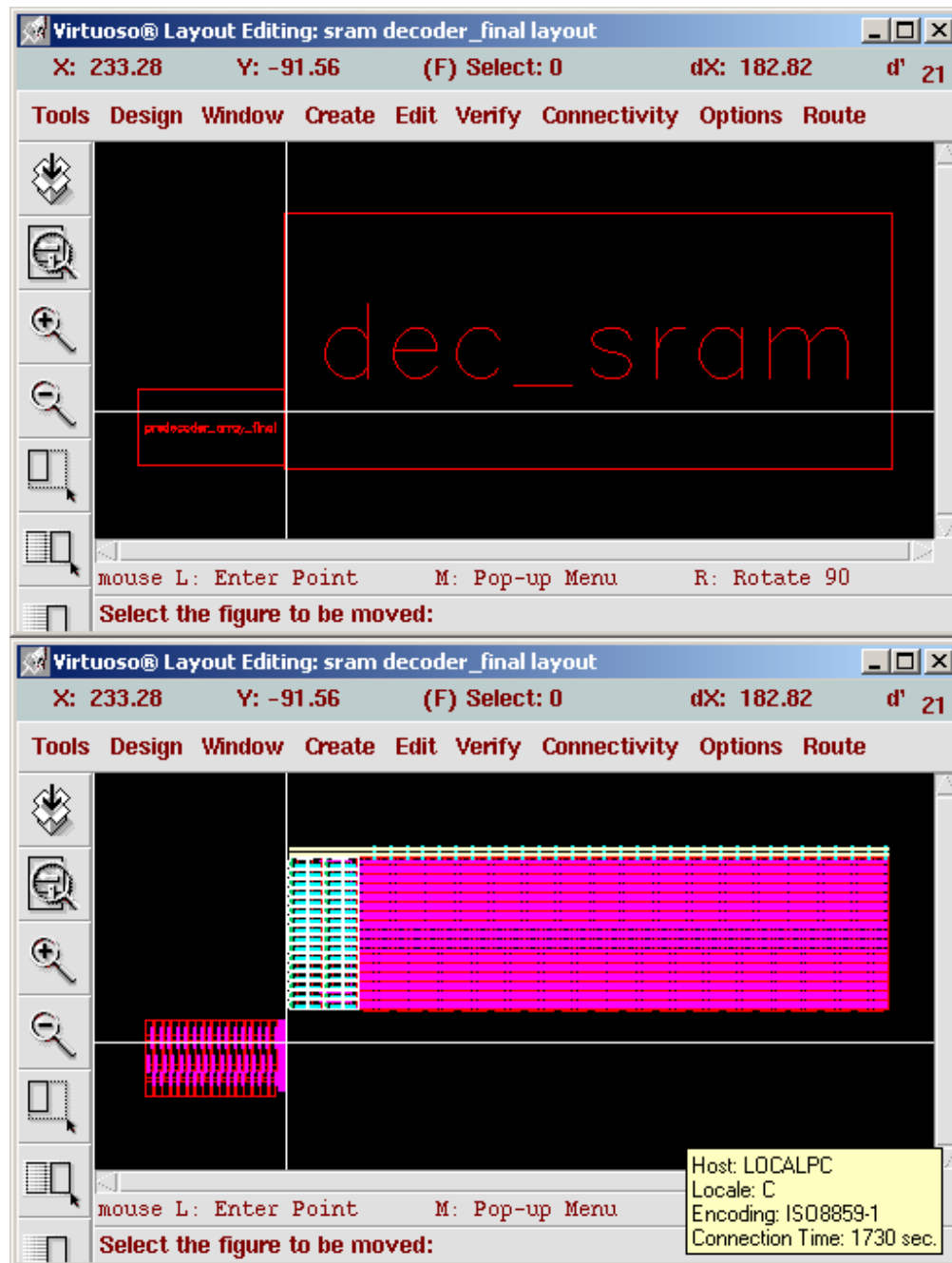

Layout=sram/decoder\_final/layout

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 2482  | nets      |
| 0     | terminals |
| 2368  | pmos      |
| 4416  | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 2482  | nets      |
| 258   | terminals |
| 2272  | pmos      |
| 4320  | nmos      |

161 net-list ambiguities were resolved by random selection.

The net-lists match.

## LVS (mysteriously) Failed

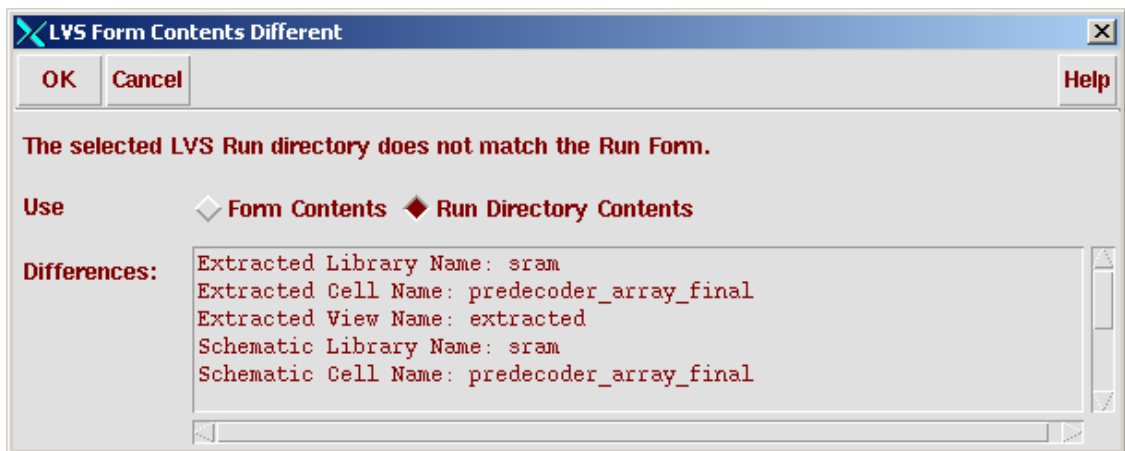

“OK”



Our group has had this LVS-failed problem for hours. We have re-done the procedure again and again, checked the lab procedures, but nothing could get rid of the LVS-failed problem. We made sure the account has plenty of quota. We are also sure we didn't delete any cadence files. We restarted Cadence, restarted the SSH, and we tried to login to cory and quasar to solve this

problem.

Suddenly all the cells that passed LVS before start giving us the  
LVS -failed message: "Job '/home/aa/ugrad/billhung/ee141/LVS' that was  
started at 'Mar 29 17:36:19 2006' has failed"  
None of the cells succeeds LVS anymore.

The log window has the following warning messages.

"

Running simulation in directory: "/home/aa/ugrad/billhung/ee141/LVS".

Begin netlist: Mar 29 17:36:20 2006  
view name list = ("auLvs" "extracted" "schematic")  
stop name list = ("auLvs")  
library name = "sram"  
cell name = "predecoder\_array\_final"  
view name = "extracted"  
globals lib = "basic"  
Running Artist Flat Netlisting ...  
End netlist: Mar 29 17:36:20 2006

Moving original netlist to extNetlist  
Removing parasitic components from netlist  
presistors removed: 0  
pcapacitors removed: 0  
pinductors removed: 0  
pdiodes removed: 0  
trans lines removed: 0  
146 nodes merged into 146 nodes

Begin netlist: Mar 29 17:36:20 2006  
view name list = ("auLvs" "schematic")  
stop name list = ("auLvs")  
library name = "sram"  
cell name = "predecoder\_array\_final"  
view name = "schematic"  
globals lib = "basic"  
Running Artist Flat Netlisting ...  
\*WARNING\* Couldn't get a write lock for  
"/home/aa/ugrad/billhung/ee141/LVS/schematic/map/current"  
Malformed Lock-Stake file.  
\*WARNING\* XXopen: failed to lock file  
/home/aa/ugrad/billhung/ee141/LVS/schematic/map/current in A\_MODE mode - is  
currently not locked.

global error:  
Unable to create /home/aa/ugrad/billhung/ee141/LVS/schematic/map/current  
file  
si: Netlist did not complete successfully.  
\*WARNING\* failed to open map file  
"/home/aa/ugrad/billhung/ee141/LVS/schematic/map/current"  
End netlist: Mar 29 17:36:20 2006

Comparison program did not complete.


"

What was the problem?


**Just delete the whole LVS folder. Or find the file described in the warning, and delete the lock file., or files that has an old timestamp.**



## Predecoder (8 Instants)

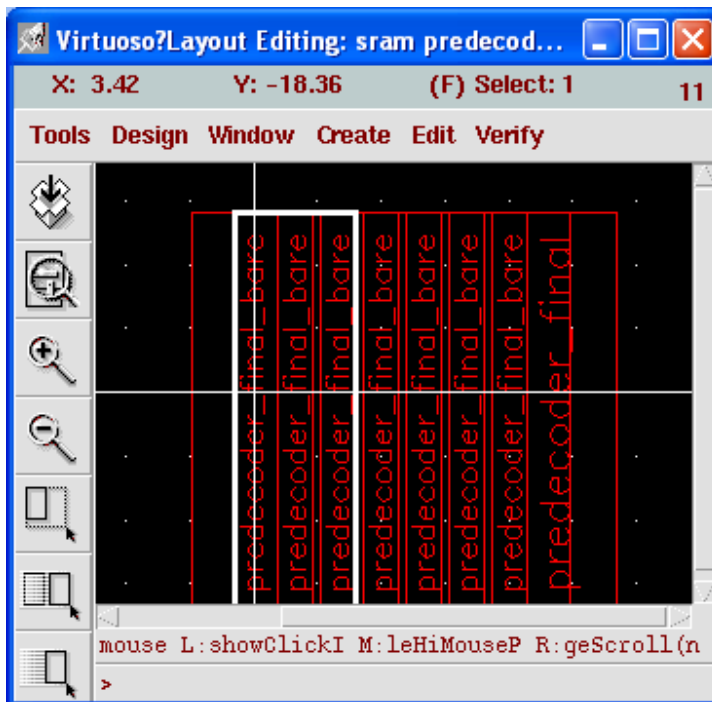

Layout=sram/predecoder\_8/layout

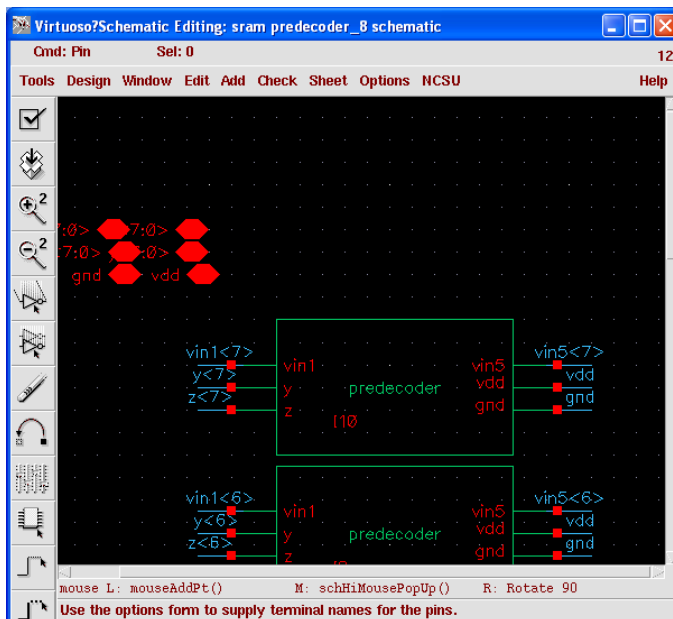

Schematic = sram/predecoder\_8/schematic

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

|       |           |
|-------|-----------|
| count |           |
| 74    | nets      |
| 0     | terminals |
| 64    | pmos      |
| 64    | nmos      |


Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

|       |           |
|-------|-----------|
| count |           |
| 74    | nets      |
| 34    | terminals |
| 48    | pmos      |
| 48    | nmos      |

16 net-list ambiguities were resolved by random selection.


The net-lists match.
 
## Minimizing Distance between Predecoder and Postdecoder



upper left=predecoder stage, lower right =postdecoderstage.

Minimizing distances.

 

Matching Pitches with the 2 predecoder stages. Lower left predecoder, upper right postdecoder.

## LVS Failed Error Again

Deleted all zero bytes files in

/home/aa/ugrad/billhung/ee141/sram/sram/decoder\_final/schematic

\*WARNING\* Couldn't get a write lock for

"/home/aa/ugrad/billhung/ee141/LVSnew/layout/map/current"

Malformed Lock-Stake file.

\*WARNING\* XXopen: failed to lock file

/home/aa/ugrad/billhung/ee141/LVSnew/layout/map/current in A\_MODE mode - is currently not locked.

global error:

Unable to create /home/aa/ugrad/billhung/ee141/LVSnew/layout/map/current file

si: Netlist did not complete successfully.



\*WARNING\* failed to open map file  
"/home/aa/ugrad/billhung/ee141/LVSnew/layout/map/current"  
End netlist: Mar 31 00:59:43 2006

Comparison program did not complete.

#### Deleted all zero bytes files in

/home/aa/ugrad/billhung/ee141/LVSnew/layout/map/current

Cellview (decoder\_final layout) from lib (sram) is saved in the panic file  
(/home/aa/ugrad/billhung/ee141/sram/sram/decoder\_final/layout/layout.cd-)

To recover do:


```
dbOpenPanicCellView("sram" "decoder_final" "layout")
```

All the saved panic files were logged in panic.log in your home directory


[1] Segmentation fault icfb

Solved the problem by not using the 32x32 SRAM array.

## 16-Postdecoder + 64-Predecoder

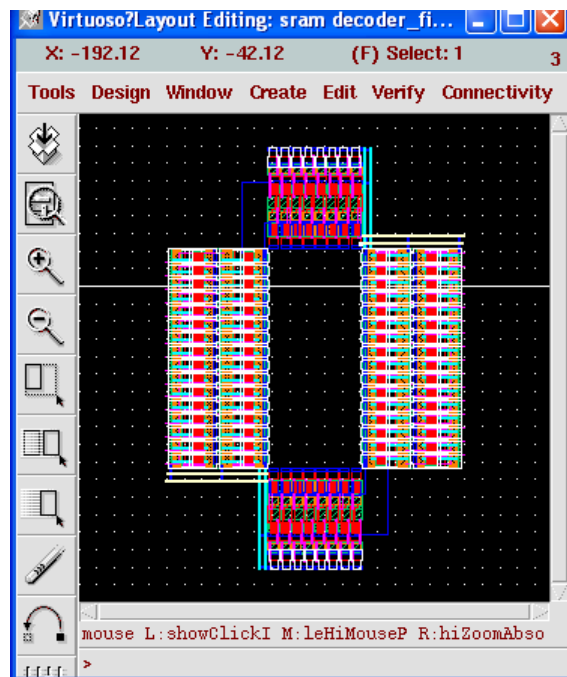

Layout=sram/decoder\_final/layout

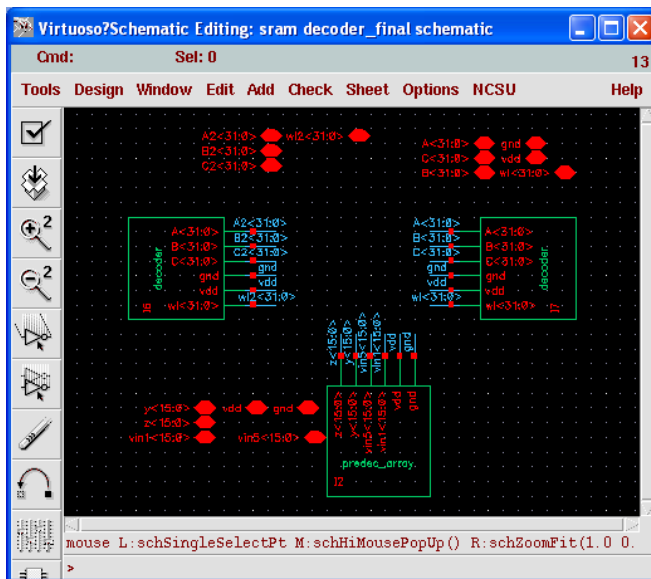

Schematic=sram/decoder\_final/schematic

## LVS Results

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/layout/netlist

| count |           |
|-------|-----------|
| 594   | nets      |
| 0     | terminals |
| 512   | pmos      |
| 512   | nmos      |

Net-list summary for /home/aa/ugrad/billhung/ee141/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 594   | nets      |
| 322   | terminals |
| 352   | pmos      |
| 352   | nmos      |

224 net-list ambiguities were resolved by random selection.

The net-lists match.


## Wire Branching Examples

1. Add instances from your library, such as this nand3 gate.

2. Add blocks to hold the place of an undetermined instance, such as this GATE\_REP.

3. Add schematic pins, such as this input pin.

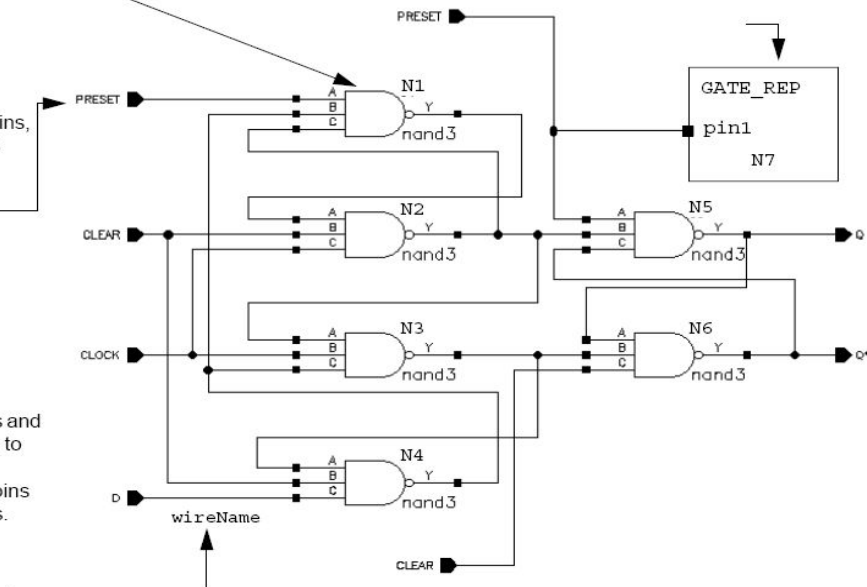4. Add wires and wire names to connect schematic pins to instances.



Use the suffix repeat operator  $\langle *n \rangle$  to repeat each bit in a group of bit names before expanding the vector term. For example, the following three names all describe the same six-bit wire:

$A\langle 0:2*2 \rangle$

$A\langle 0*2, 1*2, 2*2 \rangle$

$A\langle 0, 0, 1, 1, 2, 2 \rangle$