

Dynamic Logic

Table of contents

Finding Sizing for 5-stage Dynamic Logic	2
Matlab Code.....	2
Matlab Result.....	3
Sweeping Transistor – NAND Gate Test.....	4
HSPICE Code	4
Awave Result.....	4
Sweeping Transistor – NAND Gate with subcircuit.....	5
Sweep_transistor.sp	5
Sweep_transistor.sp	5
Gate.sp	6
Awave Result.....	7
Paramters.....	8
Sweeping Static Logic Transistors.....	8
Sweep Static Logic HSPICE.....	8
Awave Code.....	10
Dynamic Logic Gates.....	11
5-Stage Dynamic Logic that Does Not Work	12
HSPICE.....	12
Awaves.....	13
6-Stage Dynamic Logic.....	14
HSPICE.....	14
Awaves.....	16

Finding Sizing for 5-stage Dynamic Logic

Dynamic Logic chain with 3fF-not-nand-not-nand-not-cload. Try to find the sizing for HSPICE simulation.

Matlab Code

```
% Dynamic Logic
% 3fF-NOT-NAND-NOT-NAND-NOT-Cload
%Parameters
g1=1; g2=5/3; g3=1; g4=5/3; g5=1;
b1=1; b2=4; b3=1; b4=8; b5=1;
nstage=5;
%find cload
cw=5.5; %from HSPICE extraction
cox=6; co=0.31; w=0.36; l=0.24;
cg = cox*w*l + 2*co*w;
cload = cw + 2*cg*32
%Find h
G=g1*g2*g3*g4*g5; B=b1*b2*b3*b4*b5; F=(cload)/(3*cg);
H=G*B*F
h=H^(1/nstage)
%Find f
f(1)=h/(b1*g1);
f(2)=h/(b2*g2);
f(3)=h/(b3*g3);
f(4)=h/(b4*g4);
f(5)=h/(b5*g5);
s(5)=(cload)/f(5); s(4)=s(5)/f(4);
s(3)=s(4)/f(3); s(2)=s(3)/f(2);
s(1)=s(2)/f(1)

% add cw1
g1=1; g2=1; g3=5/3; g4=1;
b1=1; b2=4; b3=1; b4=1;
nstage2=4;
cw1=1.8641; %from HSPICE
cload = s(5)*8+cw1;
F2 = (cload)/(3*cg);
%cw1 is M4 of the predecoder = 1.8641
B2= b1*b2*b3*b4;
G2 = g1*g2*g3*g4;
H2 = F2* G2* B2
h2 = H2^(1/nstage2)
f1(1)=h2/(b1*g1);
f1(2)=h2/(b2*g2);
f1(3)=h2/(b3*g3);
f1(4)=h2/(b4*g4);
s1(4)=(cload)/f1(4);
s1(3)=s1(4)/f1(3);
s1(2)=s1(3)/f1(2);
s1(1)=s1(2)/f1(1);
%get w
```

```
cox=6; co=0.31; w=0.36; l=0.24;
cg = cox*w*l + 2*co*w;
inv_min = 3*cg;
nand3_min = 5*cg;
w(5)=s(5)/nand3_min;
w(4)=s1(4)/inv_min;
w(3)=s1(3)/nand3_min;
w(2)=s1(2)/inv_min;
w(1)=s1(1)/inv_min
```

Matlab Result

```
cload = 52.9624
H = 2.1160e+003
h = 4.6249
s = Columns 1 through 2
    2.2248    10.2895
Columns 3 through 4
    7.1383    33.0139
Column 5
    11.4515
H2 = 280.1037
h2 =
    4.0910
w =
Columns 1 through 2
    1.0000    4.0910
Columns 3 through 4
    2.5104    10.2702
Column 5
    3.0883
```

Sweeping Transistor – NAND Gate Test


Trying to sweep logic gate sizes in HSPICE.

HSPICE Code

```
one transistor sweep
.lib '/home/ff/ee141/MODELS/g25.mod' TT
*****
* Parameter
*****
.param vddp = 2.5
.param wnmin='0.36u'
.param wpmin='2*wnmin'
.param multiplier = 2.0449
*****
* Sources
*****
Vdd vdd 0 'vddp'
Vin vin1 0 pulse(0v 2.5v 0.1n 50ps 50ps 5ns 10ns)
*****
* Netlist
*****
.subckt NAND3 Vdd Gnd VinA VinB VinC Vout
Mp1 Vout VinA Vdd Vdd pmos l=0.24u w='wpmin'
Mp2 Vout VinB Vdd Vdd pmos l=0.24u w='wpmin'
Mp3 Vout VinC Vdd Vdd pmos l=0.24u w='wpmin'
Mn1 Vmid1 VinA Gnd Gnd nmos l=0.24u w='wnmin*3'
Mn2 Vmid2 VinB Vmid1 Gnd nmos l=0.24u w='wnmin*3'
Mn3 Vout VinC Vmid2 Gnd nmos l=0.24u w='wnmin*3'
.ends

xnand vdd 0 vin1 vdd vdd vout NAND3 M=multiplier
cout vout 0 13f
*****
* Analysis
*****
*nomod= no model info from library
.options post=2 nomod
*.op makes hspice determines DC operating point
.op
.tran 0.05ns 10ns sweep multiplier 1 5 1
.end
```

Awave Result

 

Sweeping Transistor – NAND Gate with subcircuit

Sweep one NAND gate with subcircuit in another file.

Sweep_transistor.sp

one transistor sweep

```
.lib '/home/ff/ee141/MODELS/g25.mod' TT
.inc 'gate.sp'

*****
* Parameter
*****
.param vddp = 2.5
.param wnmin='0.36u'
.param wpmin='2*wnmin'
.param multiplier = 2.0449
*****
* Sources
*****
Vdd vdd 0 'vddp'
Vin vin1 0 pulse(0v 2.5v 0.1n 50ps 50ps 5ns 10ns)
*****
* Netlist
*****

xnand vdd 0 vin1 vdd vdd vout NAND3 M='multiplier'
cout vout 0 13f

*****
* Analysis
*****
*nomod= no model info from library
.options post=2 nomod
*.op makes hspice determines DC operating point
.op

.tran 0.05ns 10ns sweep multiplier 1 5 1
.end
```

Sweep_transistor.sp

one transistor sweep

```
.lib '/home/ff/ee141/MODELS/g25.mod' TT
.inc 'gate.sp'
```

```

*****
* Parameter
*****

.param vddp = 2.5
.param wnmin='0.36u'
.param wpmin='2*wnmin'
.param multiplier = 2.0449
*****

* Sources
*****

Vdd vdd 0 'vddp'
Vin vin1 0 pulse(0v 2.5v 0.1n 50ps 50ps 5ns 10ns)
*****

* Netlist
*****

xnand vdd 0 vin1 vdd vdd vout NAND3 M='multiplier'
cout vout 0 13f

*****

* Analysis
*****

*nomod= no model info from library
.options post=2 nomod
*.op makes hspice determines DC operating point
.op

.tran 0.05ns 10ns sweep multiplier 1 5 1
.end

```

Gate.sp

```

.param wnmin='0.36u'
.param wpmin='2*wnmin'

.subckt INV vin vout vdd vss
M1 vout vin vss vss nmos l=0.24u w='wnmin'
M2 vout vin vdd vdd pmos l=0.24u w='wpmin'
.ends

.subckt NAND3 Vdd Gnd VinA VinB VinC Vout
Mp1 Vout VinA Vdd Vdd pmos l=0.24u w='wpmin'
Mp2 Vout VinB Vdd Vdd pmos l=0.24u w='wpmin'

```

```


Mp3 Vout VinC Vdd Vdd pmos l=0.24u w='wpmin'
Mn1 Vmid1 VinA Gnd Gnd nmos l=0.24u w='wnmin*3'
Mn2 Vmid2 VinB Vmid1 Gnd nmos l=0.24u w='wnmin*3'
Mn3 Vout VinC Vmid2 Gnd nmos l=0.24u w='wnmin*3'
.ends

.subckt Sram Vdd Gnd vword vbit vbitbar
  *M<name> <drain> <gate> <source> <bulk> <model> <geometry>
M0 2 5 Vdd Vdd pmos L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M1 Vdd 2 5 Vdd pmos L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M2 2 5 0 0 nmos L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6
M=1
M3 0 2 5 0 nmos L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9
M=1
M4 vbit vword 2 0 nmos L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9
M=1
M5 5 vword vbitbar 0 nmos L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6
M=1
.ends

.subckt NOR Vdd Gnd VinA VinB Vout
Mp1 Vout VinA Vdd Vdd pmos l=0.24u w=0.6u
Mp2 Vout VinB Vdd Vdd pmos l=0.24u w=0.6u
Mn1 Vout VinA vmid Gnd nmos l=0.24u w=0.72u
Mn2 vmid VinB Gnd Gnd nmos l=0.24u w=0.72u
.ends

```

Awave Result

 

Parameters

$C_w = 12.60438 \text{ fF}$
 $C_{w1} = 1.8641 \text{ fF}$
 SRAM pitch = $1.92 \mu\text{m}$
 PMOS-NMOS ratio: 1.6 (Rabaey, 2009)

Sweeping Static Logic Transistors

The goal is to find the optimal delay by sweeping the width of transistors used in the decoder circuit.

Sweep Static Logic HSPICE

PHASE II DYNAMIC LOGIC

.lib '/home/ff/ee141/MODELS/g25.mod' TT

.inc 'logic.sp'

* Parameter

.param vddp = 2.5

.param multi_nand1 = 4.09

.param multi_inv2 = 2.51

.param multi_nand3 = 10.27

.param multi_inv3 = 3.0

* Sources

Vdd vdd 0 'vddp'

* params = vlow vhigh delay rise fall pulse_width period

* example VIN IN GND PULSE 0 5 .5n .1n .1n .5n 2n

Vin vin1 0 pulse(0v 2.5v 0.1n 50ps 50ps 5ns 10ns)

* Netlist

xinv1 vin1 vin2 vdd 0 INV

xnand1_b1 vdd 0 vdd vdd vin2 vin3 NAND3 M='multi_nand1'

xnand1_b2 vdd 0 0 0 vin2 x NAND3 M='multi_nand1'

xnand1_b3 vdd 0 0 0 vin2 y NAND3 M='multi_nand1'

xnand1_b4 vdd 0 0 0 vin2 z NAND3 M='multi_nand1'

xinv2 vin3 vin4 vdd 0 INV M='multi_inv2'

cw1 vin5 0 1.8641f

xnand2_b1 vdd 0 vdd vdd vin4 vin5 NAND3 M='multi_nand3'

xnand2_b2 vdd 0 0 0 vin5 a NAND3 M='multi_nand3'

xnand2_b3 vdd 0 0 0 vin5 b NAND3 M='multi_nand3'


```

xnand2_b4 vdd 0 0 0 vin5 c NAND3 M='multi_nand3'
xnand2_b5 vdd 0 0 0 vin5 d NAND3 M='multi_nand3'
xnand2_b6 vdd 0 0 0 vin5 e NAND3 M='multi_nand3'
xnand2_b7 vdd 0 0 0 vin5 f NAND3 M='multi_nand3'
xnand2_b8 vdd 0 0 0 vin5 g NAND3 M='multi_nand3'
xinv3 vin5 vout vdd 0 INV M='multi_inv3'
cload vout 0 12.60438fF

```

* SRAM Chain

```

xsram0 vdd 0 vout vbit0 vbitbar0 Sram
xsram1 vdd 0 vout vbit1 vbitbar1 Sram
xsram2 vdd 0 vout vbit2 vbitbar2 Sram
xsram3 vdd 0 vout vbit3 vbitbar3 Sram
xsram4 vdd 0 vout vbit4 vbitbar4 Sram
xsram5 vdd 0 vout vbit5 vbitbar5 Sram
xsram6 vdd 0 vout vbit6 vbitbar6 Sram
xsram7 vdd 0 vout vbit7 vbitbar7 Sram
xsram8 vdd 0 vout vbit8 vbitbar8 Sram
xsram9 vdd 0 vout vbit9 vbitbar9 Sram
xsram10 vdd 0 vout vbit10 vbitbar10 Sram
xsram11 vdd 0 vout vbit11 vbitbar11 Sram
xsram12 vdd 0 vout vbit12 vbitbar12 Sram
xsram13 vdd 0 vout vbit13 vbitbar13 Sram
xsram14 vdd 0 vout vbit14 vbitbar14 Sram
xsram15 vdd 0 vout vbit15 vbitbar15 Sram
xsram16 vdd 0 vout vbit16 vbitbar16 Sram
xsram17 vdd 0 vout vbit17 vbitbar17 Sram
xsram18 vdd 0 vout vbit18 vbitbar18 Sram
xsram19 vdd 0 vout vbit19 vbitbar19 Sram
xsram20 vdd 0 vout vbit20 vbitbar20 Sram
xsram21 vdd 0 vout vbit21 vbitbar21 Sram
xsram22 vdd 0 vout vbit22 vbitbar22 Sram
xsram23 vdd 0 vout vbit23 vbitbar23 Sram
xsram24 vdd 0 vout vbit24 vbitbar24 Sram
xsram25 vdd 0 vout vbit25 vbitbar25 Sram
xsram26 vdd 0 vout vbit26 vbitbar26 Sram
xsram27 vdd 0 vout vbit27 vbitbar27 Sram
xsram28 vdd 0 vout vbit28 vbitbar28 Sram
xsram29 vdd 0 vout vbit29 vbitbar29 Sram
xsram30 vdd 0 vout vbit30 vbitbar30 Sram
xsram31 vdd 0 vout vbit31 vbitbar31 Sram
cout vout 0 13f

```

* Analysis

*nomod= no model info from library

.options post=2 nomod

*.op makes hspice determines DC operating point

.op

.tran 0.01ns 11ns sweep multi_nand3 9.27 11.27 1 sweep multi_nand1 3.09 5.09 1 sweep
multi_inv3 3.09 5.09 1


.meas tran tplh trig V(vin1) val='(2.5*.5)' rise=1 targ V(vout)

+ val='(2.5*.5)' rise=1


.end

Awave Code

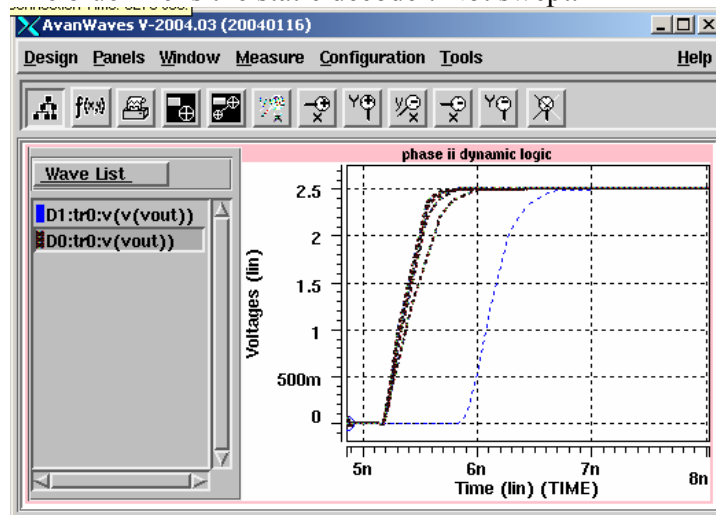
The blue line is the static decoder. Not swept.



The multiplier swept.

 


Dynamic Logic Gates

 

2-input-NAND with inverter [Nikolic, Lecture 19, page 12]

 3fF-NOT-NAND-NOT-NAND-NOT-Clod dynamic circuit



5-Stage Dynamic Logic that Does Not Work

The problem with 5-stages is when all inputs are on, the output oscillate between vdd and zero. This is not suitable for a decoder.

HSPICE

PHASE II DYNAMIC LOGIC

.lib '/home/ff/ee141/MODELS/g25.mod' TT

.inc 'gate.sp'

```
*****
* Parameter
*****

.param vddp = 2.5
.param multi_nand1 = 4.09
.param multi_inv2 = 2.51
.param multi_nand3 = 10.27
.param multi_inv3 = 3.0
*****
* Sources
*****
Vdd vdd 0 'vddp'
* params = vlow vhigh delay rise fall pulse_width period
* example VIN IN GND PULSE 0 5 .5n .1n .1n .5n 2n
Vin vin1 0 pulse(0v 2.5v 0.1n 0.1n 50ps 5ns 10ns)
Vclk clk 0 pulse(0v 2.5v 0.1n 0.1n 50ps 2.5ns 5ns)
*****
* Netlist
*****
xinv1 vin1 vin2 vdd 0 INV
xnand1_b1 vdd 0 vin2 vin2 vin2 vin3 clk vin4 DNAND3 M='multi_nand1'
xnand1_b2 vdd 0 0 0 vin2 x clk xx DNAND3 M='multi_nand1'
xnand1_b3 vdd 0 0 0 vin2 y clk yy DNAND3 M='multi_nand1'
xnand1_b4 vdd 0 0 0 vin2 z clk zz DNAND3 M='multi_nand1'
xinv2 vin3 vin4 vdd 0 INV M='multi_inv2'
cw1 vin5 0 1.8641f
xnand2_b1 vdd 0 vin4 vin4 vin4 vin5 clk vout DNAND3 M='multi_nand3'
xnand2_b2 vdd 0 0 0 vin5 a clk aa DNAND3 M='multi_nand3'
xnand2_b3 vdd 0 0 0 vin5 b clk bb DNAND3 M='multi_nand3'
xnand2_b4 vdd 0 0 0 vin5 c clk cc DNAND3 M='multi_nand3'
xnand2_b5 vdd 0 0 0 vin5 d clk dd DNAND3 M='multi_nand3'
xnand2_b6 vdd 0 0 0 vin5 e clk ee DNAND3 M='multi_nand3'
xnand2_b7 vdd 0 0 0 vin5 f clk ff DNAND3 M='multi_nand3'
xnand2_b8 vdd 0 0 0 vin5 g clk gg DNAND3 M='multi_nand3'
xinv3 vin5 vout vdd 0 INV M='multi_inv3'
cload vout 0 12.60438fF

* SRAM Chain
xsram0 vdd 0 vout vbit0 vbitbar0 Sram
xsram1 vdd 0 vout vbit1 vbitbar1 Sram
xsram2 vdd 0 vout vbit2 vbitbar2 Sram
xsram3 vdd 0 vout vbit3 vbitbar3 Sram
xsram4 vdd 0 vout vbit4 vbitbar4 Sram
xsram5 vdd 0 vout vbit5 vbitbar5 Sram
xsram6 vdd 0 vout vbit6 vbitbar6 Sram
```

```

xsram7 vdd 0 vout vbit7 vbitbar7 Sram
xsram8 vdd 0 vout vbit8 vbitbar8 Sram
xsram9 vdd 0 vout vbit9 vbitbar9 Sram
xsram10 vdd 0 vout vbit10 vbitbar10 Sram
xsram11 vdd 0 vout vbit11 vbitbar11 Sram
xsram12 vdd 0 vout vbit12 vbitbar12 Sram
xsram13 vdd 0 vout vbit13 vbitbar13 Sram
xsram14 vdd 0 vout vbit14 vbitbar14 Sram
xsram15 vdd 0 vout vbit15 vbitbar15 Sram
xsram16 vdd 0 vout vbit16 vbitbar16 Sram
xsram17 vdd 0 vout vbit17 vbitbar17 Sram
xsram18 vdd 0 vout vbit18 vbitbar18 Sram
xsram19 vdd 0 vout vbit19 vbitbar19 Sram
xsram20 vdd 0 vout vbit20 vbitbar20 Sram
xsram21 vdd 0 vout vbit21 vbitbar21 Sram
xsram22 vdd 0 vout vbit22 vbitbar22 Sram
xsram23 vdd 0 vout vbit23 vbitbar23 Sram
xsram24 vdd 0 vout vbit24 vbitbar24 Sram
xsram25 vdd 0 vout vbit25 vbitbar25 Sram
xsram26 vdd 0 vout vbit26 vbitbar26 Sram
xsram27 vdd 0 vout vbit27 vbitbar27 Sram
xsram28 vdd 0 vout vbit28 vbitbar28 Sram
xsram29 vdd 0 vout vbit29 vbitbar29 Sram
xsram30 vdd 0 vout vbit30 vbitbar30 Sram
xsram31 vdd 0 vout vbit31 vbitbar31 Sram
cout vout 0 13f

```

```
*****
```

```
* Analysis
```

```
*****
```

```
*nomod= no model info from library
```

```
.options post=2 nomod
```

```
*.op makes hspice determines DC operating point
```

```
.op
```


```
.tran 0.1ns 16ns *sweep multi _nand3
```

```
.meas tran tplh trig V(vin1) val=(2.5*.5)' rise=1 targ V(vout)
```

```
+ val=(2.5*.5)' rise=1
```

```
.end
```

Awaves

 

6-Stage Dynamic Logic

6 Stage Dynamic Logic will have the output oscillating during a read. However, for a decoder design, we need to have the output stay high for multiple cycles.

HSPICE

PHASE II DYNAMIC LOGIC

.lib '/home/ff/ee141/MODELS/g25.mod' TT

.inc 'gate.sp'

```
*****
* Parameter
*****
.param vddp = 2.5
.param multi_nand1 = 4.09
.param multi_inv2 = 2.51
.param multi_nand3 = 10.27
.param multi_inv3 = 3.0
.param multi_inv4 = 4.6
*****
* Sources
*****
Vdd vdd 0 'vddp'
* params = vlow vhigh delay rise fall pulse_width period
* example VIN IN GND PULSE 0 5 .5n .1n .1n .5n 2n
Vin vin1 0 pulse(0v 2.5v 0.1n 0.1n 50ps 5ns 10ns)
Vclk clk 0 pulse(0v 2.5v 0.1n 0.1n 50ps 2.5ns 5ns)
*****
* Netlist
*****
xinv1 vin1 vin2 vdd 0 INV
xinv2 vin2 vin3 vdd 0 INV M='multi_inv2'
xnand1_b1 vdd 0 vin3 vin3 vin4 clk vin5 DNAND3 M='multi_nand1'
xnand1_b2 vdd 0 0 0 vin3 x clk xx DNAND3 M='multi_nand1'
xnand1_b3 vdd 0 0 0 vin3 y clk yy DNAND3 M='multi_nand1'
xnand1_b4 vdd 0 0 0 vin3 z clk zz DNAND3 M='multi_nand1'
```

```

xinv3 vin4 vin5 vdd 0 INV M='multi_inv3'
cw1 vin5 0 1.8641f
xnand2_b1 vdd 0 vin5 vin5 vin5 vin6 clk vout DNAND3 M='multi_nand3'
xnand2_b2 vdd 0 0 0 vin5 a clk aa DNAND3 M='multi_nand3'
xnand2_b3 vdd 0 0 0 vin5 b clk bb DNAND3 M='multi_nand3'
xnand2_b4 vdd 0 0 0 vin5 c clk cc DNAND3 M='multi_nand3'
xnand2_b5 vdd 0 0 0 vin5 d clk dd DNAND3 M='multi_nand3'
xnand2_b6 vdd 0 0 0 vin5 e clk ee DNAND3 M='multi_nand3'
xnand2_b7 vdd 0 0 0 vin5 f clk ff DNAND3 M='multi_nand3'
xnand2_b8 vdd 0 0 0 vin5 g clk gg DNAND3 M='multi_nand3'
xinv4 vin6 vout vdd 0 INV M='multi_inv4'
cload vout 0 12.60438fF

```

* SRAM Chain

```

xsram0 vdd 0 vout vbit0 vbitbar0 Sram
xsram1 vdd 0 vout vbit1 vbitbar1 Sram
xsram2 vdd 0 vout vbit2 vbitbar2 Sram
xsram3 vdd 0 vout vbit3 vbitbar3 Sram
xsram4 vdd 0 vout vbit4 vbitbar4 Sram
xsram5 vdd 0 vout vbit5 vbitbar5 Sram
xsram6 vdd 0 vout vbit6 vbitbar6 Sram
xsram7 vdd 0 vout vbit7 vbitbar7 Sram
xsram8 vdd 0 vout vbit8 vbitbar8 Sram
xsram9 vdd 0 vout vbit9 vbitbar9 Sram
xsram10 vdd 0 vout vbit10 vbitbar10 Sram
xsram11 vdd 0 vout vbit11 vbitbar11 Sram
xsram12 vdd 0 vout vbit12 vbitbar12 Sram
xsram13 vdd 0 vout vbit13 vbitbar13 Sram
xsram14 vdd 0 vout vbit14 vbitbar14 Sram
xsram15 vdd 0 vout vbit15 vbitbar15 Sram
xsram16 vdd 0 vout vbit16 vbitbar16 Sram
xsram17 vdd 0 vout vbit17 vbitbar17 Sram
xsram18 vdd 0 vout vbit18 vbitbar18 Sram
xsram19 vdd 0 vout vbit19 vbitbar19 Sram
xsram20 vdd 0 vout vbit20 vbitbar20 Sram
xsram21 vdd 0 vout vbit21 vbitbar21 Sram
xsram22 vdd 0 vout vbit22 vbitbar22 Sram
xsram23 vdd 0 vout vbit23 vbitbar23 Sram
xsram24 vdd 0 vout vbit24 vbitbar24 Sram
xsram25 vdd 0 vout vbit25 vbitbar25 Sram
xsram26 vdd 0 vout vbit26 vbitbar26 Sram
xsram27 vdd 0 vout vbit27 vbitbar27 Sram
xsram28 vdd 0 vout vbit28 vbitbar28 Sram
xsram29 vdd 0 vout vbit29 vbitbar29 Sram
xsram30 vdd 0 vout vbit30 vbitbar30 Sram
xsram31 vdd 0 vout vbit31 vbitbar31 Sram
cout vout 0 13f

```

* Analysis

*nomod= no model info from library

.options post=2 nomod


*.op makes hspice determines DC operating point

.op

```
.tran 0.1ns 16ns *sweep multi_nand3
.meas tran tplt trig V(vin1) val=(2.5*.5)' rise=1 targ V(vout)
+ val=(2.5*.5)' rise=1
.end
```

Awaves

 6-Stage not-not-nand-not circuit Transcient Plot



Conclusion. Dynamic is not suitable for the decoder we need.