

# Cadence Layout for SRAM Phase I

Bill Hung, Dennis Wang

## Table of Contents



Cadence Layout for SRAM Phase I .....	1
Opening a New Layout and New Library .....	2
SRAM Cell Transistors Layout.....	5
Drawing NMOS .....	5
Exploring Cadence Transistor Sizes .....	7
NMOS .....	7
PMOS .....	9
Testing NMOS and PMOS Extraction.....	11
NMOS .....	11
PMOS .....	12
Half SRAM Cell Transistors Layout.....	13
Wiring within the SRAM Cell with Contacts .....	17
Contacts.....	18
Wiring word line .....	19
Wiring $\bar{BL}$ , $BL$ , $\bar{Q}$ , $Q$ and $V_{dd}$ .....	20
Instantiate N-tap .....	21
Minimizing Wires .....	21
Connecting the Grounds.....	22
Connecting the VDD .....	24
Final Layout .....	25
Testing with Repetitive Pattern .....	26
APPENDIX.....	27
Cadence Shortcut Keys .....	27
Failure Notes, mistakes that I learned from trial and error .....	27
HSPICE Minimum NMOS Extracted Netlist .....	28
HSPICE Minimum PMOS Extracted Netlist .....	29
HSPICE Q-bar between M1 NMOS drain and M2 PMOS drain.....	30
HSPICE Wiring $\bar{BL}$ , $BL$ , $\bar{Q}$ , $Q$ and $V_{dd}$ .....	31
HSPICE After Ground Metal 2 Rail .....	32
HSPICE After Ground Metal 3 Connection.....	33
Final HSPICE SRAM Cell Extracted .....	34

## List of Tables

Table 1 PMOS Dimensions in Library NCSU_TechLib_tsmc03d Layout.....	5
Table 2 Minimum PMOS and NMOS Sizes from Library NCSU_TechLib_tsmc03d .....	5
Table 3 Actual NMOS Size for Phrase I.....	7
Table 4 Actual PMOS Size for Phrase I.....	9
Table 5 Cadence Shortcut Keys .....	27

## Opening a New Layout and New Library

File->New->Library

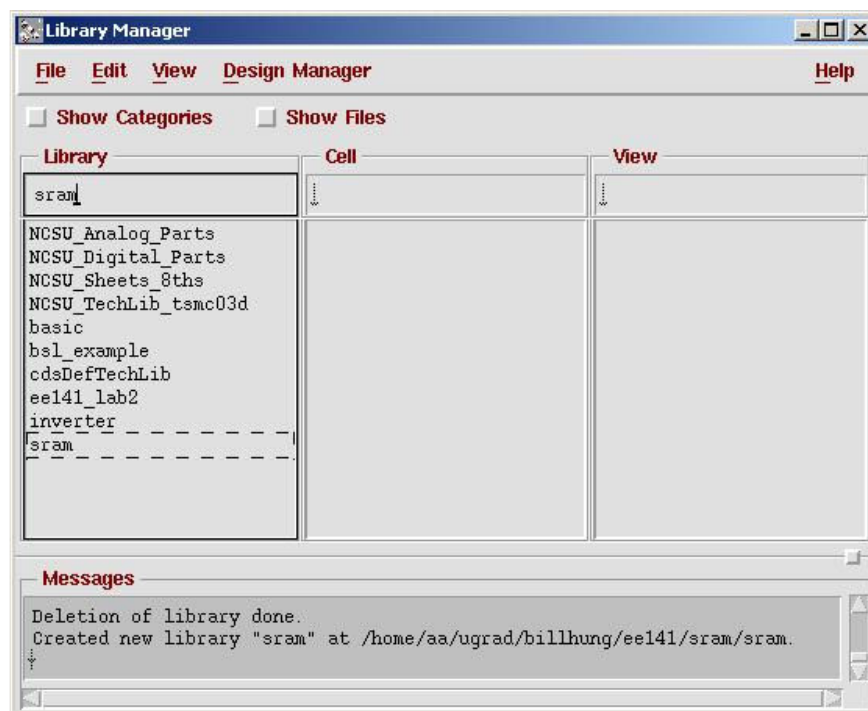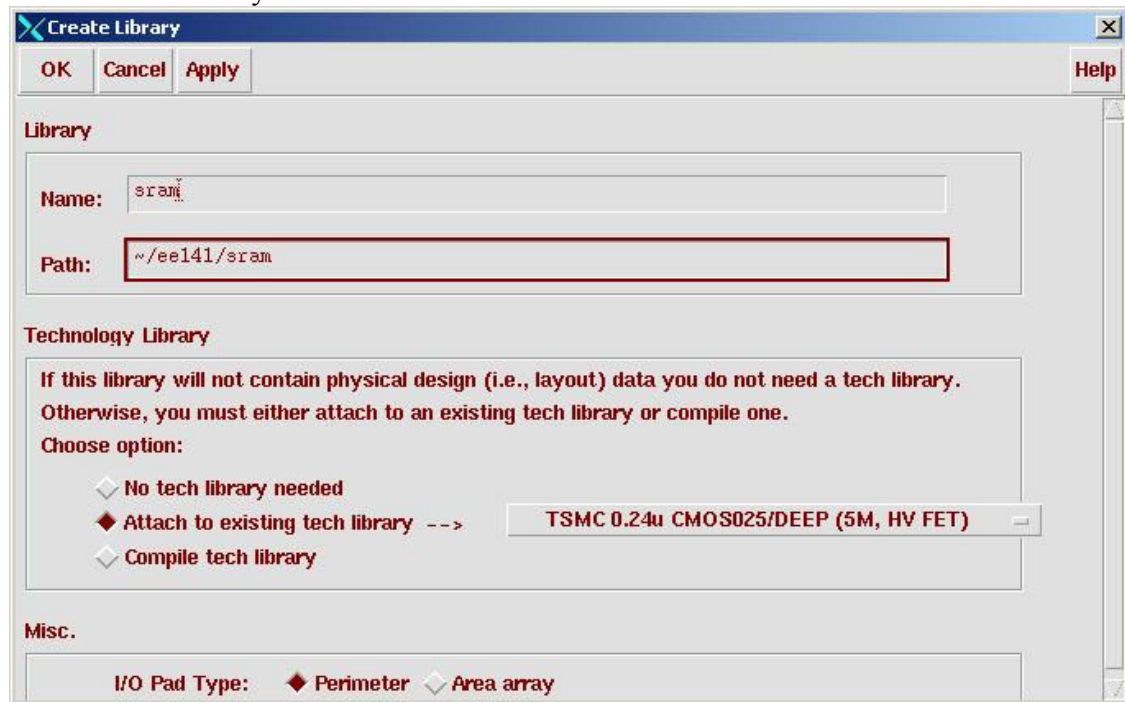

Put "sram" in Library field in Library Manager and press Enter.





Make the folder and proceed.



OK




OK

 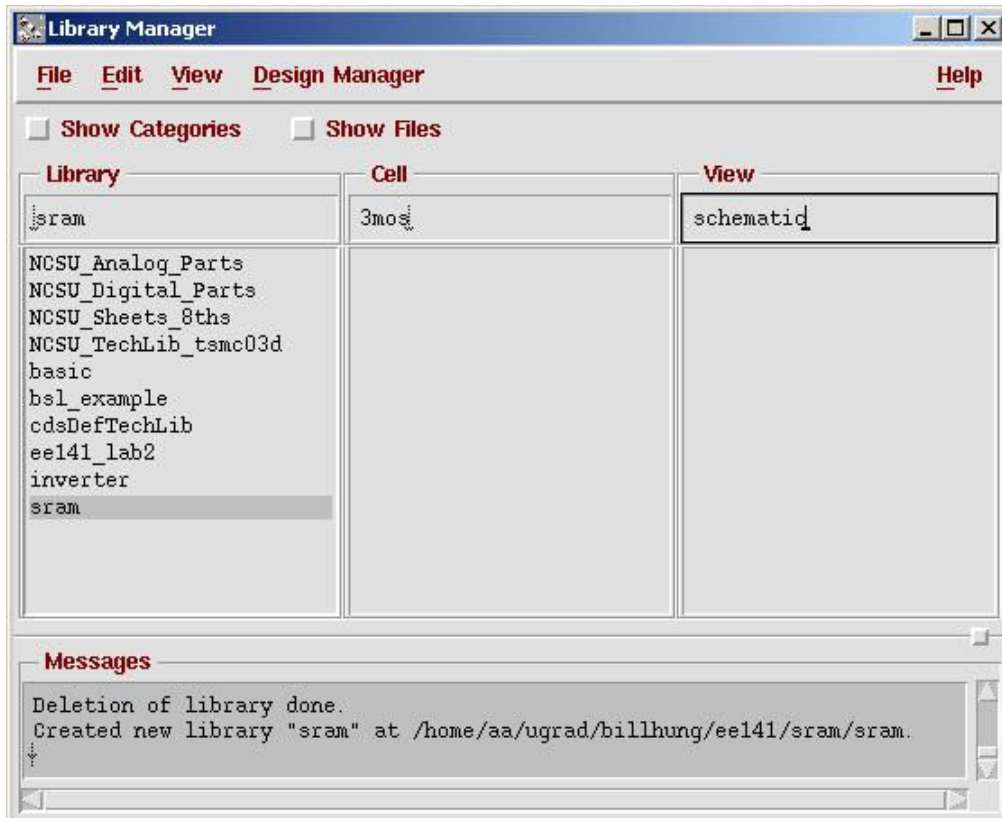

OK
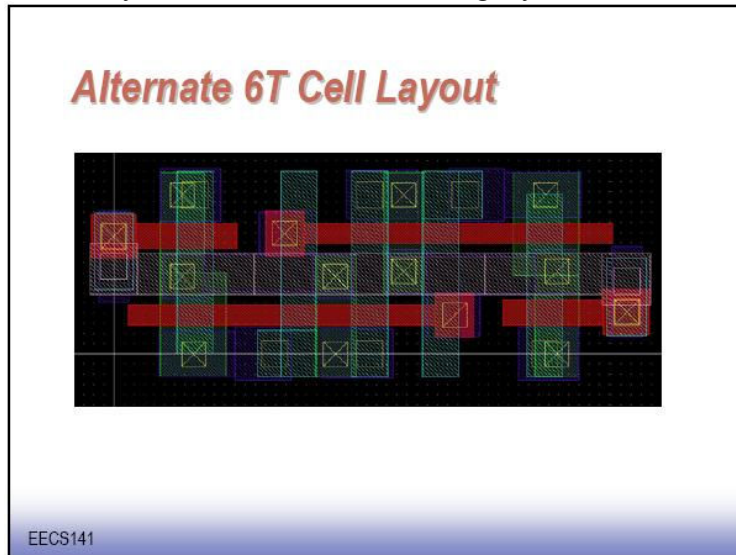
## SRAM Cell Transistors Layout

Ultimately, want to draw the following layout.



## Drawing NMOS


For now. Open NCSU\_TechLib\_tsmc03d->nmos->layout, and try to draw an NMOS myself.

**Table 1 PMOS Dimensions in Library NCSU\_TechLib\_tsmc03d Layout**

Name	Height x Width
Contact (cc)	24 x 24
Poly (poly)	1.6 x 1.0
Drain Metal (metal1)	1.0 x 0.48
Well (nactive)	1.0 x 2.2
Circumference (nselect)	1.6 x 2.68


**Table 2 Minimum PMOS and NMOS Sizes from Library NCSU\_TechLib\_tsmc03d**

Name	Width / Length
NMOS	0.36um / 0.24um
PMOS	0.36um / 0.24um

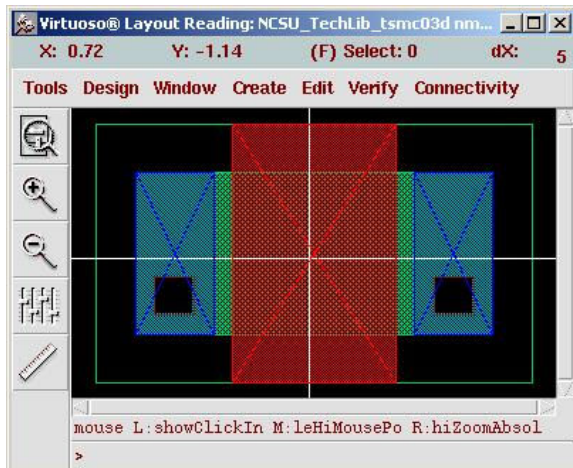


The layout by opening the NCSU\_TechLib\_tsmc03d library.

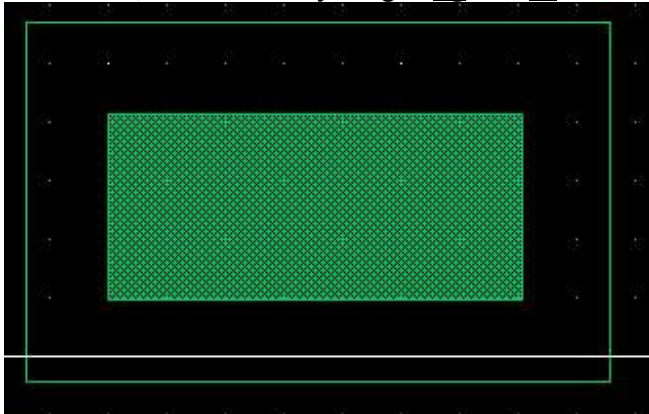“r” nselect, nactive. Everything is **dg**, not **nt** in the LSW window.




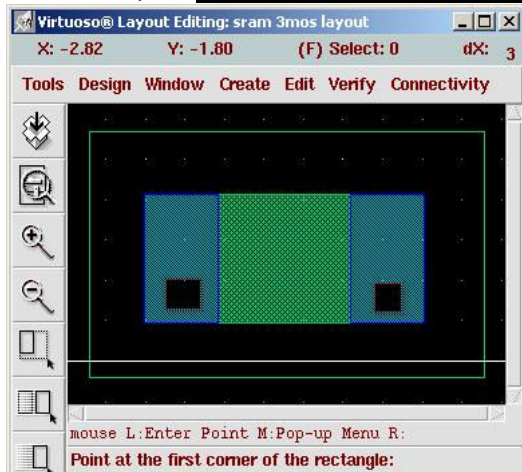“r” metall, cc. **Notice the contacts have to be exactly 0.24um x 0.24um or DRC error.**



“r” poly



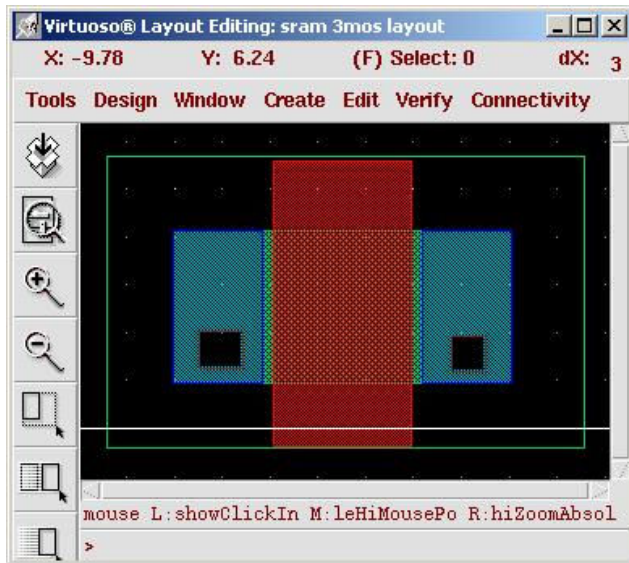


“q”, then change the left, right, bottom, top to change the size.

## Exploring Cadence Transistor Sizes


### NMOS

Table 3 Actual NMOS Size for Phrase I


Name	Width x Height
nselect (same as library)	1.92 x 1.08
nactive (Well)	1.44 x 0.48
metal1 (Drain metal)	0.48 x 0.48
poly	0.24 x 0.96
cc (contacts)	0.24 x 0.24

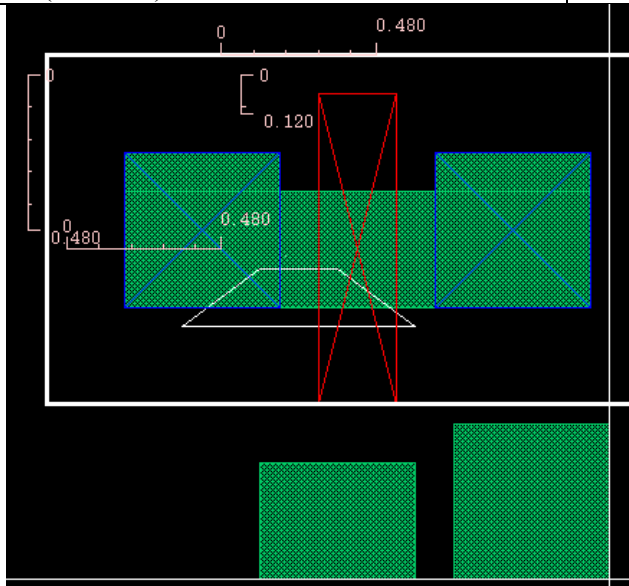


nactive below, library nmos above.

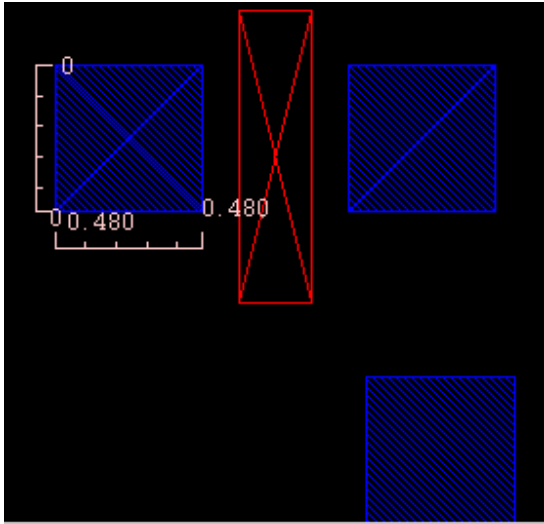

Metal1

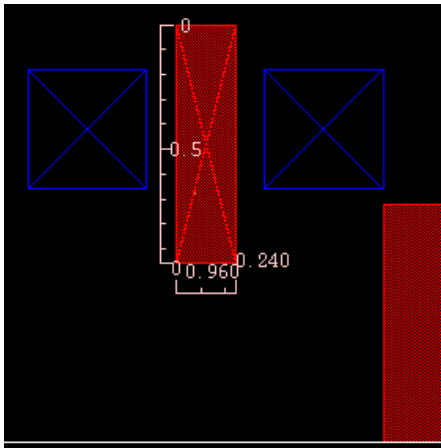


Poly

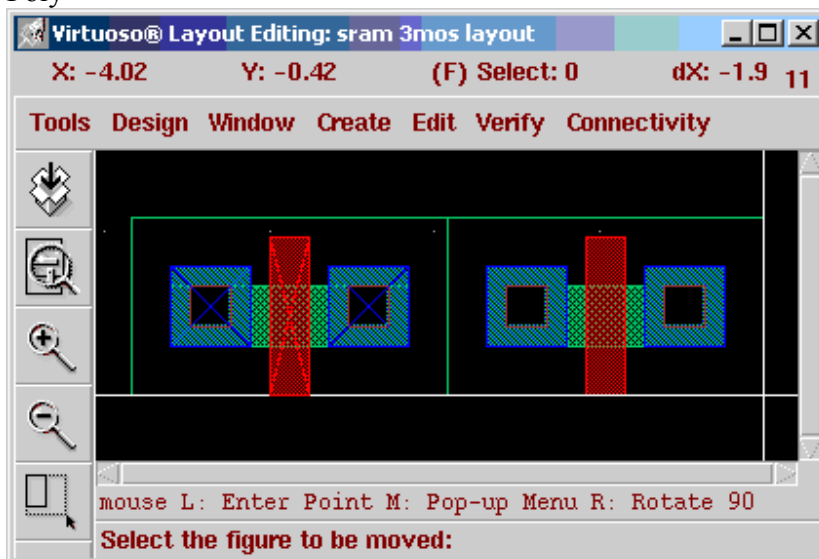

Nmos from library (left), and my nmos (right). They are exactly the same. DRC error free, extract error free.




## PMOS

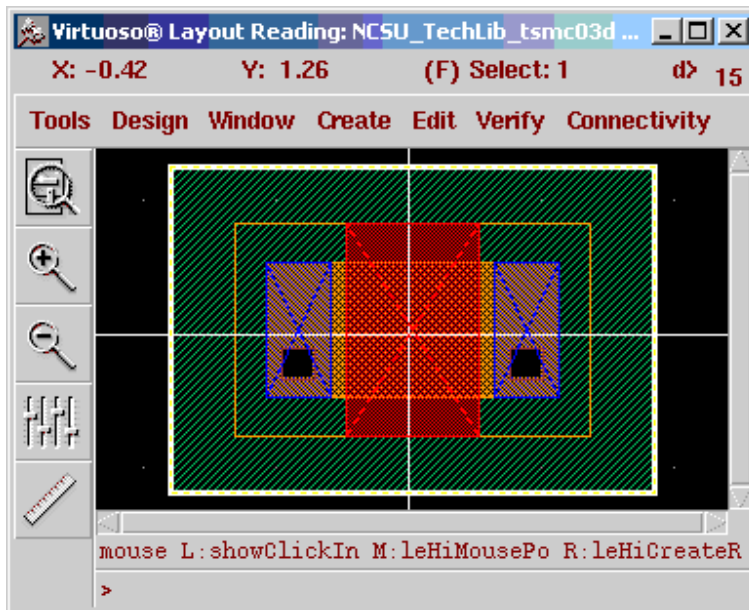


The library cell by opening the NCSU\_TechLib\_tsmc03d library

**Table 4 Actual PMOS Size for Phrase I**


Name	Width x Height
Nwell	2.880 x 1.920
pselect (orange box)	1.920 x 1.080
Pactive	1.44 x 0.48
metal1	0.48 x 0.48
cc (contacts)	0.24 x 0.24
Poly	0.24 x 0.96

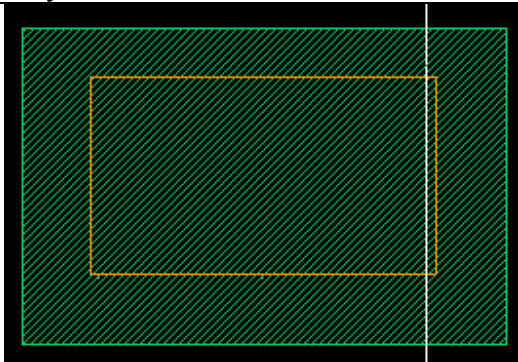


nwell and pselect (orange box)

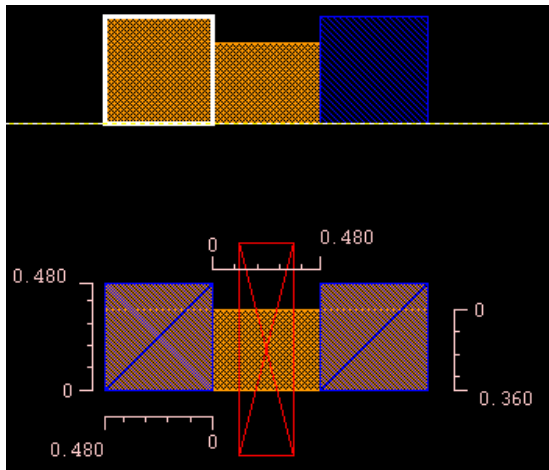

pactive, metall

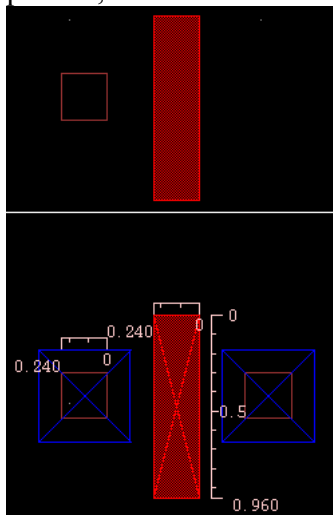

cc (contacts), poly

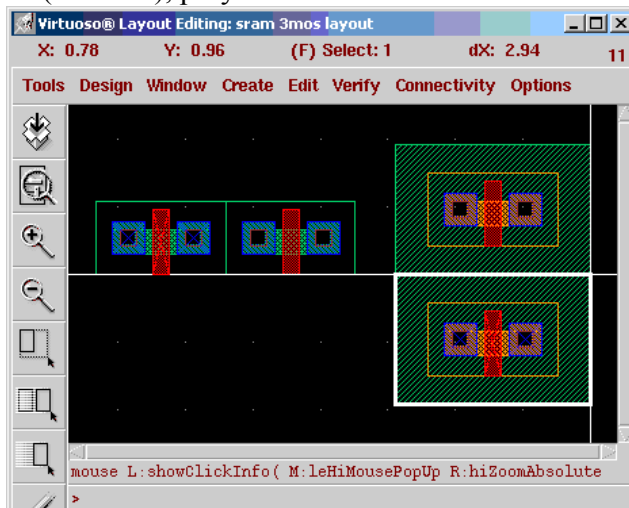


DRC-> Total errors found: 0

Extract -> Total errors found: 0

## Testing NMOS and PMOS Extraction


### NMOS

Verify->Extract

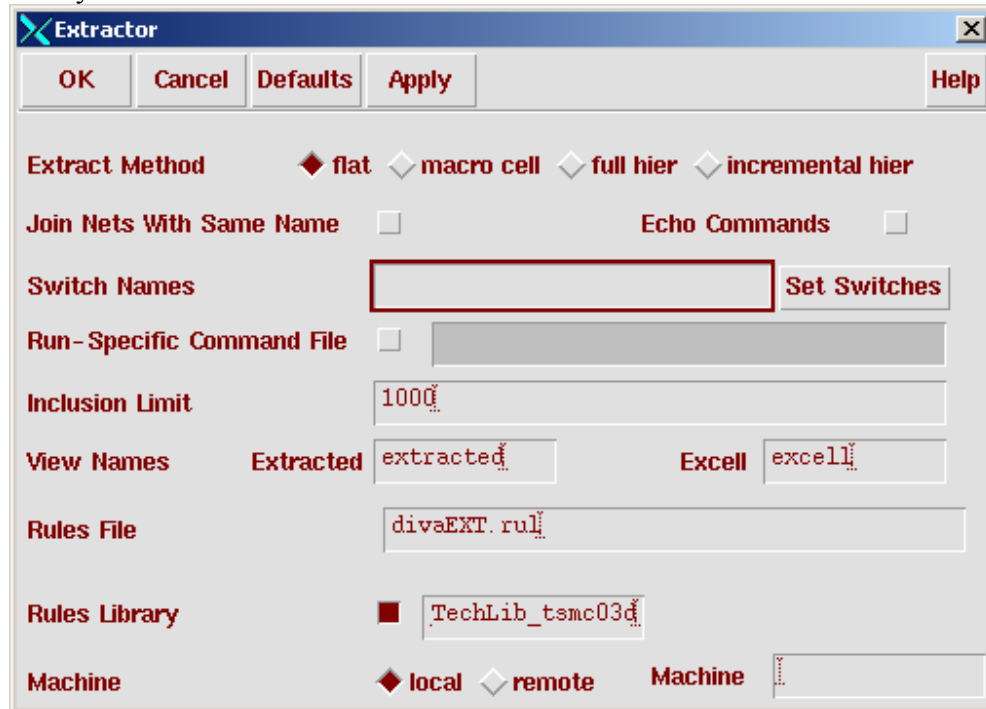

Total errors found: 0

Open to the 3mos->extract

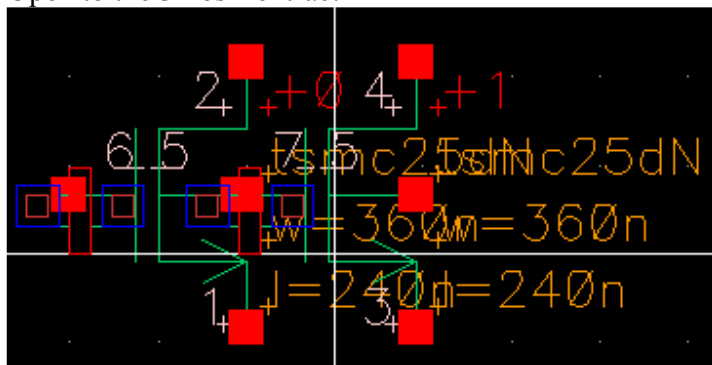

Tools->Analog Environment->Setup Environment

Check "hspice" and "flat", OK


Simulation->Netlist->Create Final

Save As -> ~/141/phrase1/min\_nmos.sp

The extracted width and length agree with the layout (360nm x 240nm). The extracted hspice netlist is attached at the end.

## PMOS

Open to the 3mos->extract

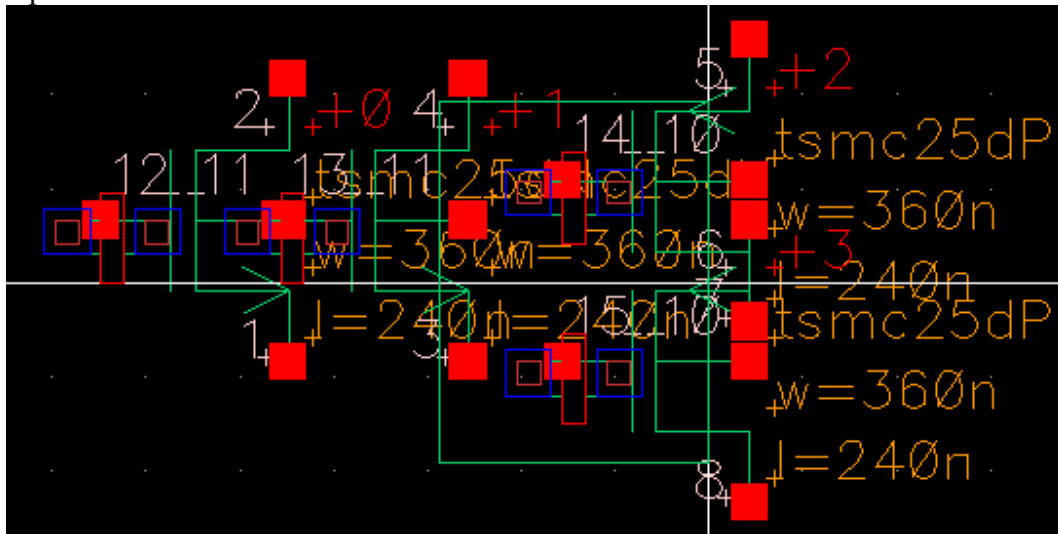

Tools->Analog Environment->Setup Environment

Check "hspice" and "flat", OK



Simulation->Netlist->Create Final

Save As -> ~/141/phrase1/min\_pmos.sp


The extracted width and length agree with the layout (360nm x 240nm). The extracted hspice netlist is attached at the end.

**Half SRAM Cell Transistors Layout****65nm SRAM**

□ ST/Philips/Motorola

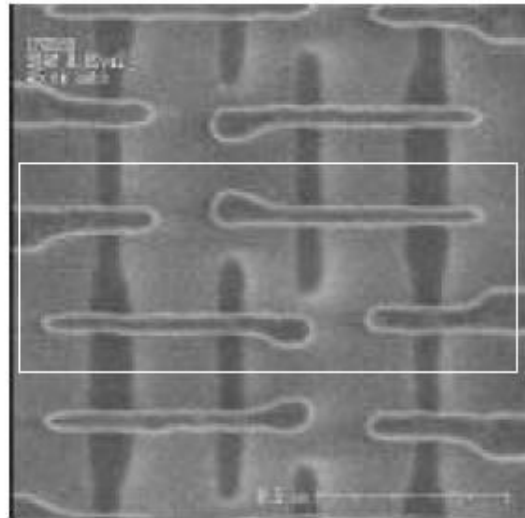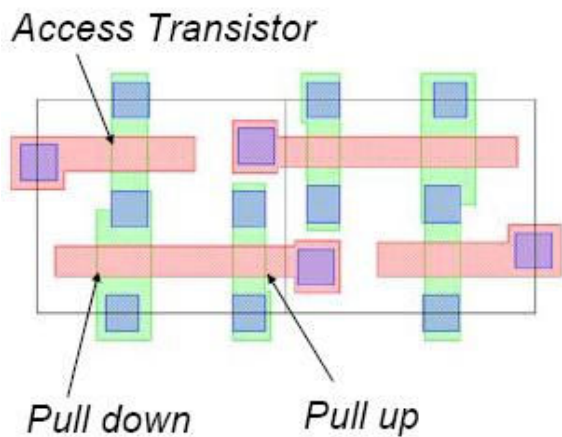

This is the goal of the layout [Nikolic, lec 17 page 7]

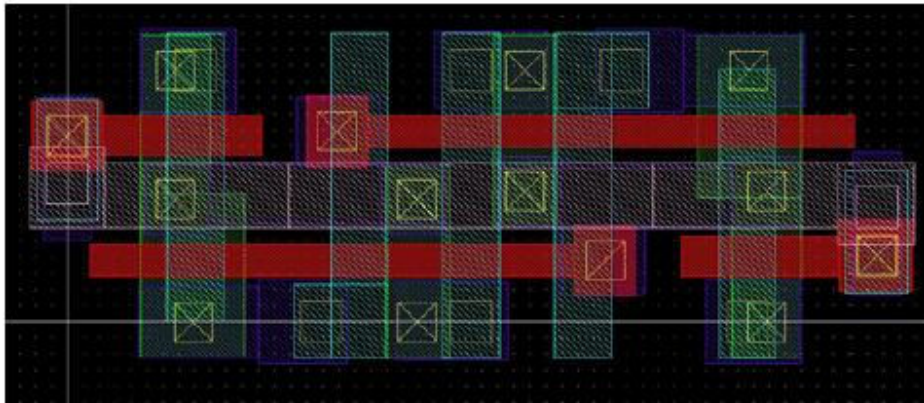**Alternate 6T Cell Layout**

Layout Example Posted by TA [EE 141, Spring 2006]

## Stick Diagram of the SRAM Cell Layout



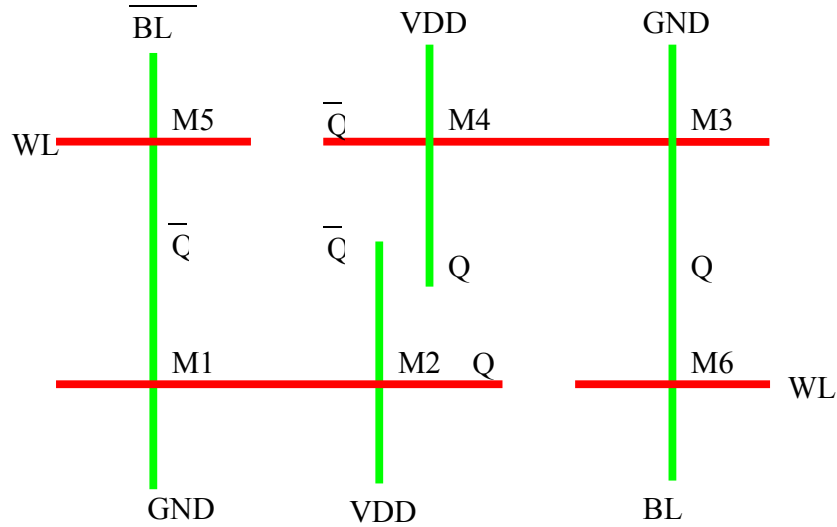


Figure 1SRAM Cell Layout Stick Diagram

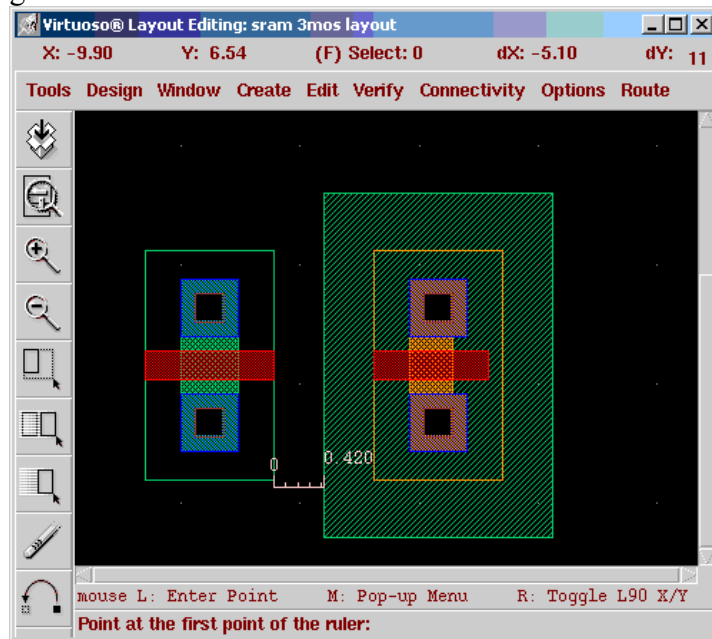
Edit->Other->Rotate to rotate the transistors. cp and align them to meet the schematic given for 65nm SRAM



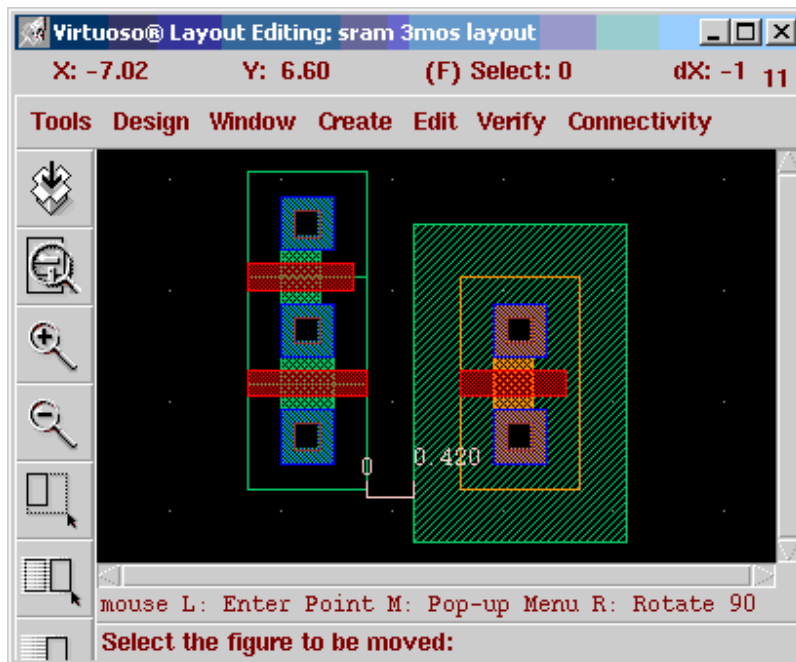Min distance (3.5 lambda) between nmos and pmos with DRC error.




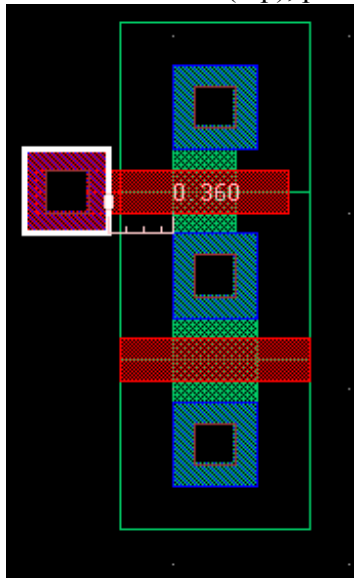Access transistor (top), pull down nmos (left bottom), and pull up pmos (right)




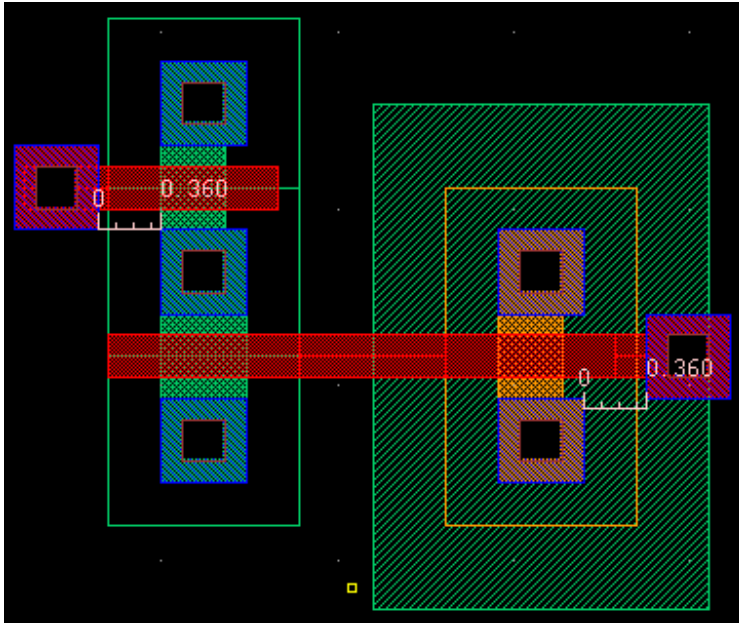M1\_POLY to metal1 min distance (3 lambda)






M1\_POLY contact and poly added to pmos

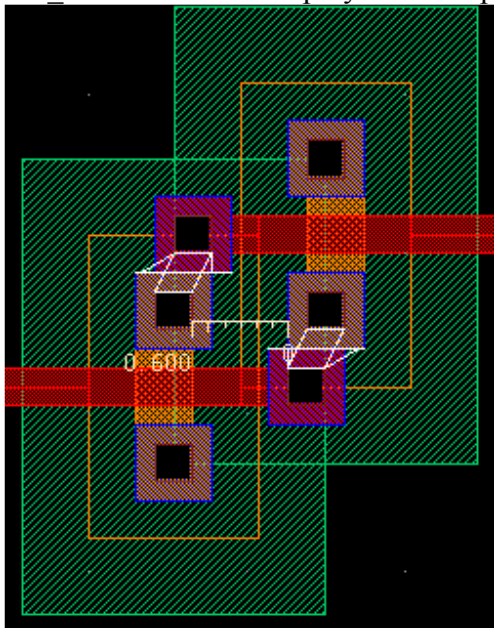


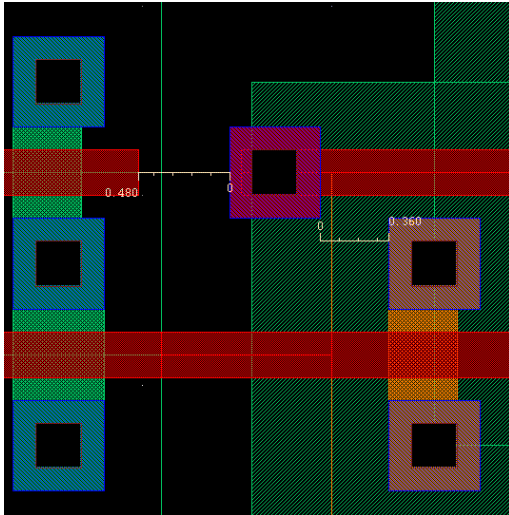Active contact to active spacing (5 lambda)




Poly to poly contact (4 lambda), active contact to active spacing (3 lambda), so this makes the 2 pmos has 6 lambda apart instead of 5 lambda apart.
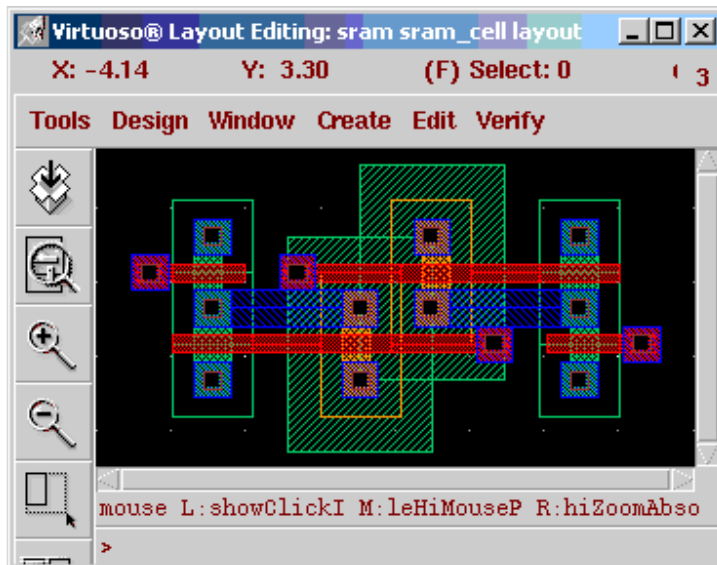
### Wiring within the SRAM Cell with Contacts




$\bar{Q}$  are connected with metal 1 between M1 NMOS drain and M2 PMOS drain. DRC error free, extract was error free. The Hspice attached in appendix. The problem here is the metal 1 between M1 and M2 using metal 1 will connect the gate of pmos M4 also, which is not correct.


## Contacts

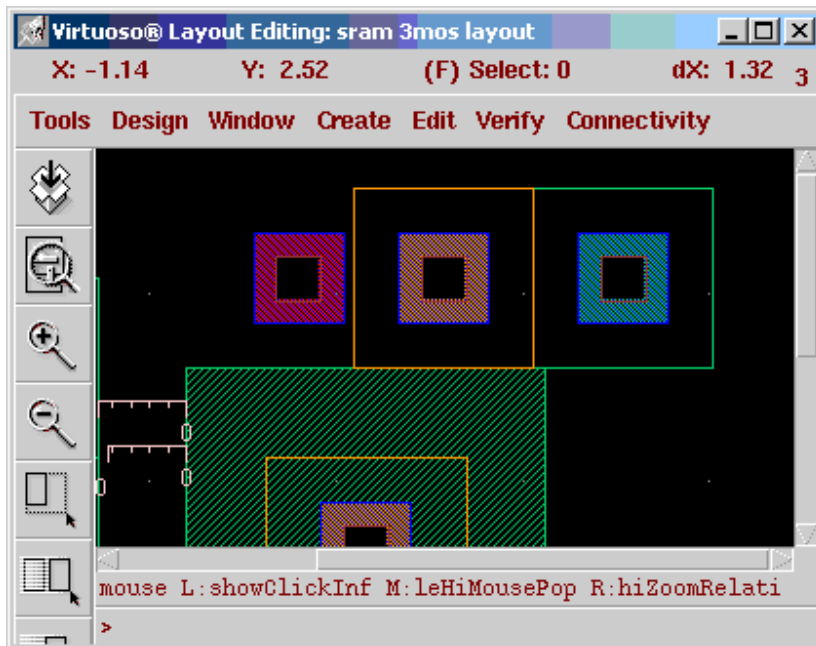

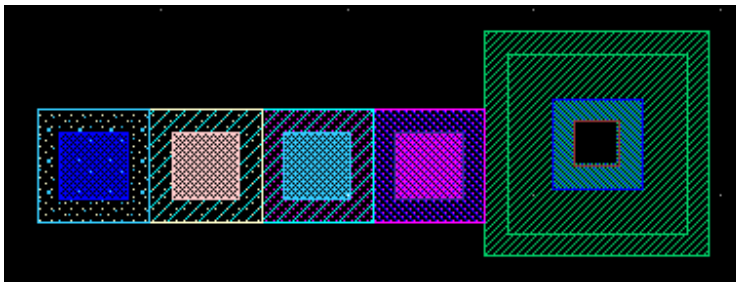Contacts M1\_POLY(left), M1\_P(middle), M1\_N (right)




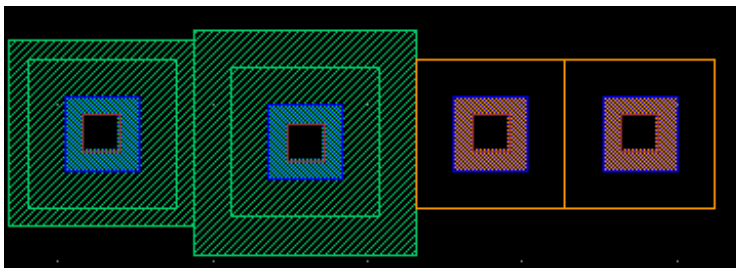(from left) Contact M5\_M4, M4\_M3, M3\_M2, M2\_M1, NTAP




(from left) NTAP = nwell/nselect/cc/ml or nwell/ml\_n, ntap, M1\_P, PTAP

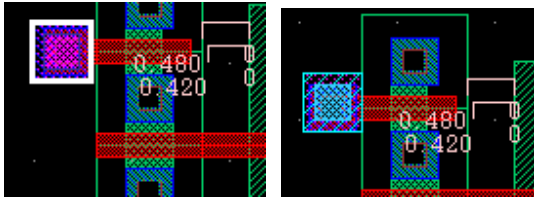Now I try to make contacts on the gate of M5



M2\_M1 contact (left), M3\_M2 contact (right) placed at the same place, onto of gate of M5 for Word Line (WL) connections.

## Wiring word line

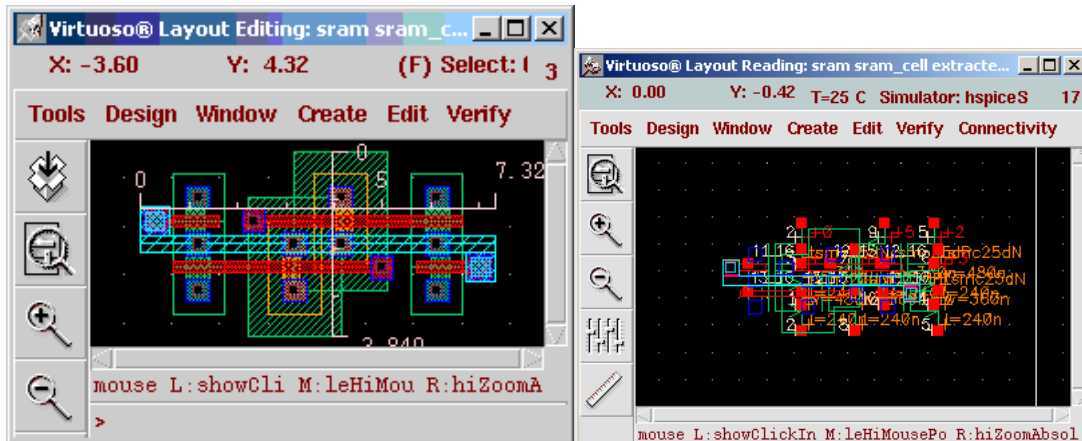


```
* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICES/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 17 23:45:35 2006
```

```
M0 5 7 14 2 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M1 12 4 6 2 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M2 13 7 9 11 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6 M=1
M3 10 4 15 11 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9 M=1
M4 8 3 13 11 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9 M=1
M5 15 3 1 11 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6 M=1
```

```
* INCLUDE FILES
* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END
```


Using M3, the horizontal wire in the graph, to connect the gate of the access transistors since according to the Layout Example Posted by TA, if we use M3 for vertical wiring, we need to use a lot of contact M1\_M2 and M2\_M3.
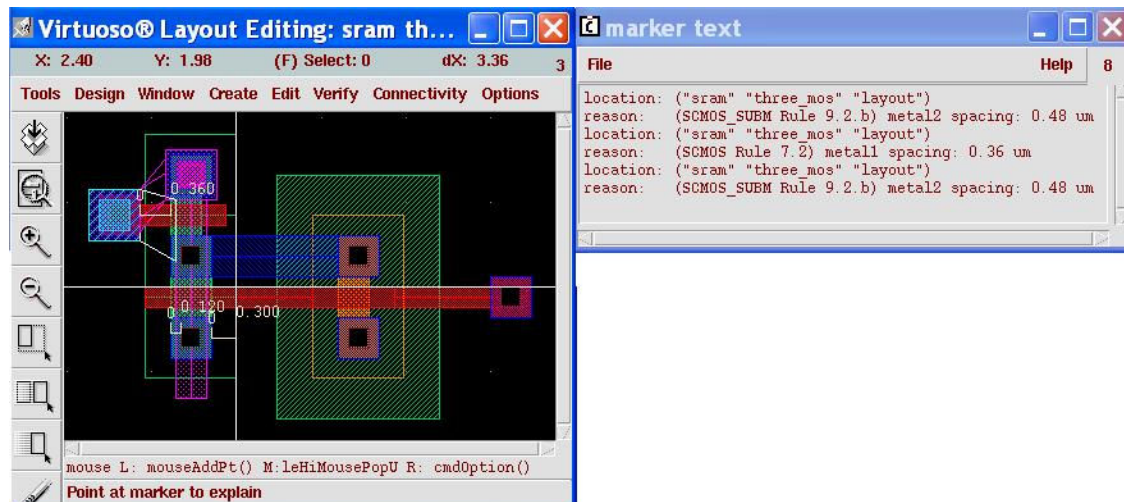
### Wiring $\bar{BL}$ , $BL$ , $\bar{Q}$ , $Q$ and $V_{dd}$



There is a problem when we use M1\_M2 as a connection to vertical  $\bar{BL}$ . The minimum spacing between M1 is 0.36um (3 lambda), and The minimum spacing between M2 is 0.48um (4 lambda).

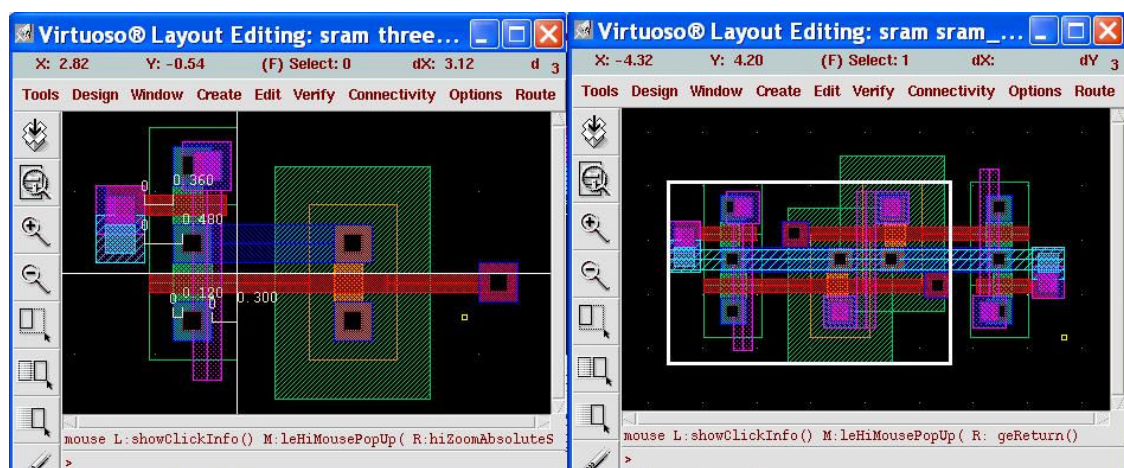
Therefore, I move M1\_M2 contact on the left (WL connection) down, and move M1\_M2 contact on the right ( $\bar{BL}$  connection) away. Now it is DRC free again. Using M2 vertically to wire  $V_{dd}$  between the 2 pmos. The result is shown below. Hspice Netlist attached at the end.





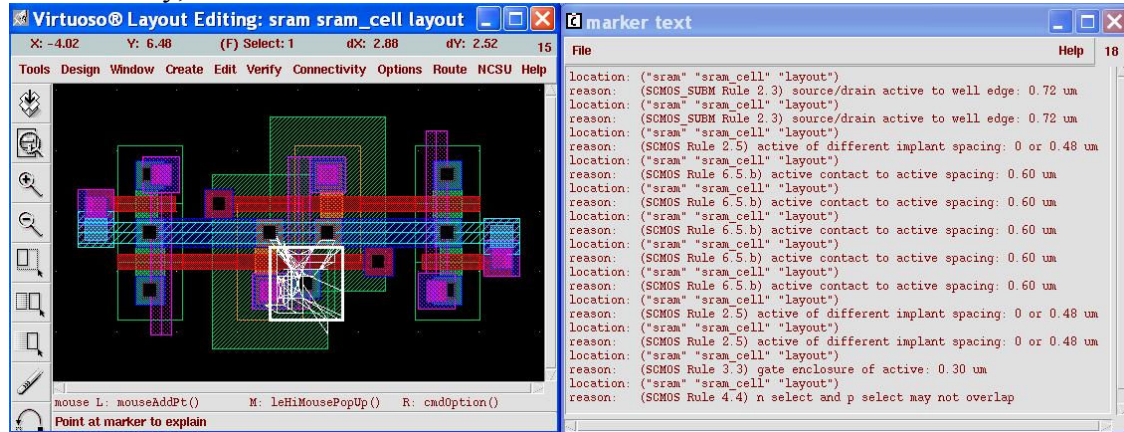
## Instantiate N-tap

First attempt: laying down the N-tap in the middle and as close as to center, but unfortunately, it didn't work



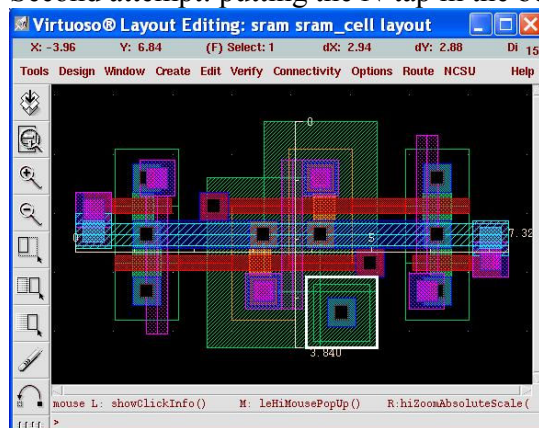Second attempt: putting the N-tap in the bottom-right corner, and it works




## Minimizing Wires




Wire minimum width 0.36um, 3 lambda

## Connecting the Grounds

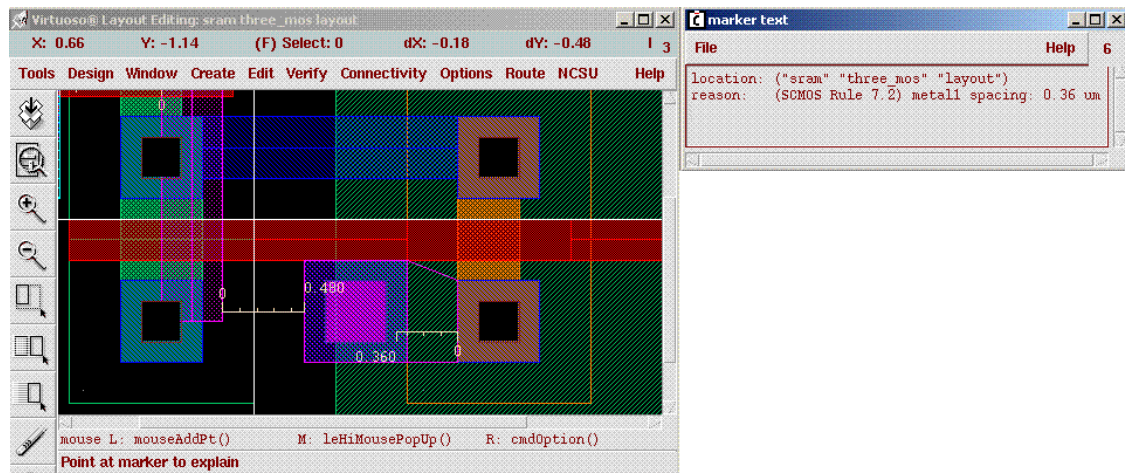


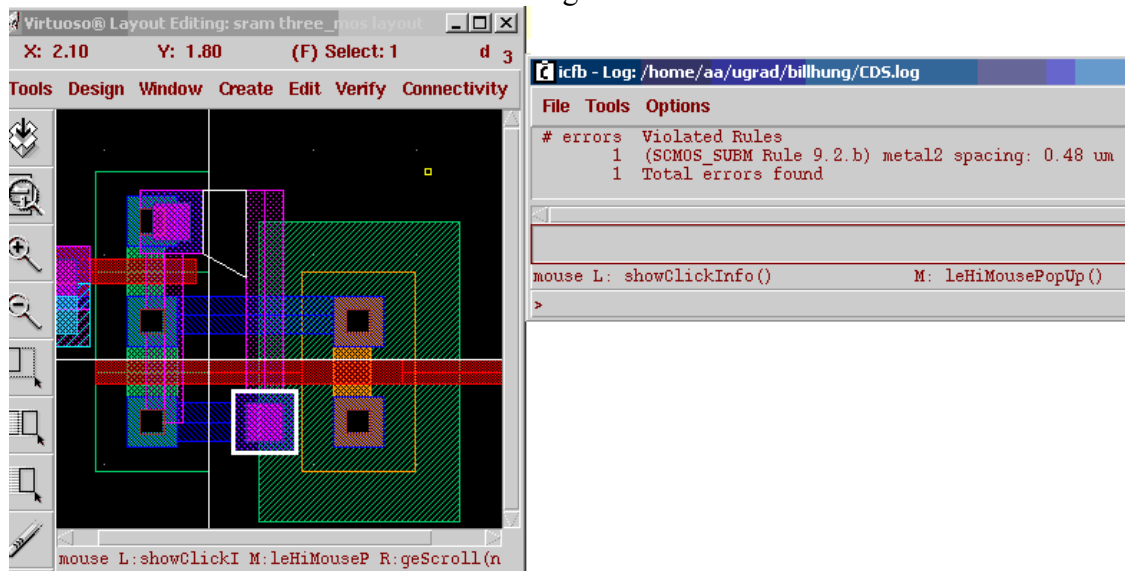The M1\_M2 contact needs 4 lambda from metal 2 and 3 lambda from metal 1. So I moved the metal 2 of the bitline-bar to the right for half a lambda. Then DRC free.




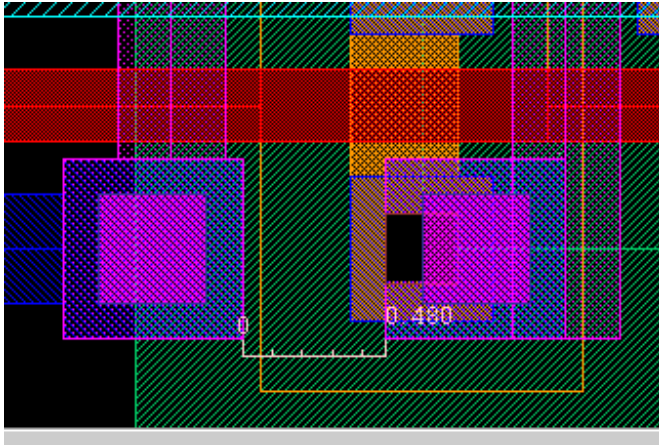The metal 1 between M1\_M2 contact and metal2 sticking up from M1\_M2 contact were drawn. The spacing between metal 2 is at least 4 lambda. So move the ground metal 2 to the right. Then DRC free.






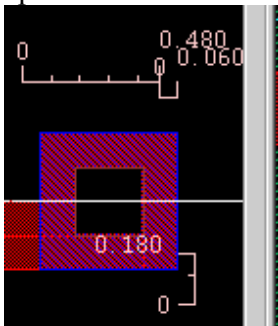Move the metal 2 contact to the right to remove metal 2 DRC error. They need 4 lambda apart.




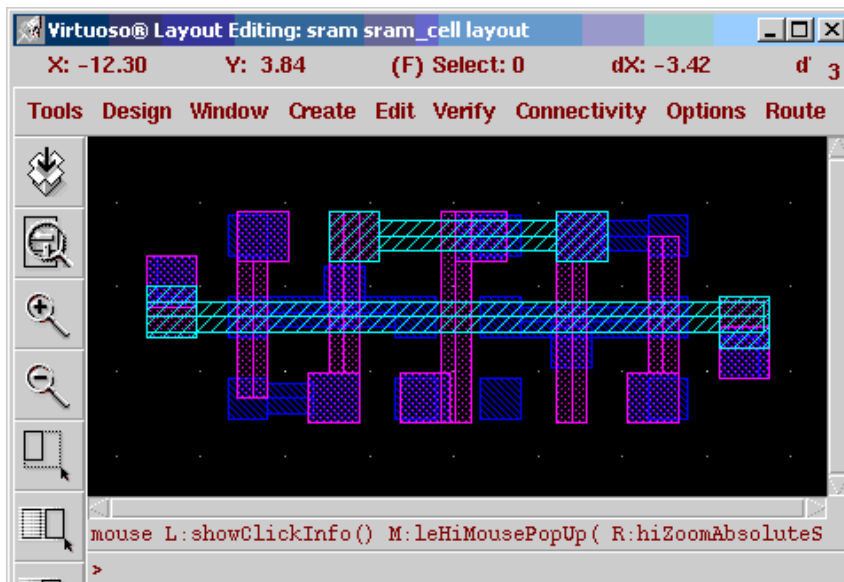After long discussion with Dennis, we decided in order to put the ntap in the cell, we have no choice but to increase the horizontal distance by half a lambda. The result is DRC free.




Connecting the grounds through metal1-metal2-metal3-metal2-metal1. DRC error free, extract error free.

### Connecting the VDD

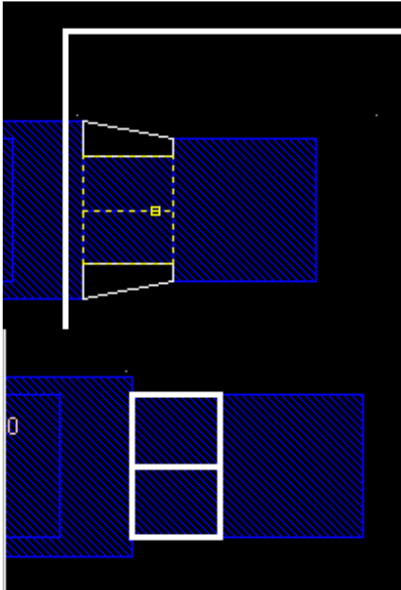


The ground is connected to the ntap through metal 1. The wire between them has to be 4 lambda instead of the minimum 3 lambda or DRC error.

## Final Layout

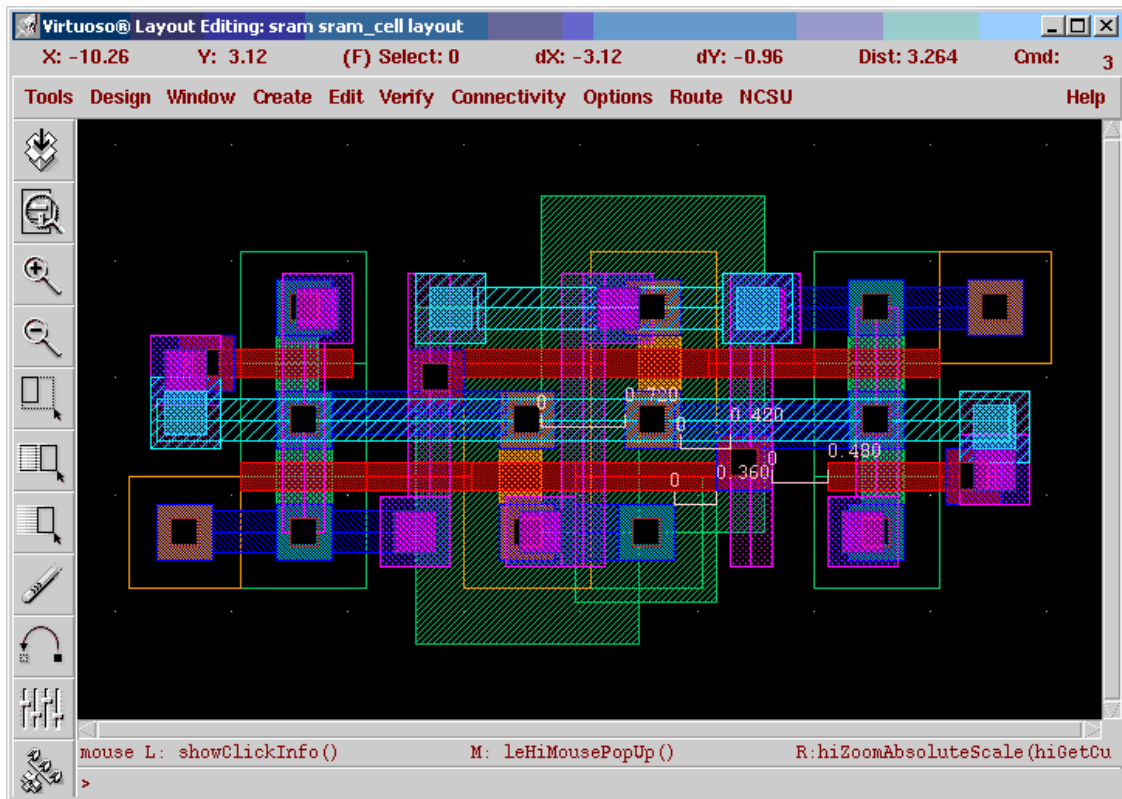


After putting the ptaps at the corners. DRC and extra error free. The hspice gives the right circuit (attached). YES!


## Final Postscript Plot

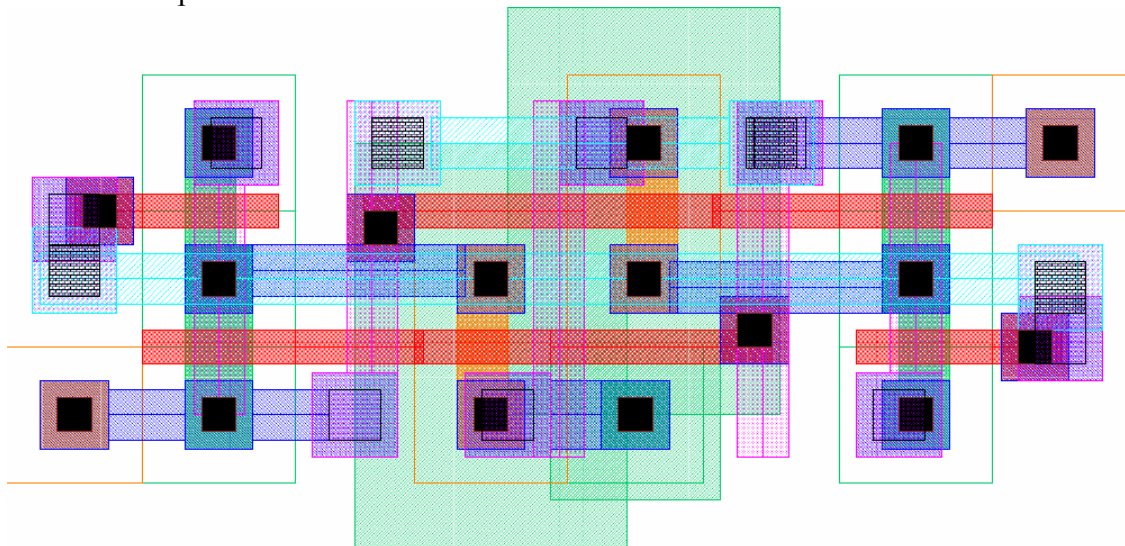

## Testing with Repetitive Pattern

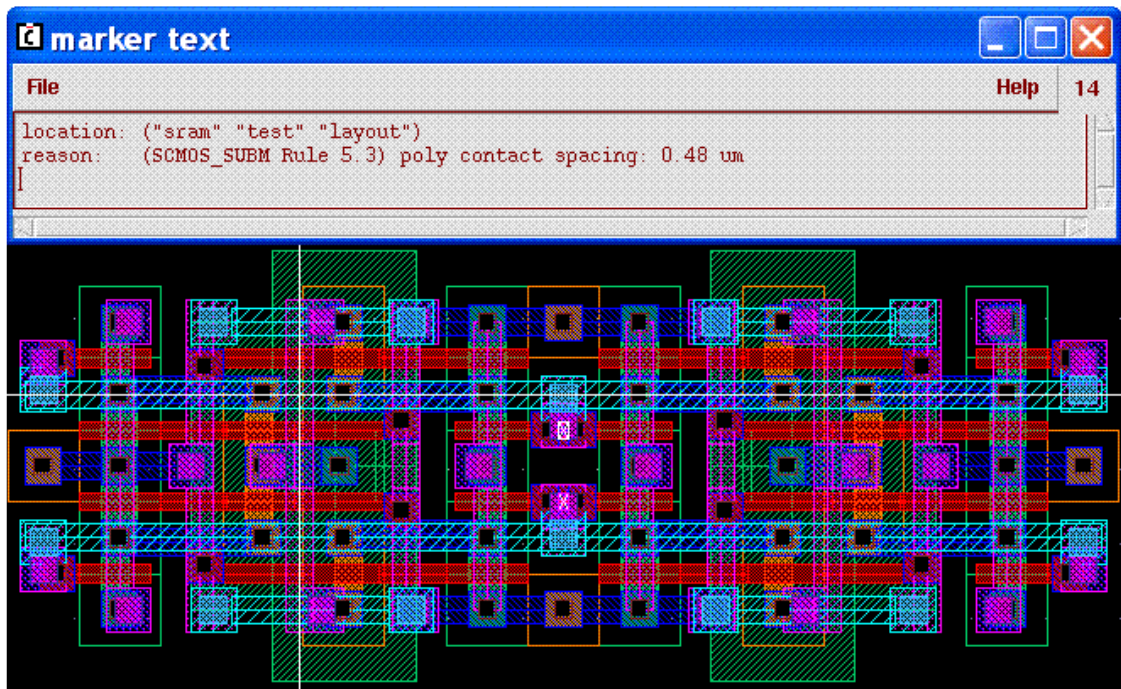

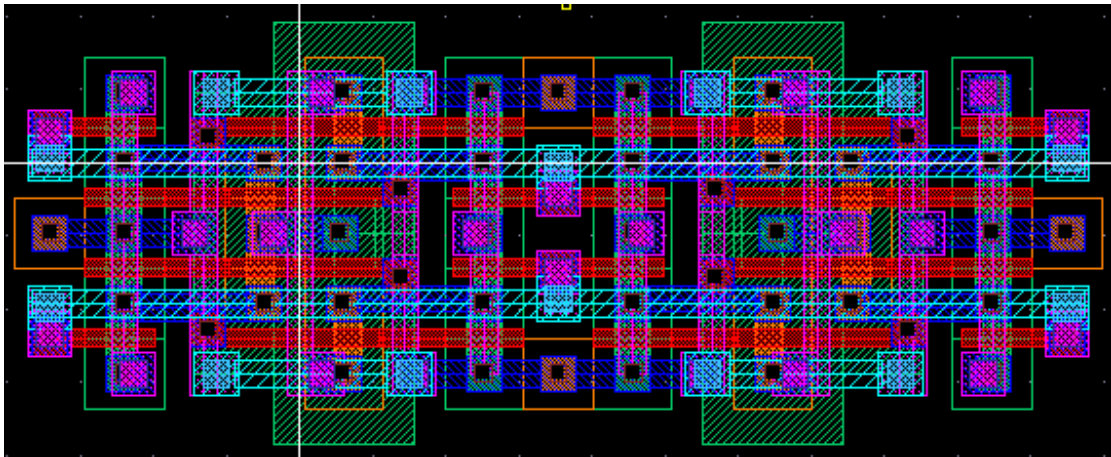The layout we have so far can not be flipped correctly since the gates of the access transistor should be center at the rotation axis.



After move the center of the poly contact, it is now DRC free

# APPENDIX


## **Cadence Shortcut Keys**

**Table 5 Cadence Shortcut Keys**

Shortcut Key	Meaning
C	Copy
M -> Flip Upside Down	Flip
O	Contact


## ***Failure Notes, mistakes that I learned from trial and error***

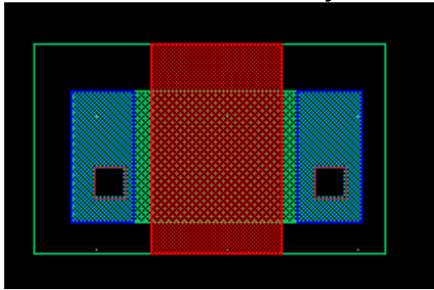1. contacts have to be exactly 0.24um x 0.24um or DRC error.



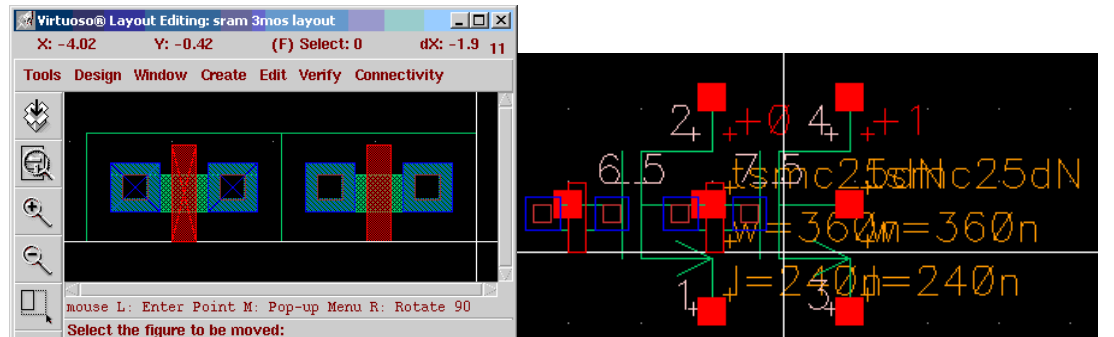2. Tried the exact dimension in Table 1, they didn't work for me. Those are the sizing parameters from the library layout. I made an nmos with the same exact dimension of the library transistor, but it ends up with lots of DRC errors. So finally opening the inverter from HW instead for sizing.



**HSPICE Minimum NMOS Extracted Netlist**


The screenshot shows the Virtuoso Layout Editor interface. On the left, a window titled 'Virtuoso® Layout Editing: 3mos 3mos layout' displays a circuit layout with various components and connections. The status bar at the bottom of this window indicates 'mouse L: Enter Point M: Pop-up Menu R: Rotate 90' and 'Select the figure to be moved:'. On the right, a large window displays the extracted HSPICE netlist for the layout.

```



* # FILE NAME: /HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/3MOS/HSPICES/
* EXTRACTED/NETLIST/3MOS.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 16 23:33:20 2006

M0 5 3 6 2 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M1 7 4 1 2 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1

* INCLUDE FILES

* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END

```

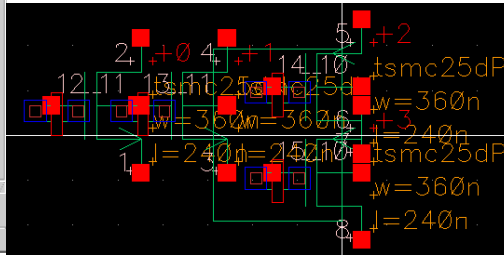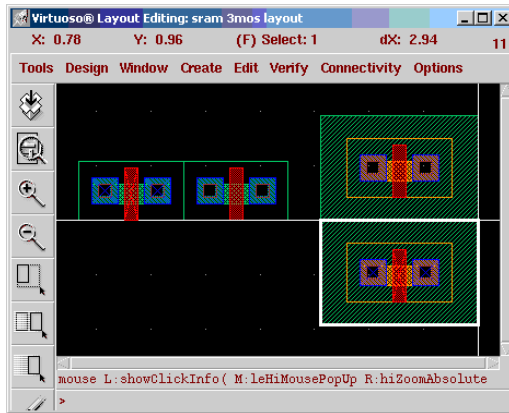**HSPICE Minimum PMOS Extracted Netlist**


```
* # FILE NAME: /HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/3MOS/HSPICES/
* EXTRACTED/NETLIST/3MOS.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 17 00:39:30 2006
```

```
M0 11 2 8 5 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M1 6 13 12 5 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M2 9 4 10 3 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M3 14 7 1 3 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
```

```
* INCLUDE FILES
```
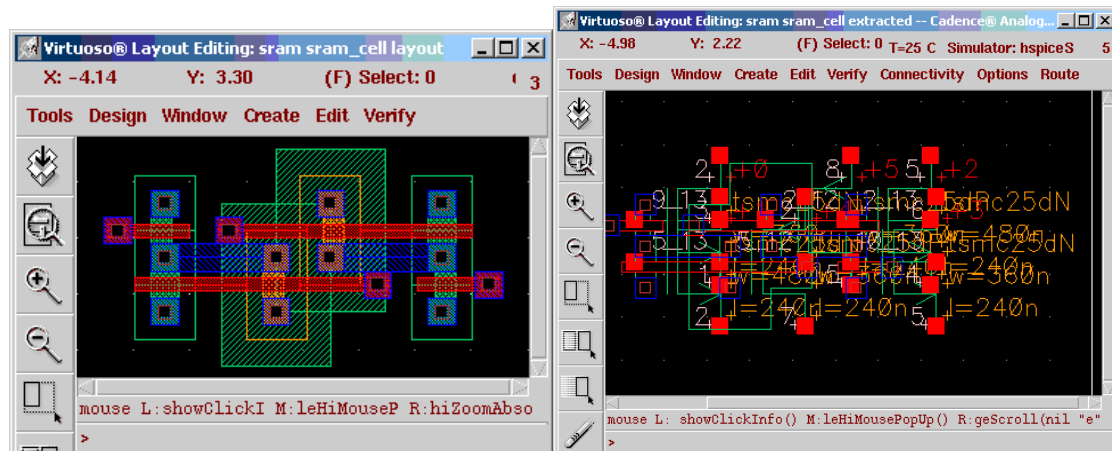
```
* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END
```



**HSPICE Q-bar between M1 NMOS drain and M2 PMOS drain**

```
* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICES/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 17 20:38:00 2006
```

```
M0 10 12 9 5 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M1 4 10 12 5 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M2 10 12 7 2 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6 M=1
M3 8 10 12 2 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9 M=1
M4 6 3 10 2 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9 M=1
M5 12 11 1 2 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6 M=1
```

```
* INCLUDE FILES
```

```
* END OF NETLIST
```

```
.TEMP 25.0000
```

```
.OP
```

```
.save
```

```
.OPTION INGOLD=2 ARTIST=2 PSF=2
```

```
+ PROBE=0
```

```
.END
```

The node 12 is Q-bar. I noticed the pmos M1 in the netlist and the two big nmos (M2 and M3 in the netlist) are connected. This is good.

The netlist suggests that with a metal 1 connecting M1 and M2 in the stick diagram (Figure 1) will connect the gate of M4. This is what we want

**HSPICE Wiring  $\bar{BL}, BL, \bar{Q}, Q$  and  $V_{dd}$** 


In the netlist extraction (we can't tell if BL will be properly connected at this stage, but we are sure that the two half cells are connected together; Qbar corresponding to node 9 whereas Q corresponding to node 10.  $V_{dd}$  is node 4)

```
* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICE
S/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 18 12:19:53 2006

M0 9 10 4 3 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M1 4 9 10 3 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M2 9 10 6 2 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6
M=1
M3 7 9 10 2 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9
M=1
M4 5 8 9 2 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9
M=1
M5 10 8 1 2 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6
M=1

* INCLUDE FILES

* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END
```

 
**HSPICE After Ground Metal 2 Rail**

```
* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICES/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 18 17:54:03 2006
```

```
M0 9 10 4 3 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M1 4 9 10 3 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6 M=1
M2 9 10 6 2 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6 M=1
M3 7 9 10 2 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9 M=1
M4 5 8 9 2 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9 M=1
M5 10 8 1 2 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6 M=1
```

```
* INCLUDE FILES
```

```
* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END
```

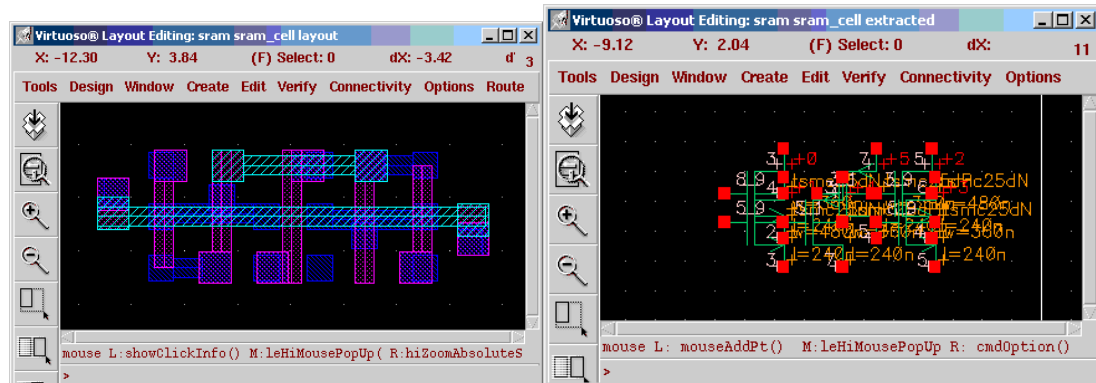
**HSPICE After Ground Metal 3 Connection**

```
* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICES/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 18 20:57:07 2006

M0 3 8 4 1 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M1 4 3 8 1 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M2 3 8 7 5 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6
M=1
M3 7 3 8 5 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9
M=1
M4 6 2 3 5 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9
M=1
M5 8 2 9 5 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6
M=1

* INCLUDE FILES

* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END
```

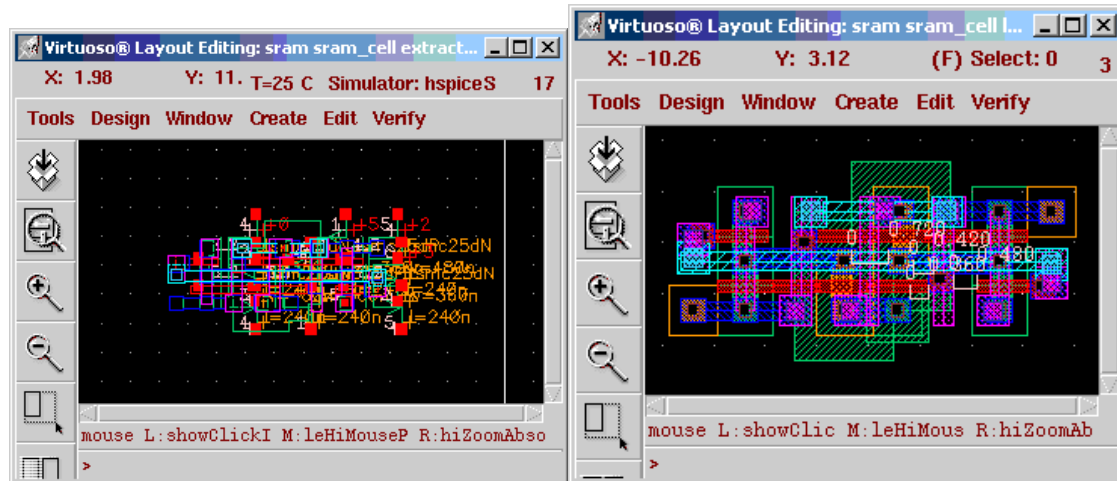**Final HSPICE SRAM Cell Extracted**

```

* # FILE NAME:
/HOME/AA/UGRAD/BILLHUNG/CADENCE/SIMULATION/SRAM_CELL/HSPICES/
* EXTRACTED/NETLIST/SRAM_CELL.C.RAW
* NETLIST OUTPUT FOR HSPICES.
* GENERATED ON MAR 18 22:14:53 2006

M0 2 5 1 1 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M1 1 2 5 1 TSMC25DP L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=273.599990319867E-15 PD=1.7999999499807E-6 PS=1.7999999499807E-6
M=1
M2 2 5 7 7 TSMC25DN L=240E-9 W=480E-9 AD=165.599996280845E-15
+AS=288.000011209114E-15 PD=779.999993483216E-9 PS=1.67999996847357E-6
M=1
M3 7 2 5 7 TSMC25DN L=240E-9 W=480E-9 AD=288.000011209114E-15
+AS=165.599996280845E-15 PD=1.67999996847357E-6 PS=779.999993483216E-9
M=1
M4 4 3 2 7 TSMC25DN L=240E-9 W=360E-9 AD=273.599990319867E-15
+AS=165.599996280845E-15 PD=1.7999999499807E-6 PS=779.999993483216E-9
M=1
M5 5 3 6 7 TSMC25DN L=240E-9 W=360E-9 AD=165.599996280845E-15
+AS=273.599990319867E-15 PD=779.999993483216E-9 PS=1.7999999499807E-6
M=1

* INCLUDE FILES

* END OF NETLIST
.TEMP 25.0000
.OP
.save
.OPTION INGOLD=2 ARTIST=2 PSF=2
+ PROBE=0
.END

```