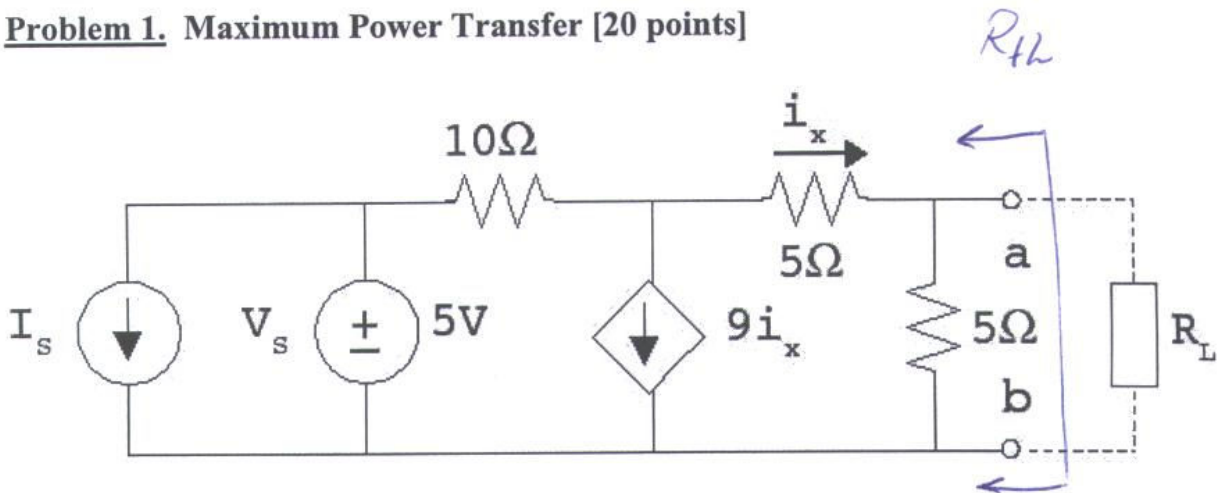



Name \_\_\_\_\_

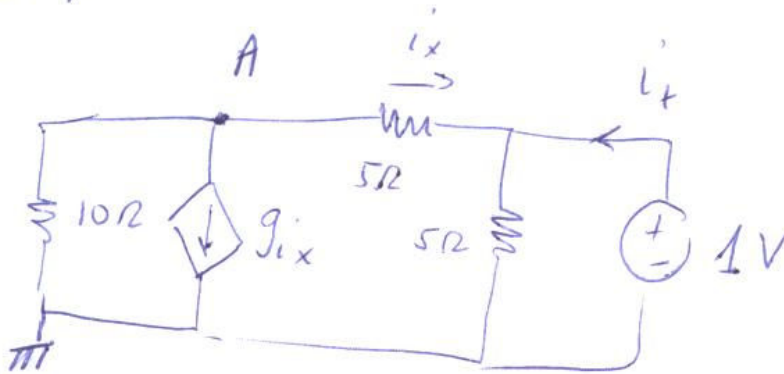**Problem 1. Maximum Power Transfer [20 points]**



Find the optimal  $R_L$  such that the power delivered to  $R_L$  is maximized. What power is dissipated by  $R_L$ ?

*The power is maximized if  $R_L = R_{th}$*



$$\text{KCL@A: } \frac{V_A}{10} + 9i_x + \frac{V_A - 1V}{5} = 0$$

$$i_x = \frac{V_A - 1V}{5} \Rightarrow \frac{V_A}{10} + 9 \left( \frac{V_A - 1V}{5} \right) = 0$$



$$V_A \left[ \frac{1}{10} + 2 \right] = 2V$$

$$V_A = \frac{2V}{2.1} = 0.95V$$


$$i_t = \frac{1V}{5} + \frac{1 - V_A}{5} = 0.21A$$

$$\Rightarrow R_{th} = 4.76\Omega \Rightarrow R_L = 4.76\Omega$$

Name \_\_\_\_\_

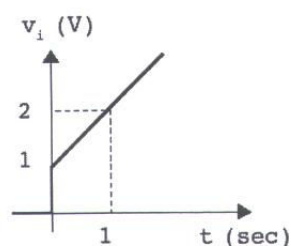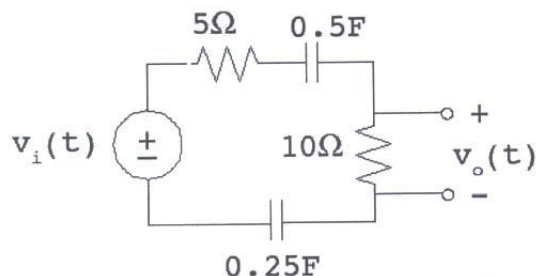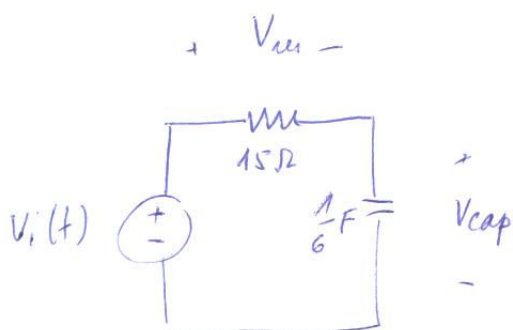**Problem 2. First-Order Transients [30 points]**

Find and plot  $v_o(t)$  for  $t \in [0, 2]$ . (Hint: It may be easier for you to first find  $i(t)$ .)  
Annotate  $v_o(0^+)$ ,  $v_o(2)$ .



$$V_o = \frac{10}{15} \quad V_{res} = \frac{2}{3} V_{res}$$

$$\tau = R_{eq} \cdot C_{eq} = 2.5 \text{ s}$$

$$\text{KVL: } V_{res} + V_{cap} = V_i$$

$$\Rightarrow R_{eq} i(t) + V_{cap}(t) = V_i(t)$$

$$R_{eq} i(t) + \frac{1}{C_{eq}} \int i(t) dt = V_i(t)$$

$$\tau \frac{di(t)}{dt} + i(t) = 1 \cdot C_{eq} \text{ for } t > 0$$

$$i(t) = i_c(t) + i_p(t), \quad i_p(t) = K$$

$$\Rightarrow \tau \cdot \frac{di_p(t)}{dt} + i_p(t) = 1/6 \Rightarrow K = 1/6$$

$$i_c(t) = K' e^{-t/\tau}$$


$$\Rightarrow i(t) = \frac{1}{6} + K' e^{-t/\tau}$$

$$\Rightarrow \frac{1}{6} + K' = \frac{1}{15} \quad K' = -\frac{1}{10}$$

$$\Rightarrow i(t) = \frac{1}{6} - \frac{1}{10} e^{-t/\tau} \Rightarrow v_o = 10 i(t) = \underline{\underline{\frac{5}{3} - e^{-t/\tau}}}$$

$$\text{and } i(0^+) = \frac{V_i(0^+)}{R_{eq}} = \frac{1}{15}$$

Name \_\_\_\_\_

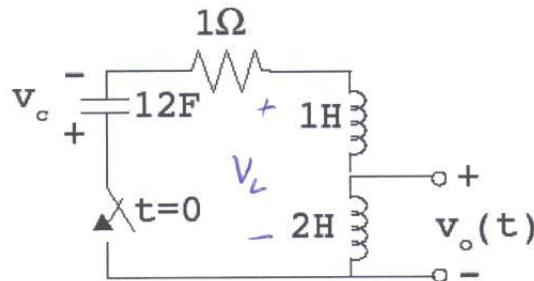**Problem 3. Second-Order Transients [30 points]**

The switch has been open for a long time with the capacitor charged to  $v_c = 10$  V. The switch closes at time  $t = 0$ . Find  $v_o(t)$  for  $t > 0$ .

$$\frac{V_o}{V_L} = \frac{2}{3}$$

$$\text{KVL: } V_{\text{cap}} + V_L + V_R = 0$$

$$\frac{1}{C} \int i(t) dt + L \frac{di(t)}{dt} + \frac{i}{R} = 0$$

$$\Rightarrow \frac{1}{LC} i(t) + \frac{di(t)}{dt} \cdot \frac{1}{RL} + \frac{d^2 i(t)}{dt^2} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{6} \text{ rad/s} \quad \zeta = \frac{\alpha}{\omega_0} = \frac{1}{2RL\omega_0} = 1$$

$\Rightarrow$  The solution is of the form:  $K_1 + K_2 e^{-\omega_0 t} + K_3 t e^{-\omega_0 t}$   
Finding  $K_1, K_2, K_3$  from initial conditions:

$$i(0^+) = i(0^-) = 0 \Rightarrow K_1 + K_2 = 0 \quad \left. \vphantom{i(0^+)} \right\} \Rightarrow K_2 = 0$$


$$i(\infty) = 0 \Rightarrow K_1 = 0$$

$$V_L(0^+) = L \frac{di(0^+)}{dt} = -10V \Rightarrow K_3 = -10/3$$

$$\Rightarrow i(t) = -10/3 t e^{-\omega_0 t}$$

$$\Rightarrow V_o(t) = L \frac{di(t)}{dt} = -\frac{20}{3} [e^{-\omega_0 t} - \omega_0 t e^{-\omega_0 t}]$$

Name \_\_\_\_\_

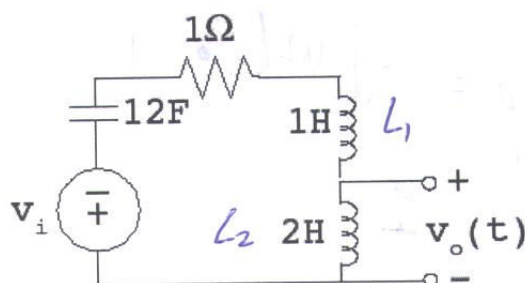**Problem 4. Steady-State Sinusoidal Analysis [20 points]** $v_i(t) = 5 \cos(0.1t + 30^\circ)$ . What is  $v_o(t)$ ?

$$V_o = \frac{Z_{L_2}}{Z_{eq}} V_i(t) \quad (6)$$

$$\frac{V_o}{V_i} = \frac{j\omega L_2}{R + \frac{1}{j\omega C} + j\omega(L_1 + L_2)} = \frac{\omega^2 L_2 C}{1 - \omega^2(L_1 + L_2)C + j\omega RC} \quad (7)$$

$$\frac{V_o}{V_i}(0.1) = \frac{(0.1)^2 \cdot 2 \cdot 12}{1 - (0.1)^2(3)12 + j0.1 \cdot 1 \cdot 12} \quad (8)$$

$$= \frac{0.24}{0.64 + j0.12} = -0.88 \angle 148.06^\circ \quad (9)$$

process of finding Phasor (8,9)

$$\Rightarrow v_o(t) = -0.88 \cos(0.1t + 148.06^\circ) \quad (10) \text{ Final Answer}$$

**BONUS [2 points]:** Sketch the bode plot of the transfer function from  $v_i$  to  $v_o$ .