

EE40 HW1 p1

1.10

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} (3 - 3e^{-2t}) = 6e^{-2t} \text{ A}$$

1.16

V is constant

$$V = \frac{dw}{dq} \rightarrow w = \int V dq = V \int dq = Vq$$

$$\rightarrow q = \frac{w}{V} = \frac{600 \text{ J}}{12 \text{ V}} = 50 \text{ C}$$

increase chem. energy \rightarrow absorb electrical energy


$\rightarrow p > 0 \rightarrow$ current in terminal a (+) \rightarrow electrons out a

\rightarrow electrons from b to a

1.18

$$p(t) = v_{ab}(t) i_a(t) = 50 \sin(200\pi t) \text{ W}$$

a) $p(t)$ (W)

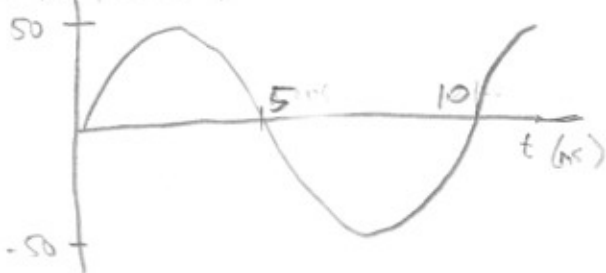

$$(b) p = \frac{dw}{dt} \rightarrow w = \int p dt = \int_0^{0.005} 50 \sin(200\pi t) dt = -\frac{50}{200\pi} \cos(200\pi t) \Big|_0^{0.005}$$

$$w = -\frac{1}{4\pi} (-1 - 1) = \frac{1}{2\pi} = 0.159 \text{ J}$$


(c) From the plot we can see it will be 0 J or doing the math:

$$w = \int_0^{0.01} 50 \sin(200\pi t) dt = -\frac{50}{200\pi} \cos(200\pi t) \Big|_0^{0.01}$$

$$= -\frac{1}{4\pi} (1 - 1) = 0 \text{ J}$$

Ex 40 HW 1 p 2

P 1.28

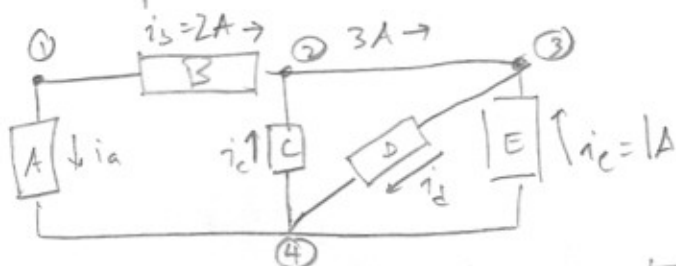


KCL @ ① $i_a + i_b = 0A \rightarrow i_a + 2A = 0 \rightarrow i_a = -2A$

KCL @ ② $-i_b + 3A - i_c = 0A \rightarrow -2A + 3A - i_c = 0A \rightarrow i_c = 1A$

KCL @ ③ $-3A - i_e + i_d = 0A \rightarrow -3A - 1A + i_d = 0A \rightarrow i_d = 4A$

Elements A and B are in series. (All other nodes connect 3 or more elements)

P 1.32

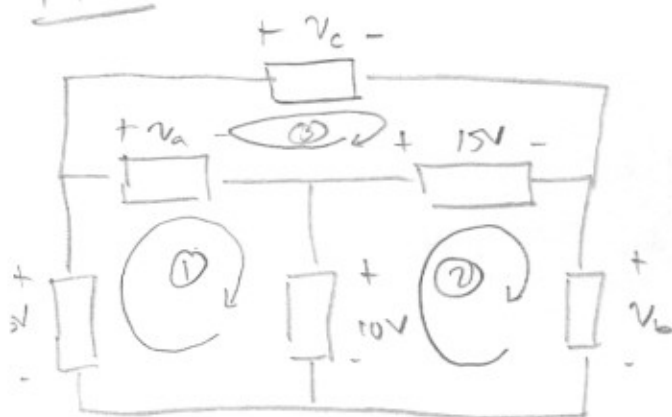

KVL on ①: $v_a + 10V - 5V = 0V$

$v_a = -5V$

KVL on ②

$v_b - 10V + 15V = 0V$

$v_b = -5V$

KVL on ③

$v_c - 15V - v_a = 0V$

$v_c - 15V + 5V = 0V$

$v_c = 10V$

P 1.36



KVL on ① (acba) $v_{ac} + 15V - 5V = 0V$

$v_{ac} = -10V$

KVL on ② (abcd a)

$5V - 15V + v_{cd} + 10V = 0V$

$v_{cd} = 20V$

P 1.43

$P = v i = v \left(\frac{v}{R} \right) = \frac{v^2}{R} \rightarrow R = \frac{v^2}{P} = \frac{(100V)^2}{100W} = 100\Omega$

$P_{new} = \frac{v_{new}^2}{R} = \frac{(0.9 v_{old})^2}{R} = \frac{0.81 v_{old}^2}{R} = 0.81 P_{old}$

So power is reduced by 19%

240 HW1 p3

> 1.46


$$R = \frac{\rho L}{A} = 0.5 \Omega$$

$$2) R_a = \frac{\rho 2L}{A} = 2 \frac{\rho L}{A} = 2R = \boxed{1 \Omega}$$

$$(b) R = \frac{\rho L}{A} = \frac{\rho L}{\pi (\frac{d}{2})^2}$$

$$R_b = \frac{\rho L}{\pi (\frac{2d}{2})^2} = \frac{\rho L}{4\pi (\frac{d}{2})^2} = \frac{R}{4} = \boxed{0.125 \Omega}$$

P 1.47

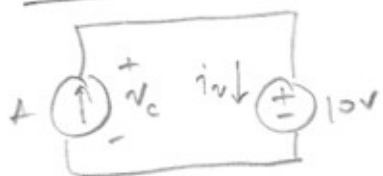


By KCL $i_v = 2A \rightarrow P_v = (10V)(2A) = 20W$

By KVL $v_c = 10V \rightarrow P_c = (10V)(-2A) = -20W$

The current source is supplying power and the voltage source is absorbing it.

P 1.51

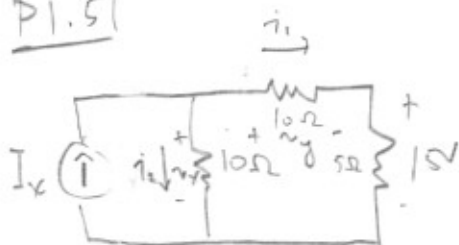

By ohm's law on the 5Ω:

$$i_1 = \frac{15V}{5\Omega} = 3A$$

By ohm's law on the top 10Ω:

$$v_y = i_1(10\Omega) = (3A)(10\Omega) = 30V$$

By KVL on the loop with all the resistors:

$$v_x - 15V - v_y = 0V$$

$$v_x - 15V - 30V = 0V \rightarrow v_x = 45V$$


By ohm's law on the last resistor:

$$i_2 = \frac{v_x}{10\Omega} = \frac{45V}{10\Omega} = 4.5A$$

By KCL at the top left

$$-I_x + 3A + 4.5A = 0A \rightarrow I_x = \boxed{7.5A}$$

P1.57

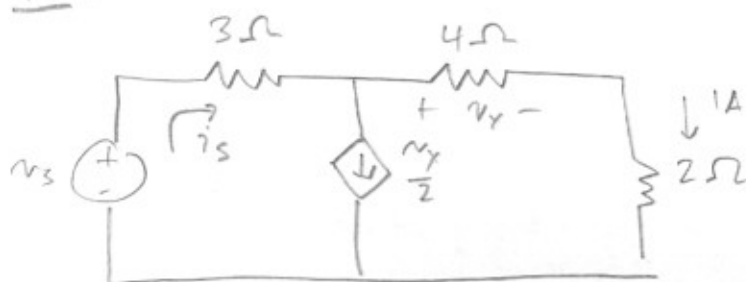


Ohm's law on the 4Ω : $v_y = (1A)(4\Omega) = 4V$

KCL @ bottom: $i_s - \frac{v_y}{2\Omega} - 1A = 0$
 $i_s = \frac{4V}{2\Omega} + 1A = 3A$


KVL around outside: $-v_s + 3i_s + 4V + (1A)(2\Omega) = 0$
 $v_s = \boxed{15V}$

P2.14

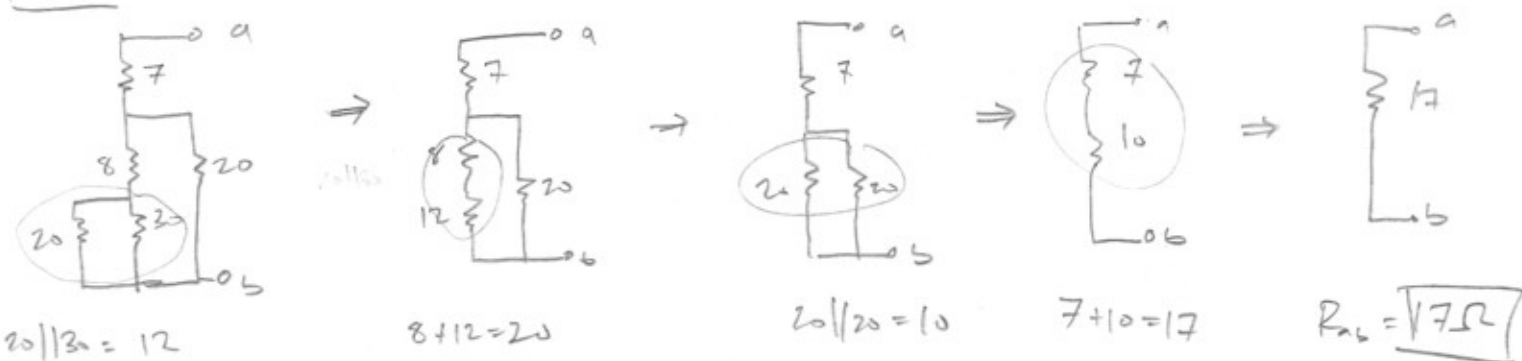


P2.27

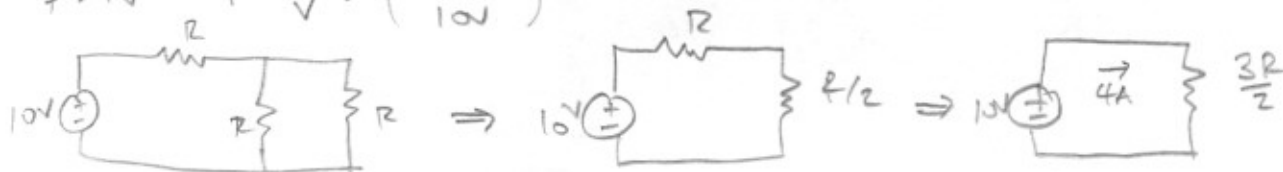$P = i v \rightarrow i = \frac{P}{v} = \frac{-40W}{10V} = -4A$



By Ohm's law: $\frac{P}{2} = \frac{v}{i} \rightarrow \frac{3R}{2} = \frac{10V}{4A} = \frac{5}{3}\Omega = \boxed{1.667\Omega}$

P2.36

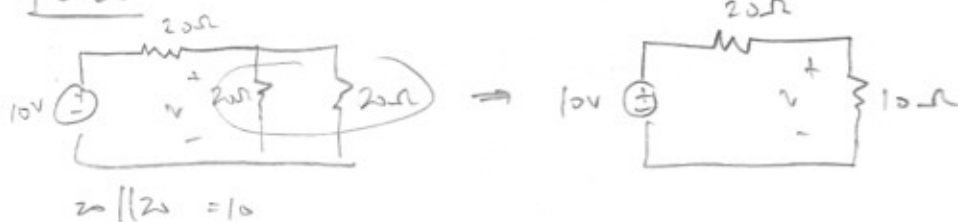


By voltage division:
 $v = \left(\frac{10}{10+20}\right)10V = \boxed{\frac{10}{3}V = 3.333V}$

P2.37

$$i_3 = \left(\frac{R_2}{R_2 + R_3} \right) i_s = \frac{15\Omega}{(15\Omega + 5\Omega)} 10A = \boxed{7.5A}$$

P2.38

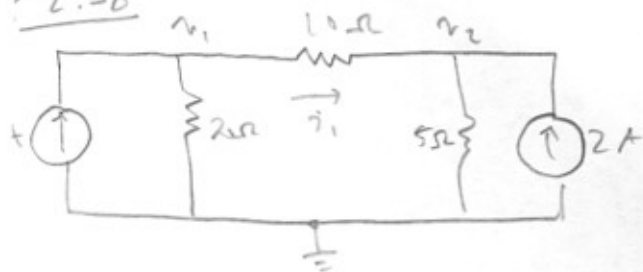

$$\textcircled{1} -1A + \frac{v_1 - v_2}{10\Omega} + \frac{v_1}{20\Omega} = 0$$

$$\textcircled{2} \frac{v_2 - v_1}{10\Omega} + \frac{v_2}{5\Omega} - 2A = 0$$

Solving: $\textcircled{1} \quad 3v_1 - 2v_2 = 20 = 0$

$\textcircled{2} \quad -v_1 + 3v_2 = 20$

$\textcircled{1} + 3\textcircled{2}$


$$7v_2 = 80$$

$$v_2 = \frac{80}{7} = \boxed{11.429 = v_2}$$

$$v_1 = 3v_2 - 20 = \boxed{14.286 = v_1}$$

$$i_1 = \frac{v_1 - v_2}{10\Omega} = \boxed{0.286A = i_1}$$

P2.52

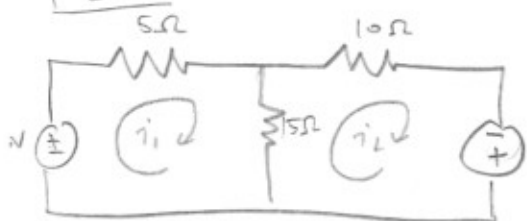

$$\textcircled{1} -20V + 5\Omega i_1 + 15\Omega (i_1 - i_2) = 0$$

$$\textcircled{2} 15\Omega (i_2 - i_1) + 10\Omega i_2 - 10V = 0$$

Solving:

$$\textcircled{1} \quad 20i_1 - 15i_2 = 20$$

$$\textcircled{2} \quad -15i_1 + 25i_2 = 10$$

$$5\textcircled{1} + 3\textcircled{2} = 55i_1 = 130$$

$$i_1 = \frac{130}{55} = \boxed{2.364A = i_1}$$

$$i_2 = \frac{10 + 15i_1}{25} = \boxed{1.818A = i_2}$$