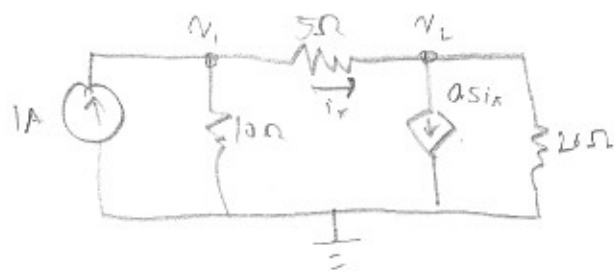


P2.46



$$\textcircled{1} -1A + \frac{v_1}{10\Omega} + \frac{v_1 - v_2}{5\Omega} = 0 \quad \swarrow i_x$$

$$\textcircled{2} \frac{v_2 - v_1}{5\Omega} + \frac{v_2}{2\Omega} + 0.5\left(\frac{v_1 - v_2}{5\Omega}\right) = 0$$


Simplifying: $0.3v_1 - 0.2v_2 = 1$
 $-0.1v_1 + 0.15v_2 = 0$

Solving: $v_1 = 6V, v_2 = 4V$

$i_x = \frac{v_1 - v_2}{5} = 0.4A$

P2.49

Using the hint, we apply a test current:

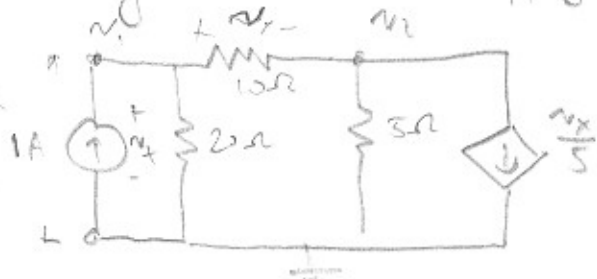

$$\textcircled{1} -1A + \frac{v_1}{2\Omega} + \frac{v_1 - v_2}{10\Omega} = 0 \quad \swarrow i_x$$


$$\textcircled{2} \frac{v_2 - v_1}{10\Omega} + \frac{v_2}{5\Omega} + \frac{1}{5}\left(\frac{v_1 - v_2}{10\Omega}\right) = 0$$

Simplifying: $0.15v_1 - 0.1v_2 = 1$
 $v_1 + v_2 = 0 \rightarrow v_2 = -v_1$

Substituting: $0.15v_1 + 0.1v_1 = 1$
 $\rightarrow v_1 = 4 \rightarrow v_2 = -v_1 = -4V$

$R_{eq} = \frac{v_x}{i_x} = \frac{4V}{1A} = 4\Omega$

P2.51

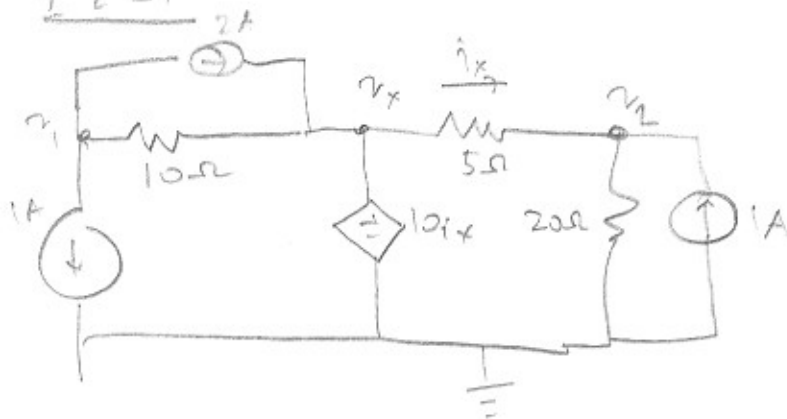

Ohm's law on 5Ω:

$$10i_x - v_2 = (i_x)(5\Omega) \rightarrow i_x = \frac{v_2}{5}$$

$$v_x - v_2 = \left(\frac{v_2}{5}\right)(5) \rightarrow v_x = 2v_2$$

Now we can do nodal:


$$\textcircled{1} -3A + \frac{v_1 - 2v_2}{10\Omega} = 0$$

$$\textcircled{2} \frac{v_2 - 2v_2}{5\Omega} + \frac{v_2}{2\Omega} - 1A = 0$$

Solving: $v_1 = -43.333V, v_2 = -6.667V$

EE46 HW2 p2

P2.61

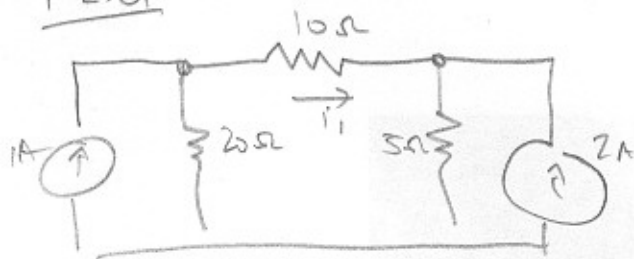


Because of the current sources there is only 1 unknown mesh current: i_1 .

Using KVL: $10i_1 + 5(i_1 + 2) + 20(i_1 - 1) = 0$

$$i_1 = \frac{2}{7} = 0.286$$

P2.46 (using mesh)

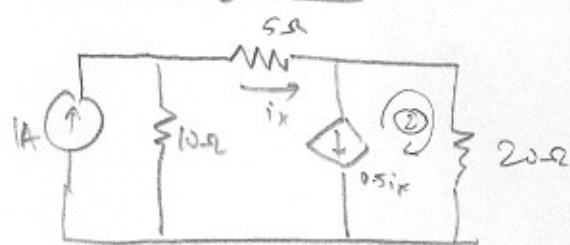

We know one mesh from the current source, we call the next i_x and the last, i_2 . Can be solved using the

Because we don't know the voltage across the dependent source we use a supermesh!

$$5i_x + 20i_2 + 10(i_x - 1) = 0$$

For our second equation, we use the dependent source:


$$i_x - i_2 = 0.5i_x \rightarrow i_2 = \frac{1}{2}i_x$$

Substituting in:

$$5i_x + 10i_x + 10i_x - 10 = 0 \rightarrow i_x = \frac{2}{5} = 0.4$$

P2.66

First, V_{oc} :

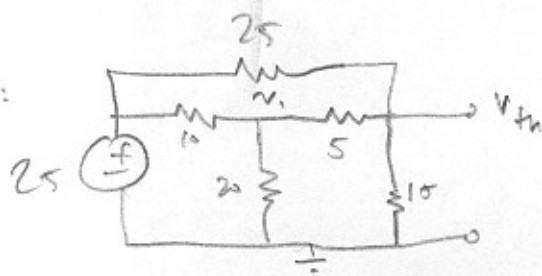


Node 1: $\frac{v_1 - 25}{10} + \frac{v_1}{20} + \frac{v_1 - V_{th}}{5} = 0$

Node 2: $\frac{V_{th} - 25}{25} + \frac{V_{th} - v_1}{5} + \frac{V_{th}}{15} = 0$

Simplifying: $0.35v_1 - 0.2V_{th} = 2.5$
 $-0.2v_1 + 0.3067V_{th} = 1$

Solving: $v_1 = 14.356$
 $V_{th} = 12.624$

Then i_{sc} :

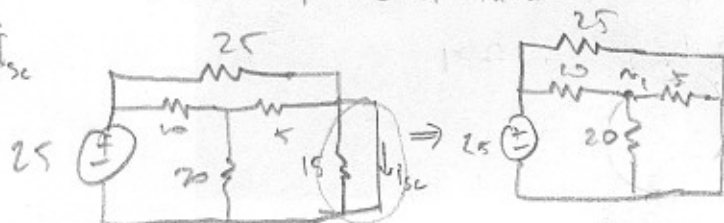


Node 1: $\frac{v_1 - 25}{10} + \frac{v_1}{20} + \frac{v_1}{5} = 0 \rightarrow v_1 = 10$

KCL: $i_{sc} = \frac{25V}{25\Omega} + \frac{v_1}{5\Omega} = \frac{17}{5} = 3.4$



P 2.66 (cont'd)

$$R_{eq} = \frac{V_{oc}}{i_{sc}} = \frac{12.624}{2.429} = 5.197$$

Thevenin:

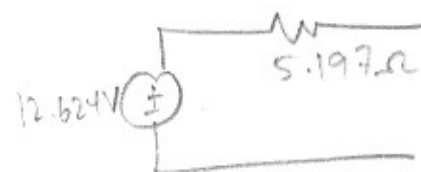


Norton:

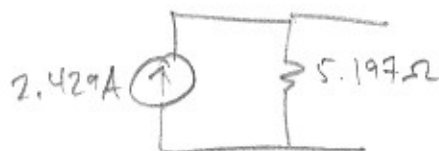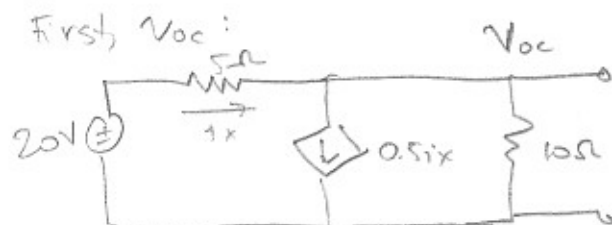P 2.72First, V_{oc} :

Kohler:

$$\frac{V_{oc} - 20}{5} + 0.5 \left(\frac{20 - V_{oc}}{5} \right) + \frac{V_{oc}}{10} = 0$$

$$V_{oc} = 10V$$

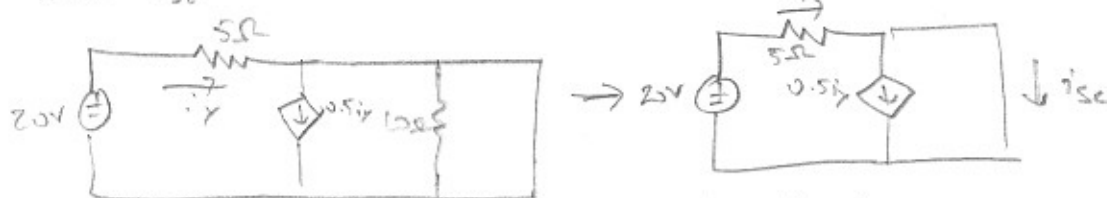
Then i_{sc} :

$$\text{Ohm's: } i_x = \frac{20V}{5\Omega} = 4A$$

$$\text{KCL: } i_{sc} = i_x - 0.5i_x = 2A$$

$$R_{eq} = \frac{V_{oc}}{i_{sc}} = \frac{10V}{2A} = 5\Omega$$


Thevenin:

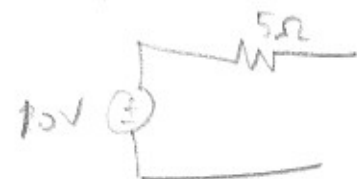

Norton:

P 2.81

From the voltage source:

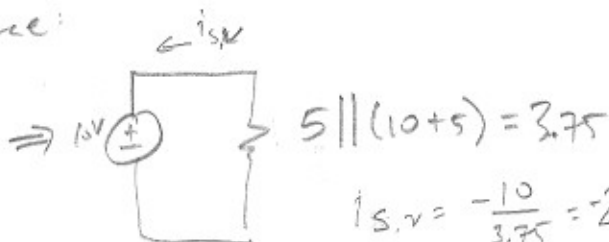


$$i_{s.v} = \frac{-10}{3.75} = -2.667A$$

EE40 HW2 p4

P2.81 (cont'd)

from the current source:

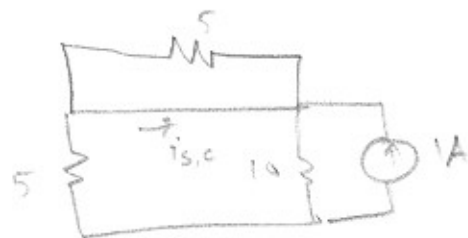


$$i_{sc} = \left(\frac{10}{5+10} \right) (1A) = -0.667A$$

$$i_s = i_{sv} + i_{sc} = -2.667A - 0.667A = \boxed{-3.333A}$$

P2.85

(a) Zeroing the 1A:

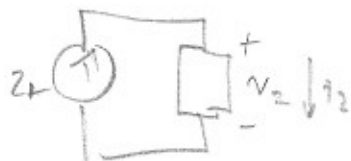


$$i_2 = 2A, \quad v_2 = 2(2)^3 = 16V$$

(b) Zeroing the 2A:



$$i_1 = 1A, \quad v_1 = 2(1)^3 = 2V$$

(c) With both:

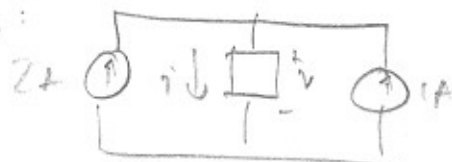


$$i = 3A, \quad v = 2(3)^3 = 54V$$

$$16V + 2V \neq 54V$$

Superposition does not apply because A is nonlinear.

P2.47 (using superposition)

From the 5A source:

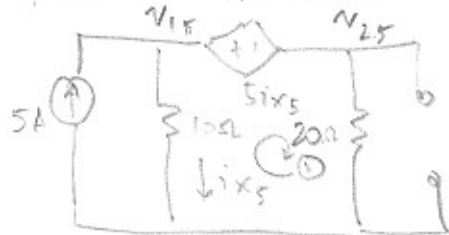

Using Mesh:

$$5i_{x5} + 20i_1 + 10(i_1 - 5) = 0 \quad \text{where } i_{x5} = 5 - i_1$$

$$25 - 5i_1 + 20i_1 + 10i_1 - 50 = 0$$

$$i_1 = 1A$$

$$v_{15} = (5 - i_1)10 = 40V$$

$$v_{25} = 20i_1 = 20V$$

From the 3A source:



Using Mesh:

$$5i_{x3} + 20(i_1 + 3) + 10i_1 = 0 \quad \text{where } i_{x3} = -i_1$$

$$-5i_1 + 20i_1 + 60 + 10i_1 = 0$$

$$i_1 = -2.4A$$

$$v_{13} = (-i_1)(10\Omega) = 24V$$

$$v_{23} = (i_1 + 3)20\Omega = 140V$$


$$v_1 = v_{13} + v_{15} = 64V$$

$$v_2 = v_{23} + v_{25} = 160V$$


HW2 p5

P3.10


$$v = \frac{1}{C} \int i dt + v_0$$

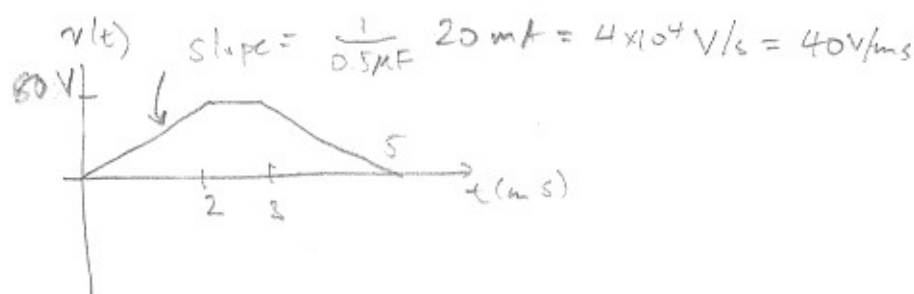

$$p = i v$$

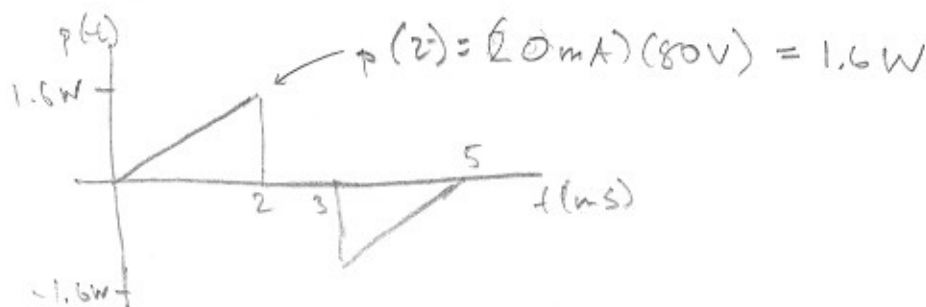

$$W = \frac{1}{2} C v^2$$

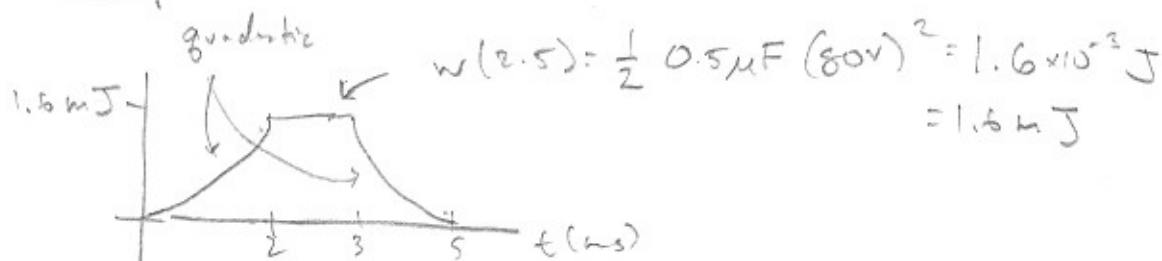

P3.19

$$p(0) = i(0) v(0) = (5 \text{ mA})(-20 \text{ V}) = -100 \text{ mW} \quad \text{power is flowing out (p < 0)}$$

$$v(t) = \frac{1}{C} \left[\int_0^t i(t) dt \right] - v(0) = \frac{1}{100 \mu F} \left[\int_0^t 5 \text{ mA} dt \right] - 20 \text{ V}$$

$$= 50t - 20$$

$$p(1) = i(1) v(1) = (5 \text{ mA})(50(1) - 20) = 150 \text{ mW}$$

power is flowing in (p > 0)

P3.25

Because the charges are the same: $C_1 v_1 = C_2 v_2 \rightarrow v_1 = 2v_2$

and by KVL $v_1 + v_2 = 12 \text{ V}$

Solving: $v_1 = 8 \text{ V}, v_2 = 4 \text{ V}$



P3.43

$$i(t) = \frac{1}{L} \left[\int_0^t v(t) dt \right] + i(0) = \frac{1}{2H} \int_0^t v(t) dt$$

$$i(2) = 15A \quad \text{slope} = \frac{1}{2H} 10V = 5A/s$$


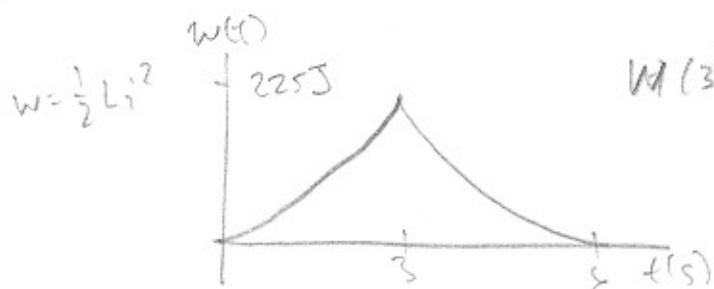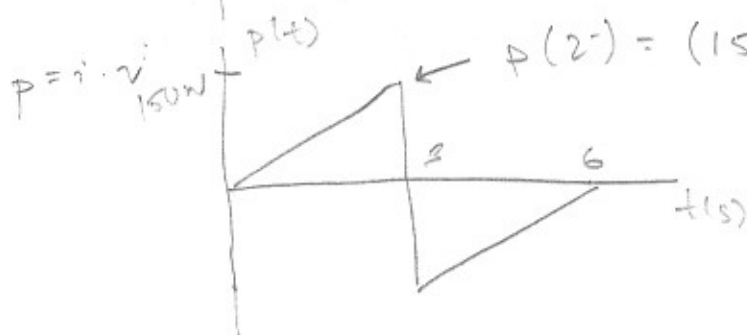
$$p = i \cdot v \quad p(2) = (15A)(10V) = 150W$$



$$w(3) = \frac{1}{2}(2H)(15A)^2 = 225J$$

P3.58

To find $i(t)$, we combine the inductors in parallel.

$$i(t) = \frac{L_1 + L_2}{L_1 L_2} \int_0^t v(t) dt + i(0) \rightarrow i(t) \frac{L_1 L_2}{L_1 + L_2} = \int_0^t v(t) dt$$

For L_1 alone, the voltage is also $v(t)$ making

$$i_1(t) = \frac{1}{L_1} \int_0^t v(t) dt + i_1(0) \rightarrow i_1(t) L_1 = \int_0^t v(t) dt$$


Setting these equal: $i(t) \frac{L_1 L_2}{L_1 + L_2} = i_1(t) L_1$

$$i_1(t) = \frac{L_2}{L_1 + L_2} i(t)$$

The math is the same for $i_2(t) = \frac{L_1}{L_1 + L_2} i(t)$

Notice this is a current divider just like with resistors!

1)

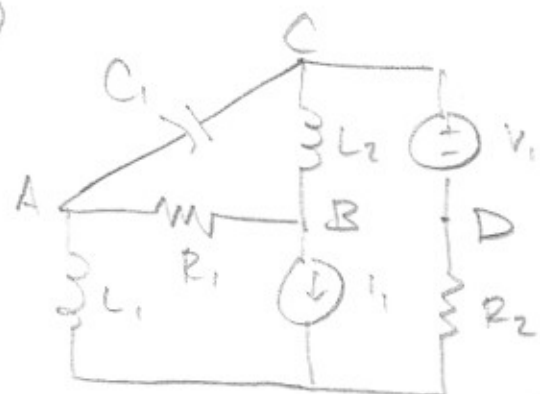

We will use nodal analysis with a supernode combining C and D.

For the voltage source:

$$\boxed{C - D = V_1}$$

For the supernode:

$$C_1 \frac{d}{dt}(C-A) + \frac{1}{L} \int (C-B) dt + C_0 - B_0 + \frac{D}{R_2} = 0$$

Taking a derivative:

$$\boxed{C_1 \ddot{C} - C_1 \ddot{A} + \frac{1}{L} C - \frac{1}{L} B + \frac{1}{R_2} \dot{D} = 0}$$

For node A:

$$\frac{1}{L} \int A dt + A_0 + \frac{1}{R}(A-B) + C_1 \frac{d}{dt}(A-C) = 0$$


$$\boxed{\frac{1}{L} A + \frac{1}{R} \dot{A} - \frac{1}{R} \dot{B} + C_1 \ddot{A} - C_1 \ddot{C} = 0}$$

For node B:



$$\frac{1}{L} \int (B-C) dt + B_0 - C_0 + \frac{1}{R}(B-A) + I_1 = 0$$

$$\boxed{\frac{1}{L} B - \frac{1}{L} C + \frac{1}{R} \dot{B} - \frac{1}{R} \dot{A} + \dot{I}_1 = 0}$$

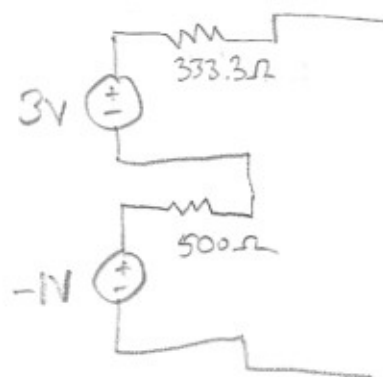
2) Since the networks are in series, we will represent them with their thevenin equivalent



Combining

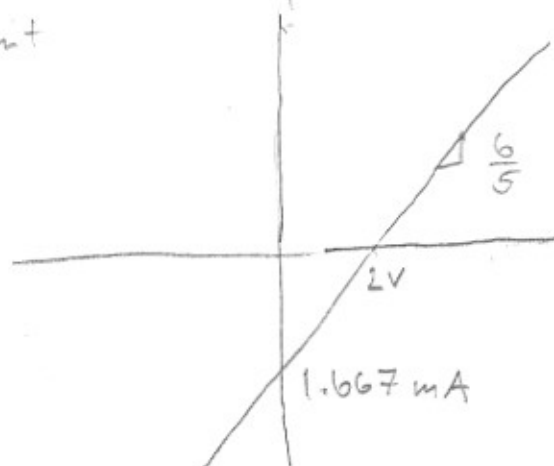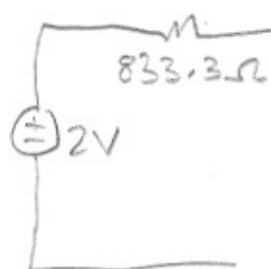

Finding v_o

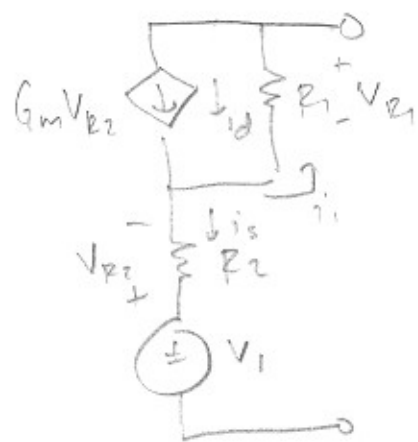

Since there can be no current through the bottom branch, $V_{R2} = 0 \cdot R_2 = 0$


This means the dependent source will have $i_d = (G_m \cdot 0) = 0$

By KCL $i_i = i_d - i_s = 0$

So $V_{R1} = 0 \cdot R_1 = 0$

Thus $V_{th} = V_1$

Finding i_{sc}

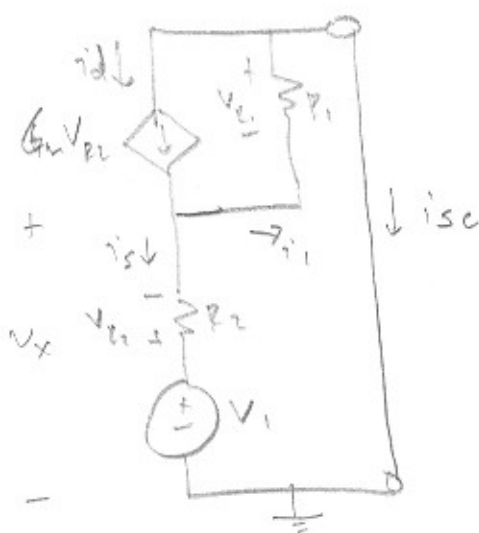

Mod. 2:

We have 1 unknown: v_x

$$KCL: G_m V_{R2} = \frac{v_x}{R_1} + \frac{v_x - V_1}{R_2}$$

But $V_{R2} = V_1 - v_x$, making this:

$$G_m V_1 - G_m v_x = \frac{v_x}{R_1} + \frac{v_x - V_1}{R_2}$$

$$\rightarrow v_x = \frac{(G_m V_1 + \frac{V_1}{R_1})}{(\frac{1}{R_1} + \frac{1}{R_2} + G_m)}$$

$$i_{sc} = -i_s = \frac{V_1 - v_x}{R_2} = \frac{V_1 - \left(\frac{G_m V_1 + \frac{V_1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + G_m} \right)}{R_2}$$

$$R_{eq} = \frac{V_{th}}{I_n} = \frac{V_1 R_2}{V_1 - \left(\frac{G_m V_1 + \frac{V_1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + G_m} \right)} = R_{eq}$$

