

**University of California**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

Octavian Florescu

**Problem Set 3**  
**Due Monday June 17<sup>th</sup> at 6pm**

**EE40**  
**Summer 2006**

**Reading:**

Chap 4, 5 (skip 5.7), 6-6.8 of Hambley 3<sup>rd</sup> Edition

**Problems:**


*Chap 4:* 4.15, 4.36, 4.38, 4.45, 4.51

*Chap 5:* 5.32, 5.43, 5.44, 5.46, 5.47

*Chap 6:* 6.14, 6.27, 6.46, 6.56, 6.57


Additional Problems:

**Problem 1:**

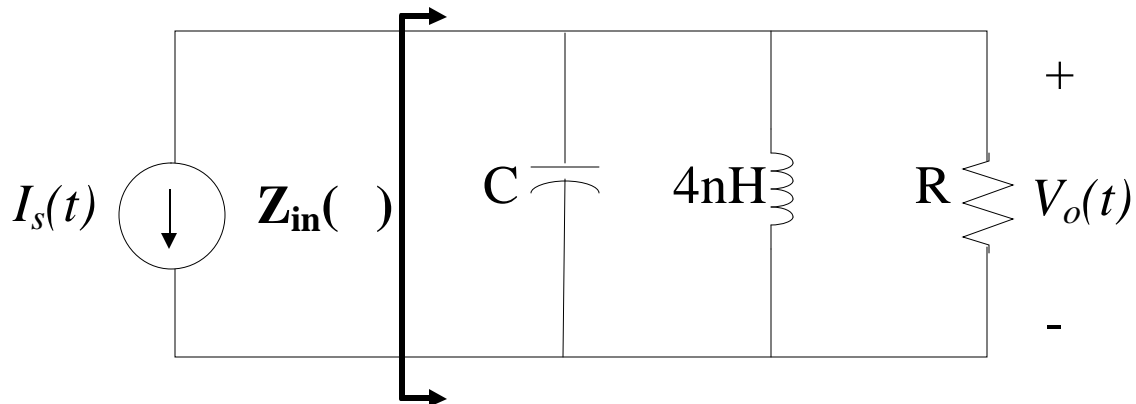


- a. For the circuit above, find the values of  $C$  and  $R$  such that  $\omega_o = 1 \text{ Mrad/s}$  and  $\zeta = 1/2$ .
- b. Is the system over-damped, critically damped or under-damped?
- c. Find complex impedance  $Z_{in}(\omega)$ . What is the value of  $Z_{in}(\omega_o)$ ?
- d.  $I_s(t) = A \cos(\omega_o t) + A \cos(2\omega_o t) + A \cos(\omega_o t/2)$ . Find  $V_o(t)$ . [Hint: no need to solve differential equation. Use phasors]

**Problem 2:**

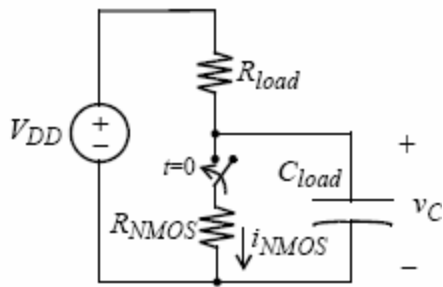

Plot  $v_C(t)$  for  $R_{load}=10k$  ,  $R_{NMOS}=1k$  ,  $C_{load}=10\mu F$  and  $V_{DD}=5V$

**Problem 3:**

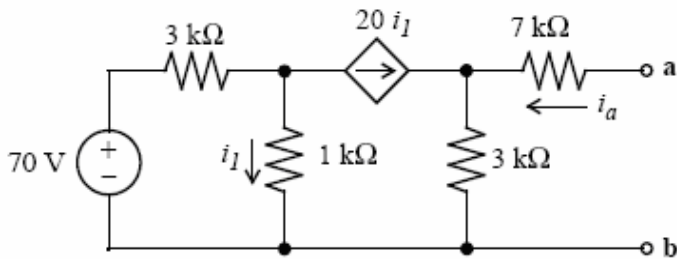

Find the Norton Equivalent between nodes **a** and **b**.