

P4.15

At steady state, the capacitors are like open circuits and the inductors like shorts:



Because of the open circuit $i_1 = 0A$. Therefore all the current goes through the loop with i_2 and i_3 .

$$i_2 = i_3 = 2A$$

P4.36

$$(a) \quad i(0^+) = \frac{v_1(0^+) - v_2(0^+)}{R} = \frac{100V - 0V}{100k\Omega} = 1mA$$

$$(b) \quad \underbrace{i(t)R}_{v_R} + \underbrace{\frac{1}{C_2} \int_0^t i(t) dt + v_2(0^+)}_{v_2} + \underbrace{\frac{1}{C_1} \int_0^t i(t) dt - v_1(0^+)}_{-v_1} = 0$$

In differential form:

$$R \frac{di(t)}{dt} + \left(\frac{1}{C_1} + \frac{1}{C_2} \right) i(t) = 0$$

$$(c) \quad \tau = \frac{R}{\left(\frac{1}{C_1} + \frac{1}{C_2} \right)} = \frac{RC_1 C_2}{C_1 + C_2} = \frac{(100k\Omega)(1\mu F)(1\mu F)}{(1\mu F + 1\mu F)} = \frac{10^5 10^{-6} 10^{-6}}{2 \times 10^{-6}} s$$

$$= \frac{1}{20} s = \boxed{50ms}$$

$$(d) \quad i(t) = K e^{-t/\tau}$$

$$i(0^+) = 1mA \rightarrow K = 1mA \quad \Rightarrow \quad \boxed{i(t) = (1mA) e^{-t/(50ms)}}$$

$$(e) \quad v_2(t) = \frac{1}{C_2} \int_0^t i(t) dt + v_2(0^+)$$

$$v_2(\infty) = \frac{1}{1\mu F} \int_0^\infty 1mA e^{-t/50ms} dt + 0$$

$$= 10^6 [-50 \times 10^{-3} \times 10^{-3} e^{-t/5 \times 10^{-2}}]_0^\infty = -50(0-1) = \boxed{50V}$$

P 4.38

$$\text{KVL: } i(t)R + L \frac{di(t)}{dt} = v(t)$$

$$2 \frac{di(t)}{dt} + 10i(t) = 10t$$

$$i_p(t) = A + Bt$$

$$\frac{d}{dt} i_p(t) = B \rightarrow 2B + 10A + 10Bt = 10t$$

$$2B + 10A = 0 \quad 10B = 10 \rightarrow B = 1, A = -0.2$$

$$i_p(t) = -0.2 + t$$

$$i_c(t) = K e^{-t/(L/R)} = K e^{-5t}$$

$$i(t) = i_p(t) + i_c(t) = -0.2 + t + K e^{-5t}$$

$$i(0) = 0 \rightarrow -0.2 + 0 + K = 0 \rightarrow K = 0.2$$

$$i(t) = -0.2 + t + 0.2 e^{-5t}$$

P 4.45

$$\text{KVL: } L \frac{di(t)}{dt} + i(t)R + v_c(t) = v_s \quad i(t) = C \frac{dv_c(t)}{dt}$$

$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = v_s$$

$$\ddot{v}_c(t) + \frac{R}{L} \dot{v}_c(t) + \frac{1}{LC} v_c(t) = v_s/LC$$

Since v_s is a constant, we will let $v_{cp}(t) = K$

$$\therefore \dot{v}_{cp}(t) = 0 \quad \text{and} \quad \frac{1}{LC} v_{cp}(t) = v_s/LC \rightarrow v_{cp}(t) = v_c = 50V$$

To find $v_{ce}(t)$, we look at the characteristic equation:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{The roots are } s = \frac{R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

$$s_1 = -267.9$$

$$s_2 = -3732$$

$$v_c(t) = 50 + K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$v_c(0) = 0 \rightarrow K_1 + K_2 = -50$$

$$i(0) = 0 \rightarrow \frac{dv_c(t)}{dt} = 0 \rightarrow s_1 K_1 + s_2 K_2 = 0$$

$$K_1 = -53.87 \quad K_2 = 3.867$$

$$v_c(t) = 50 - 53.87 e^{-267.9t} + 3.867 e^{-3732t}$$

P4.51

KVL:

$$\int L \frac{di(t)}{dt} + i(t)R + \frac{1}{C} \int i(t) dt + i_c(0) = 10 \cos(100t)$$

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = -1000 \sin(100t)$$

try $i_p(t) = A \sin 100t + B \cos 100t$

$$\frac{d}{dt} i_p(t) = 100A \cos 100t - 100B \sin 100t$$

$$\frac{d^2}{dt^2} i_p(t) = -10000A \sin 100t - 10000B \cos 100t = -10^3 \sin 100t$$

$$-10^4 A \sin 100t - 10^4 B \cos 100t + 5 \times 10^3 A \cos 100t - 5 \times 10^3 B \sin 100t + 10^4 A \sin 100t + 10^4 B \cos 100t$$

$$(-10^4 A - 5 \times 10^3 B + 10^4 A) \sin 100t + (-10^4 B + 5 \times 10^3 A + 10^4 B) \cos 100t = -10^3 \sin 100t$$

$$-5 \times 10^3 B = -10^4$$

$$5 \times 10^3 A = 0$$

$$B = 0.2$$

$$A = 0$$

$$i_p(t) = 0.2 \cos 100t$$

For the complementary solution:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad s = 25 \pm j96.82$$

$$i_c(t) = K_1 e^{-25t} \cos(96.82t) + K_2 e^{-25t} \sin(96.82t)$$

$$i(t) = 0.2 \cos 100t + K_1 e^{-25t} \cos(96.82t) + K_2 e^{-25t} \sin(96.82t)$$

$$i(0^+) = 0 = 0.2 + K_1 \rightarrow K_1 = -0.2$$

$$\frac{di(0^+)}{dt} = 10 = -25K_1 + 96.82K_2 \rightarrow K_2 = 0.052$$

$$i(t) = 0.2 \cos(100t) - 0.2 e^{-25t} \cos(96.82t) + 0.052 e^{-25t} \sin(96.82t)$$

P5.32

$$Z = \frac{1}{j\omega C + \frac{1}{j\omega L}} = \frac{j\omega L}{1 - \omega^2 LC} = \frac{j\omega 0.1}{1 - \omega^2 10^{-6}}$$

for $\omega = 500 \quad Z = 66.67 \Omega$

for $\omega = 1000 \quad Z = \frac{j100}{1-1} = \infty \Omega$

for $\omega = 2000 \quad Z = -j66.67 \Omega$


P 5.43

$$Z_{eq} = j\omega L + \frac{1}{\frac{1}{R} + j\omega C} = 100j + \frac{1}{10^{-2} + j10^{-2}} = 50 + j50 = 70.7 \angle 45^\circ$$

$$I = \frac{100 \angle 0}{70.7 \angle 45^\circ} = \frac{100 \angle 0}{70.7 \angle 45^\circ} = 1.41 \angle -45^\circ$$

$$I_R = \frac{1/j\omega C}{R + 1/j\omega C} I = \frac{-j100}{100 - j100} 1.41 \angle -45^\circ = 1 \angle -90^\circ$$

$$I_C = \frac{R}{R + 1/j\omega C} I = \frac{100}{100 - j100} 1.41 \angle -45^\circ = 1 \angle 0^\circ$$

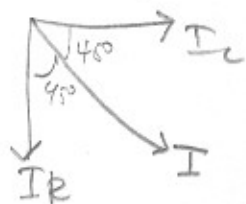P 5.44

$$\text{KVL @ ①} \quad \frac{V_1}{10} + \frac{V_1 - V_2}{5 + j15} = 1 \angle 0^\circ$$

$$\text{KVL @ ②} \quad \frac{V_2}{-j10} + \frac{V_2 - V_1}{5 + j15} = 1 \angle 30^\circ$$

$$\xrightarrow{\text{solve}} \begin{aligned} V_1 &= 6.735 \angle -38.54^\circ \\ V_2 &= 16.25 \angle -55.52^\circ \end{aligned}$$

P 5.46

$$\text{KVL on ①} \quad 5I_1 + j15(I_1 - I_2) - 20 = 0$$

$$\text{KVL on ②} \quad -j10I_2 + (-10) + j15(I_2 - I_1) = 0$$

$$\text{Solving: } \begin{aligned} I_1 &= 1.644 \angle 80.54^\circ \\ I_2 &= 2.977 \angle 74.2^\circ \end{aligned}$$

P 5.47

$$\text{Supermesh: } 5I_1 + j5I_2 + 10I_2 - 10 = 0$$

$$I_1 - I_2 = 2$$

$$\text{Solving: } I_1 = 2, \quad I_2 = 0$$

P6.14

$$v_m(t) = V_m \cos \omega t = V_m \angle 0$$

$$v_{out}(t) = \int V_m \cos \omega t = -\frac{V_m}{\omega} \sin \omega t = -\frac{V_m}{\omega} \cos(\omega t - 90^\circ) = \frac{V_m}{\omega} \angle -90^\circ$$

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{\omega} \angle -90^\circ = \frac{1}{j\omega}$$

P6.21




(a) Voltage Divider:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2 + j\omega L} = \frac{R_2 / (R_1 + R_2)}{1 + j(\omega / \omega_B)}$$

$$\text{where } \omega_B = \frac{R_1 + R_2}{L}, f_B = \frac{R_1 + R_2}{2\pi L}$$

$$(b) f_B = 31.83 \text{ kHz}$$

$$H(0) = 0.5$$

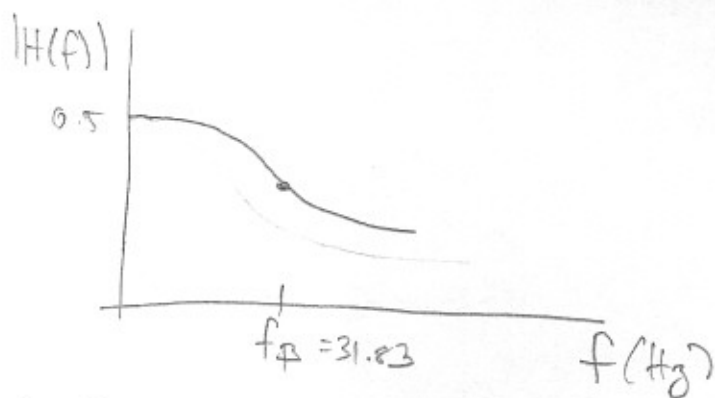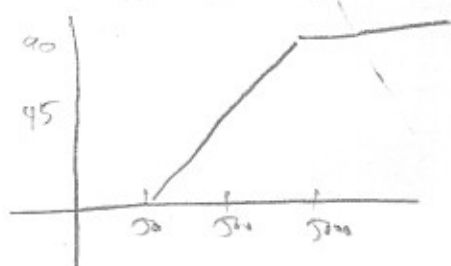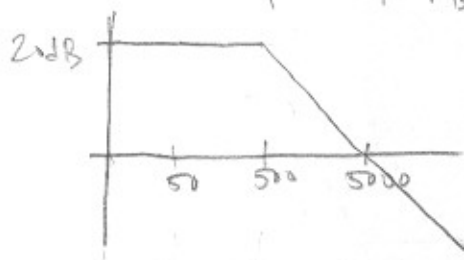
P6.46Lowpass w/ $f_B = 500$ 

* The phase is reversed because of the "-" in the denominator

P6.56 Voltage Divider:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega L}{R + j\omega L} = \frac{j\omega / (R/L)}{1 + j\omega / (R/L)} \quad f_B = \frac{R}{2\pi L} = 1 \text{ MHz}$$

High-pass w/ f_B 1MHz

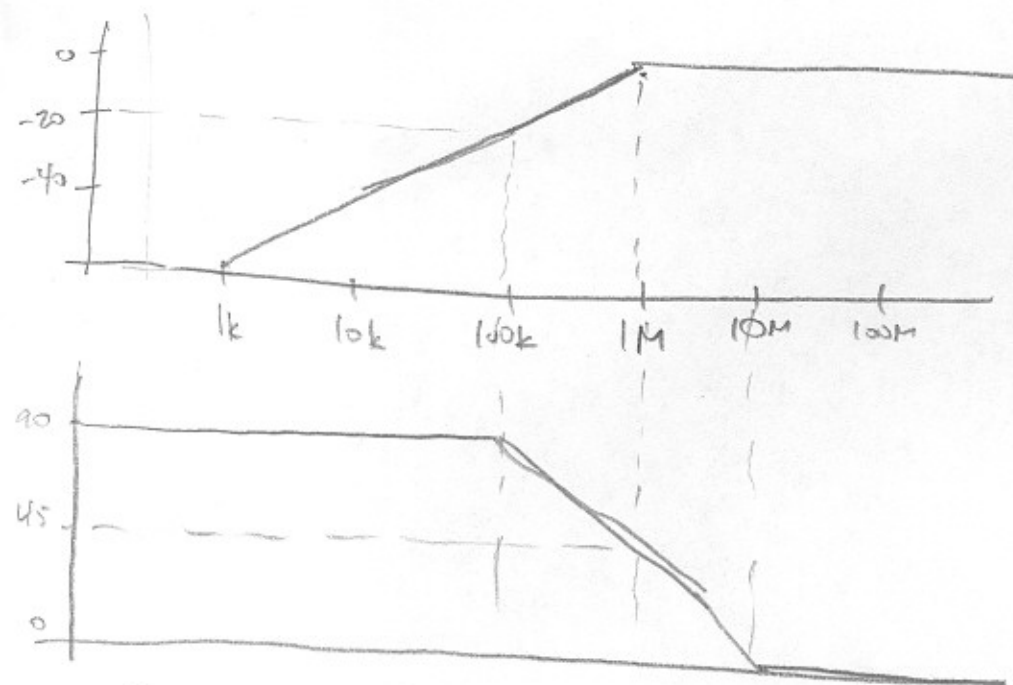

P6.57


Voltage Divider:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{R_2 / (R_1 + R_2)}{1 + \frac{1}{j\omega(R_1 + R_2)C}} = \frac{R_2}{R_1 + R_2} \frac{j\omega / \omega_B}{1 + j\omega / \omega_B}$$

$$\text{HPF } \omega / f_B = \frac{1}{2\pi C(R_1 + R_2)} = 15.92 \text{ Hz}$$

$$\omega_B = \frac{R_1}{C(R_1 + R_2)}$$

$$H(\omega) = \frac{R_2}{R_1 + R_2} = 0.1 = -20 \text{ dB}$$

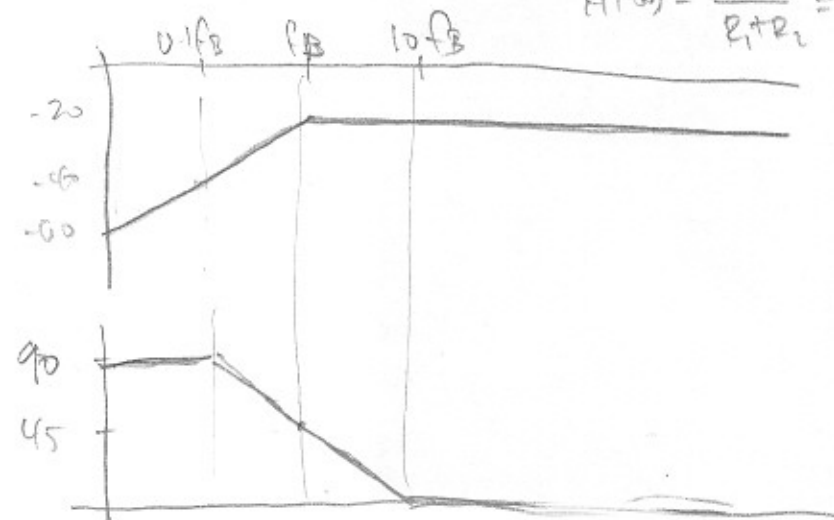

Prob 1

(a) KCL: $C \frac{dv_o(t)}{dt} + \frac{v_o(t)}{R} + \frac{1}{L} \int v_o(t) dt + v_c(0) = -I_s(t)$

Characteristic equation:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$\frac{1}{LC} = \omega_0^2$$

$$C = \frac{1}{L\omega_0^2} = \frac{1}{4 \times 10^{-9} \times 10^{12}} = 250 \mu F$$

$$\frac{1}{RC} = 2\zeta\omega_0$$

$$R = \frac{1}{2C\zeta\omega_0} = \frac{1}{250} = 4 m\Omega$$

(b) $\zeta < 1 \rightarrow$ underdamped

(c) $Z_{in}(\omega) = \frac{1}{j\omega C + \frac{1}{R} + \frac{1}{j\omega L}} = \frac{j\omega L}{1 - \omega^2 LC + j\omega \frac{L}{R}}$

$$Z_{in}(\omega_0) = \frac{j 4 \times 10^{-3}}{1 - 1 + j} = 4 m\Omega$$

(d) $V_o = Z_{in}(\omega_0) A \cos \omega_0 t + Z_{in}(2\omega_0) A \cos(2\omega_0 t) + Z_{in}(\frac{\omega_0}{2}) A \cos(\omega_0 t/2)$

$$= 4 \times 10^{-3} A \cos \omega_0 t + 2.219 \times 10^{-3} A \cos(2\omega_0 t - 56.3^\circ)$$

$$+ 2.219 \times 10^{-3} A \cos(\frac{\omega_0}{2} t + 56.3^\circ)$$

Prob 2

KCL: $\frac{V_{DD} - v_c(t)}{R_L} = C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{R_{upres}}$

$$C \dot{v}_c + \left(\frac{1}{R_{up}} + \frac{1}{R_L} \right) v_c = \frac{V_{DD}}{R_L}$$

$$10 \times 10^{-6} \dot{v}_c + 1.1 \times 10^{-3} v_c = 5 \times 10^{-4}$$


$$v_{cp} = \frac{5 \times 10^{-4}}{1.1 \times 10^{-3}} = 0.4545$$

$$v_{cc} = K e^{-t/9.1 \times 10^{-3}}$$

$$v_c(0) = V_{DD} = 5V = 0.4545 + K e^{-t/9.1 \times 10^{-3}}$$

$$K = 5 - 0.4545 = 4.545$$


$$v_c(t) = 0.4545 + 4.545 e^{-t/9.1 \times 10^{-3}}$$

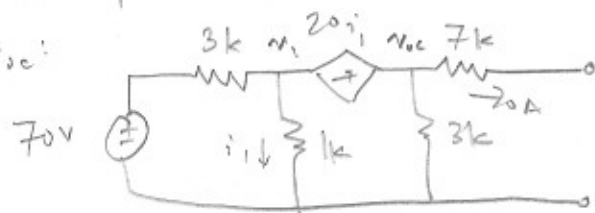V_{oc} :

$$\text{KCL @ } v_1: \frac{v_1 - 70}{3k} + \frac{v_1}{1k} + \frac{20v_1}{1k} = 0 \rightarrow 21.33 \times 10^{-3} v_1 + 23.33 \times 10^{-3} = 0$$

$$v_1 = 1.094 \text{ V}$$

$$\text{KCL @ } v_{oc}: \frac{20v_1}{1k} = \frac{v_{oc}}{3k} \rightarrow v_{oc} = 60v_1 = \boxed{65.63 \text{ V}}$$

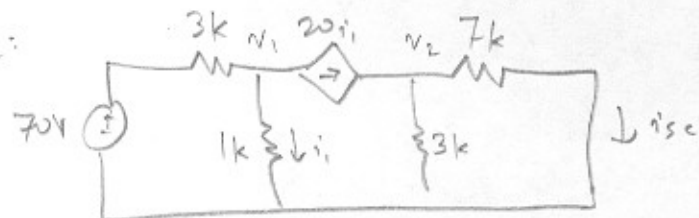 i_{sc} :

$$v_1 = 1.094 \text{ V as before}$$

$$\text{KCL @ } v_2: \frac{20v_1}{1k} = \frac{v_2}{7k \parallel 3k} \rightarrow v_2 = 42v_1 = 45.94 \text{ V}$$

$$i_{sc} = \frac{v_2}{7k} = \boxed{6.563 \text{ mA}}$$

$$R_{eq} = \frac{v_{oc}}{i_{sc}} = 10 \text{ k}\Omega$$

