

P4.49

$$\text{KCL: } \frac{v(t)}{R} + \frac{1}{L} \int v(t) dt + i_L(0) + C \frac{dv(t)}{dt} = 1A$$

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-5} \cdot 10^{-9}}} = 10^7 = 10 \text{ MHz}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 50 \cdot 10^{-9}} = 10^7$$

$$\zeta = \frac{\alpha}{\omega_0} = \frac{10^7}{10^7} = 1$$

(b) Evaluating our KCL eqn @ $t=0^+$:

$$\frac{0}{R} + \frac{1}{L} \int_0^0 v(t) dt + 0 + C v'(0^+) = 1$$

$$v'(0^+) = \frac{1}{C} = 10^9 \text{ V/s}$$

(c) At steady state ($t \rightarrow \infty$), the inductor acts as a short so the particular solution is $v(t) = 0$

(d) Critically damped $\rightarrow v(t) = k_1 e^{\omega_0 t} + k_2 t e^{\omega_0 t}$

$$\text{I.C.: } v(0) = 0 \rightarrow k_1 + 0 = 0 \rightarrow k_1 = 0$$

$$v'(0^+) = 10^9 \rightarrow k_1 \omega_0 + k_2 + 0 = 10^9 \rightarrow k_2 = 10^9$$

$$v(t) = 10^9 t e^{-10^7 t}$$

P 4.35

$$\frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t) dt + i_L(0) = 5 \cos 10t$$

$$\frac{L}{R} \frac{d}{dt} v(t) + v(t) = -50 \sin 10t$$

$$\text{try } v_p(t) = A \cos 10t + B \sin 10t$$

$$\frac{d}{dt} v_p(t) = -A \sin 10t + B \cos 10t$$

$$\frac{1}{R} (-A \sin 10t + B \cos 10t) + A \cos 10t + B \sin 10t = -50 \sin 10t$$

$$(A + \frac{10BL}{R}) \cos 10t + (B - \frac{10AL}{R}) \sin 10t = -50 \sin 10t$$

$$A + \frac{10BL}{R} = 0$$

$$B - \frac{10AL}{R} = -50$$

$$\rightarrow A = 25 \quad B = -25 \quad \rightarrow v_p(t) = 25 \cos 10t - 25 \sin 10t$$

$$\tau = \frac{L}{R} = 0.1s$$

$$v_c(t) = K e^{-t/\tau}$$

$$v(t) = 25 \cos 10t - 25 \sin 10t + K e^{-t/\tau}$$

@ $t=0^+$ \rightarrow inductor acts as open circuit

$$\therefore v(0^+) = i(0^+) R = 5A \cdot 10\Omega = 50V$$

$$v(0^+) = 25 - 0 + K = 50 \rightarrow K = 25$$

$$\therefore v(t) = 25 \cos 10t - 25 \sin 10t + 25 e^{-t/\tau} \quad \text{for } t > 0$$

P 6.59

The transfer function is $\frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$

$$V_{out} = H(200\pi) 5 \cos(200\pi t) + H(2000\pi) 5 \cos(2000\pi t)$$

$$= 0.4975 \cos(200\pi t + 84.29^\circ) + 3.536 \cos(2000\pi t + 45^\circ)$$

EE40 HW4 soln p.3
PG 81

$$(a) H(f) = \frac{j\omega L + \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C} + R} = \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega RC} = \frac{1 - 4\pi^2 f LC}{1 - 4\pi^2 f LC + j2\pi f RC}$$

(b) MATLAB code would be something like:

$$R=10;$$

$$L=0.01;$$

$$C=2.533e-8;$$

$$\log f = 3:0.01:5; \quad \% \text{ log frequencies}$$

$$f = 10.^{\log f}$$

$$\omega = 2 * \pi * f;$$

$$H = (1 - \omega.*\omega*L*C)./(1 - \omega.*\omega*L*C + j*\omega*R*C);$$

$$\text{semilogx}(f, 20 * \log_{10}(\text{abs}(H)))$$

(The plot will be a notch filter with the notch at 10^4 Hz and an attenuation of ≈ 65 dB.)

(c) At low frequencies, the capacitor acts like an open circuit so there is no current making

$$V_{out} \approx V_{in} \quad \text{or} \quad H(f) \approx 1$$

(d) At high frequencies, the inductor acts like an open circuit making $V_{out} \approx V_{in}$ or $H(f) \approx 1$

P14.17

$$(a) v_- = v_+ = 0 \quad \text{bc of negative feedback} \quad i_R = 2\text{mA by KCL @ } (i_- = 0)$$

$$v_- - v_o = (2\text{mA})(1\text{k}\Omega) \quad \text{by Ohm's Law}$$

$$\therefore v_o = -2\text{V}$$


$$(b) v_- = v_+ = 5\text{V} \quad i_R = 2\text{mA by KCL @ } (i_- = 0)$$

$$v_- - v_o = (2\text{mA})(3\text{k}\Omega)$$

$$\therefore v_o = 5\text{V} - 6\text{V} = -1\text{V}$$

EEEN HW 4 Soln p 4

P 14.17 (cont'd)

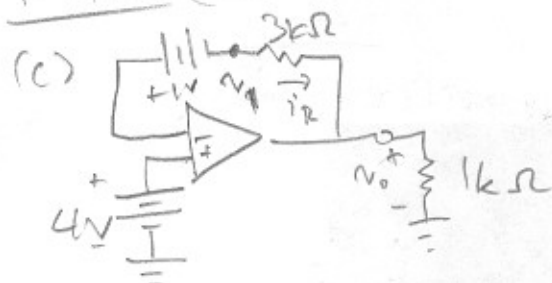

$$v_- = v_+ = 4V$$


$$v_1 = v_- - 1V = 3V$$

$$\text{Since } i_L = 0, i_R = 0 \rightarrow v_1 = v_2 = 3V$$

(d) $i_- = 0 \rightarrow i_R = 0$
 $v_- = v_+ = 0V$ } $\rightarrow v_o = v_+ = 0V$

(e) $v_- = v_+ = 5V$
 $v_o = v_- - 2V = 3V$

P 14.18

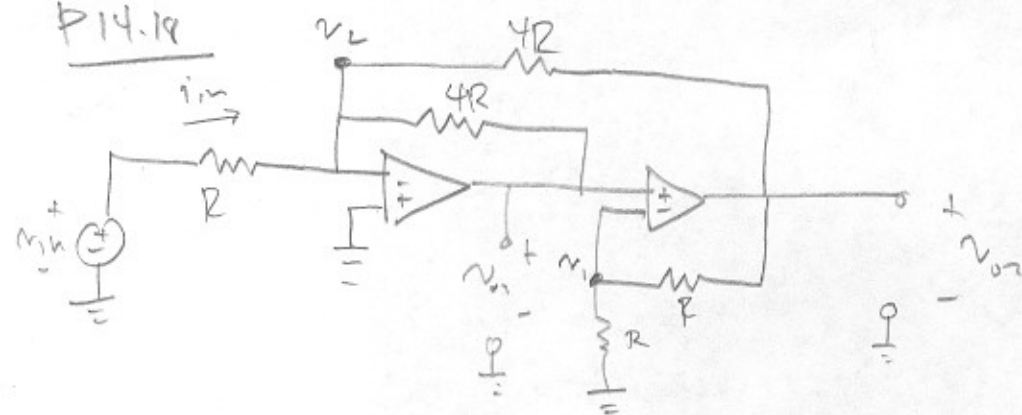

$$v_{o1} = v_1 \text{ (by neg feedback on OP-AMP 2)}$$

$$v_1 = v_{o2} / 2 \text{ (by voltage divider)}$$

$$\rightarrow v_{o2} = 2v_{o1}$$

$$v_2 = 0V \text{ (by neg feedback on OP-AMP 1)}$$


$$i_{in} + \frac{v_{o1}}{4R} + \frac{v_{o2}}{4R} = 0 \text{ (KCL @ 2)}$$

$$i_{in} = \frac{v_{in}}{R} \text{ (ohm's)}$$

$$\therefore \frac{v_{in}}{R} = -\frac{3v_{o1}}{4R} \rightarrow \frac{v_{o1}}{v_{in}} = -\frac{4}{3} \quad \frac{v_{o2}}{v_{in}} = 2\left(-\frac{4}{3}\right) = -\frac{8}{3}$$

$$A_1 = -\frac{4}{3} \quad A_2 = -\frac{8}{3}$$


EE40 HW 4 soln. p. 5
P14.24
(c)

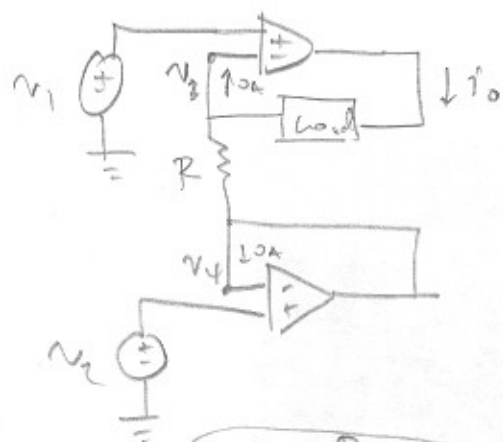

$$v_3 = v_1 \quad v_4 = v_2$$

$$i_o = \frac{v_3 - v_4}{R} = \boxed{\frac{v_1 - v_2}{R}}$$

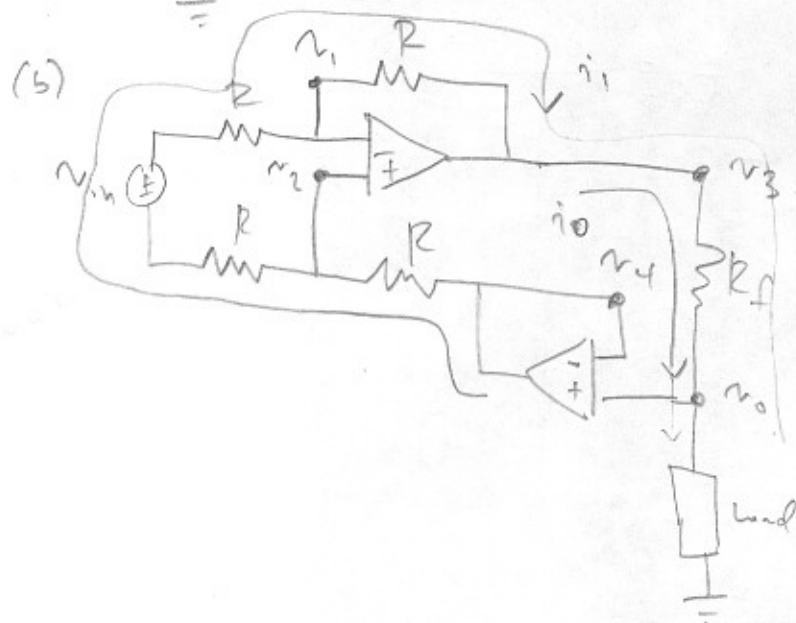Since i_o does not depend on R_L , the output impedance is ∞ .



KVL from v_2 to v_1

$$v_2 - i_1 R + v_{in} - i_1 R = v_1$$

$$\text{But } v_1 = v_2 \rightarrow i_1 = \frac{v_{in} R}{2R}$$

KVL from v_4 to v_3

$$v_4 - i_1 R + v_{in} + R_f i_o = v_3$$


$$\text{But } v_4 = v_3 \rightarrow v_{in} = 4i_1 R - i_o R_f$$

$$= 2v_{in} - i_o R_f$$

$$\rightarrow i_o = -\frac{v_{in}}{R_f}$$

Again i_o is indep of R_L so output impedance is ∞ .

P14.26

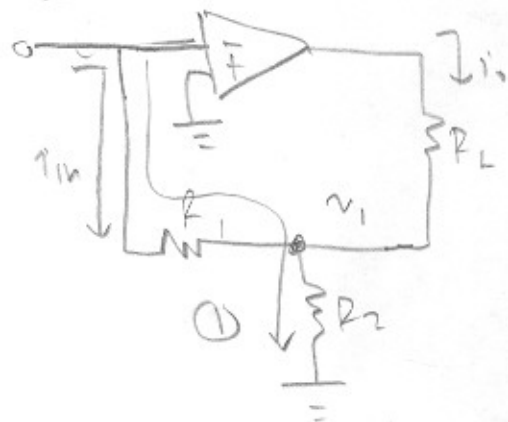

KVL on path ①:


$$0V - i_{in} R_1 - (i_{in} + i_o) R_2 = 0V$$

$$\rightarrow i_o = \frac{-i_{in} (R_1 + R_2)}{R_2} = \boxed{-\frac{(R_1 + R_2)}{R_2} i_{in}}$$

i_o is indep. of R_L so output impedance is infinite

(a) inverting amp: $\frac{v_o}{v_i} = -\frac{R_2}{R_1} = -10$, ideally

With this model:

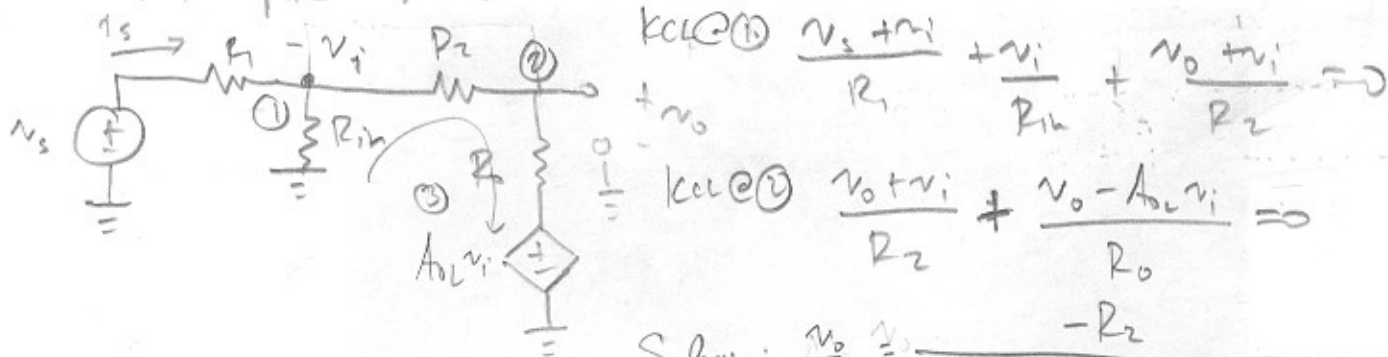

Solving: $\frac{v_o}{v_s} = \frac{-R_2}{R_1 \left[1 + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in}} \right) \frac{R_2 R_2 + R_2^2}{A_{OL} R_2 - R_o} \right]}$

$= -9.9989$

(b) $Z_i = \frac{v_s}{i_s} = R_1 = 1 \text{ k}\Omega$ ideally


With this model

Ohm's: $v_s = R_1 i_s - v_i$

KVL @ ③: $v_i + (R_2 + R_o) \left(\frac{v_i}{R_{in}} + i_s \right) + A_{OL} v_i = 0$

Solving: $Z_{in} = \frac{v_s}{i_s} = R_1 + \frac{R_2 + R_o}{1 + A_{OL} + (R_2 + R_o)/R_{in}} = 1.0001 \text{ k}\Omega$

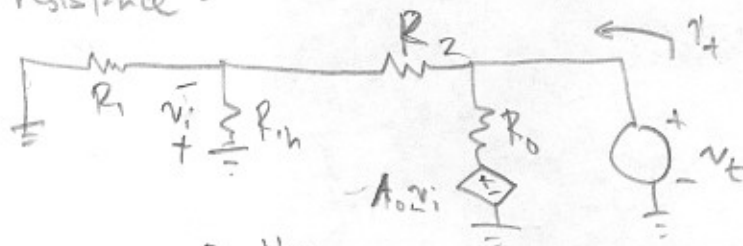(c) finding output impedance is just like finding Thevenin resistance:




$v_i = -\frac{R_{in} \parallel R_1}{R_2 + R_{in} \parallel R_1} v_t$ (voltage divider)

$i_t = \frac{v_t}{R_2 + R_{in} \parallel R_1} + \frac{v_t - A_{OL} v_i}{R_o}$ (KCL)

$Z_o = \frac{v_t}{i_t} = \frac{1}{\frac{1}{R_2 + R_{in} \parallel R_1} + \frac{1}{R_o} + \frac{A_{OL}(R_{in} \parallel R_1)}{R_o(R_2 + R_{in} \parallel R_1)}} = 2.75 \text{ m}\Omega$

EE40 HW 4 soln p.7

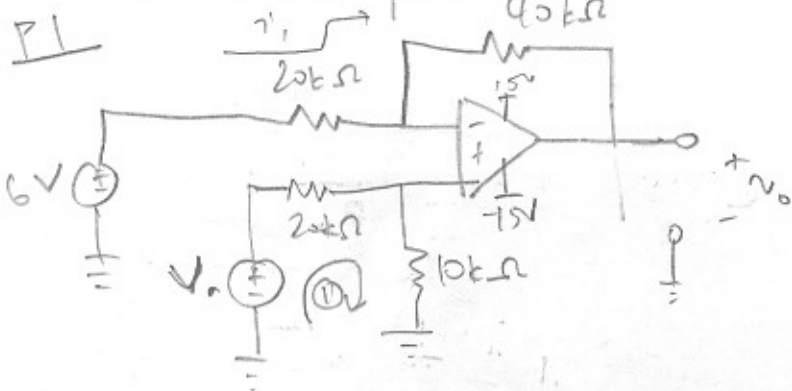

$$v_+ = \frac{v_a}{3} \text{ (by KVL on ① - voltage divider)}$$

$$v_- = v_+$$

$$i_1 = \frac{6V - v_-}{20k} = \text{(ohm's law)}$$

$$v_o - v_- = -i_1(40k) = 12V - \frac{2}{3}v_a$$

$$\frac{v_o}{v_a} = -\frac{2}{3} \text{ (w/ 12V offset)}$$


P2

$$\frac{v_{in}}{j\omega L + R} + v_o j\omega C + \frac{v_o}{2R} = 0$$


$$\frac{v_o}{v_{in}} = \frac{(-1)}{(R + j\omega L)(\frac{1}{2R} + j\omega C)} = \frac{-\frac{1}{R} 2R}{(1 + j\omega L/R)(1 + j\omega 2RC)}$$

$$= \frac{-2}{(1 + j\omega/(R/L))(1 + j\omega/(1/2RC))}$$
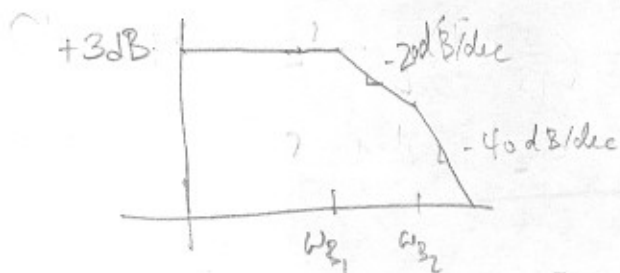
$$\text{let } \omega_{B1} = \frac{R}{L} \quad \omega_{B2} = \frac{1}{2RC}$$






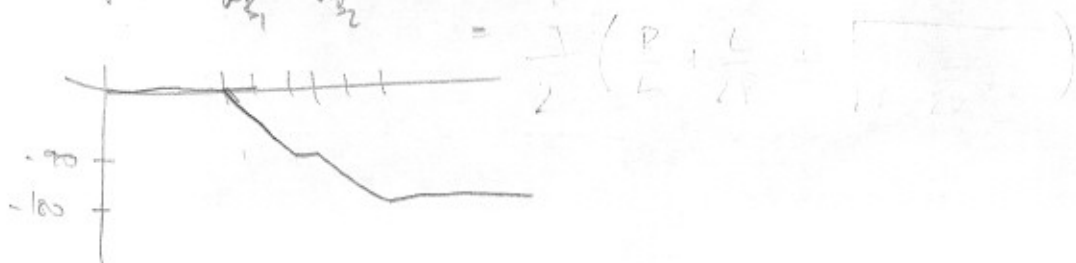Bode plots vary depending on how close ω_B 's are...



P3 $\frac{v_{in}}{j\omega} = \frac{v_o}{R+j\omega L} \rightarrow \frac{v_o}{v_{in}} = \frac{R+j\omega L}{j\omega} = \frac{1}{L} \frac{1+j\omega L/R}{j\omega}$

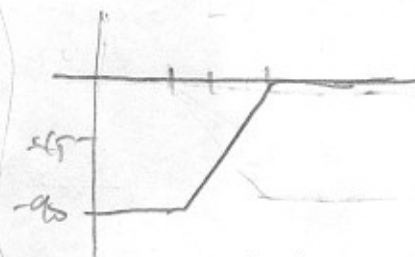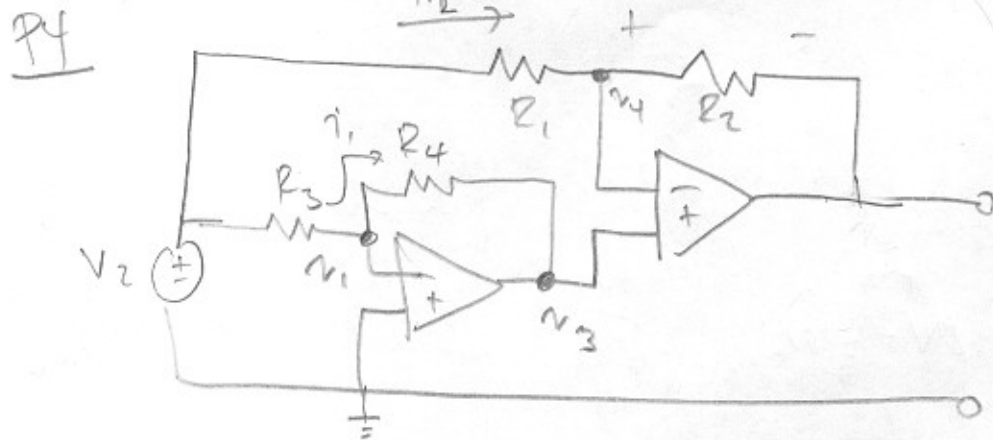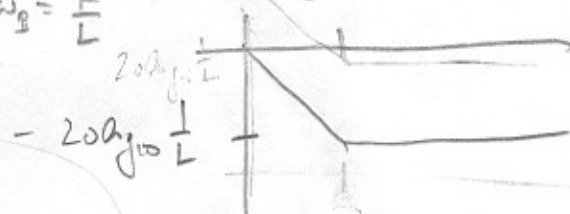$= \frac{1}{L} \left(\frac{j\omega/(R/L)}{1+j\omega/(R/L)} \right) \leftarrow \text{HPF w/ } \omega_B = \frac{R}{L}$



note $\log \frac{1}{x} = -\log x$
 so we just
 invert the transfer
 function

$$\left. \begin{array}{l} v_1 = 0 \\ i_1 = \frac{v_2}{R_3} \end{array} \right\} \rightarrow v_3 = -\frac{R_4}{R_3} v_2$$


$$v_4 = v_3 = -\frac{R_4}{R_3} v_2$$

$$i_2 = \frac{v_2 - v_4}{R_1} = v_2 \left(\frac{1 + \frac{R_4}{R_3}}{R_1} \right)$$

$$v_o = i_2 R_2 = \frac{R_2}{R_1} \left(1 + \frac{R_4}{R_3} \right) v_2$$

EE40 HW1 soln p9.

P5

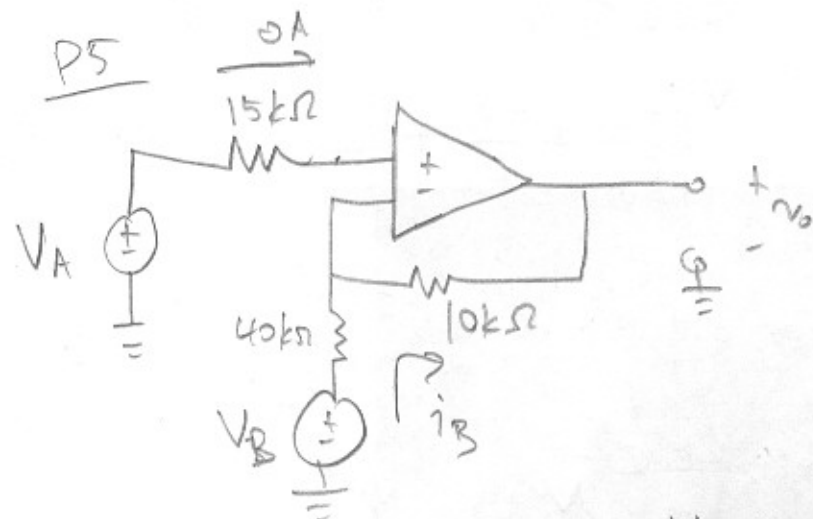


$$v_- = v_+ = V_A \rightarrow i_B = \frac{V_B - V_A}{40k\Omega}$$

$$v_o = V_A - i_B 10k\Omega$$

$$= \frac{5V_A - 3V_B}{4}$$

P6

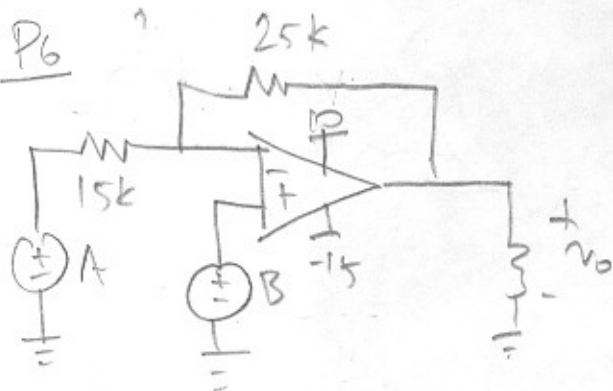

By KCL @ (-)

$$\frac{A - B}{15k} = \frac{B - v_o}{25k}$$

$$@ V_o = 10V \rightarrow A = \frac{8}{5} B - 6V$$


$$@ V_o = -15V \rightarrow A = \frac{8}{5} B + 9V$$

$$\text{if } A = 2B \rightarrow 2B = \frac{8}{5} B - 6V \rightarrow B = -15V$$

$$2B = \frac{8}{5} B + 9V \rightarrow B = 22.5V$$

Ex 4.14 p 10

P7 Voc:

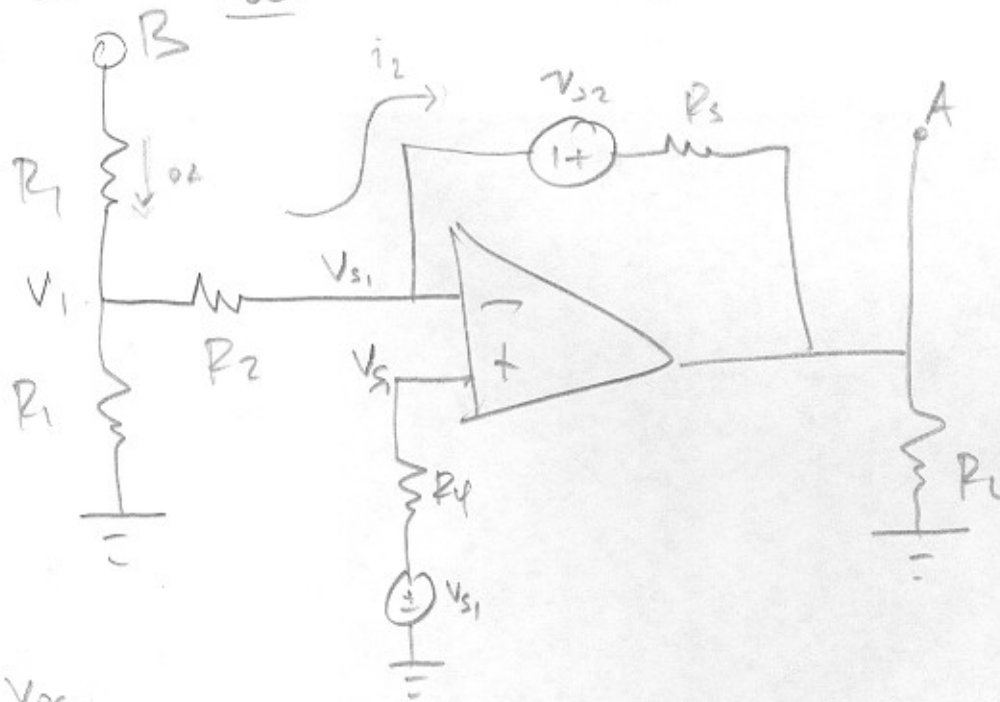

Voc:

$$V_{AB} = V_{S1} + V_{S2} - i_2 R_3$$

$$i_2 = -\frac{V_{S1}}{R_1 + R_2}$$

$$V_{oc} = V_{S1} + V_{S2} + \frac{V_{S1} R_3}{R_1 + R_2} = \left(\frac{R_1 + R_2 + R_3}{R_1 + R_2} \right) V_{S1} + V_{S2} = V_{th}$$


Ex 10 HW4 soln p11

P7 (cont'd)

R_{eq} : (zero sources apply v_t)

KCL @ v_1
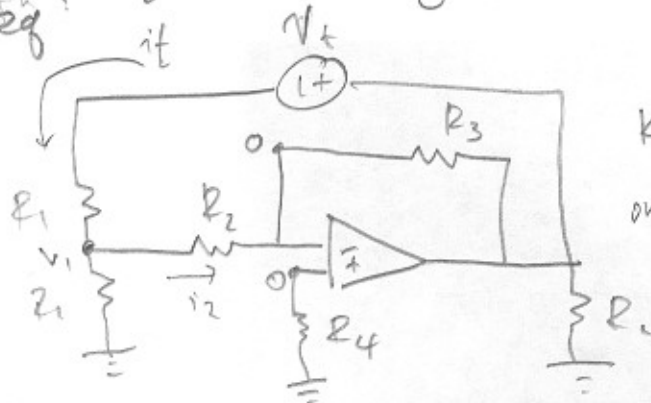
$$i_t = \frac{v_1}{R_1} + \frac{v_1}{R_2} \rightarrow v_1 = \frac{i_t (R_1 + R_2)}{R_1 R_2}$$



KVL:

$$v_t - i_t R_1 + i_2 (R_2 + R_3) = 0$$

Ohm's:

$$i_2 = \frac{v_1}{R_2}$$

Substituting:

$$v_t - i_t R_1 + \frac{i_t (R_1 + R_2) (R_2 + R_3)}{R_1 R_2} = 0$$

$$\rightarrow R_{eq} = \frac{v_t}{i_t} = R_1 - \frac{(R_1 + R_2) (R_2 + R_3)}{R_1 R_2}$$

