

University of California
College of Engineering
Department of Electrical Engineering
and Computer Sciences

Octavian Florescu

Problem Set 5
Due Tuesday August 1st

EE40
Summer 2006

Reading:

Chap 10-10.4 of Hambley.
Chap 2, 3.3-3.6 of Sodini and Howe.


Problems:

Chap 10: 10.11, 10.13, 10.16, 10.21, 10.33, 10.34, 10.35
Chap 2: E2.4, E2.10, E2.11, P2.2, P2.5, P2.7, 2.10

Additional Problems:

Problem 1


- a. Explain in your own words how forward biasing a diode generates a current.
- b. Explain in your own words how a reverse biasing a diode generates a current.
- c. Find the majority and minority carriers in this device.
- d. Draw the charge density, the electric field and the built-in potential of this device.
- e. Find the junction capacitance if the thickness of this diode is 1 μm .

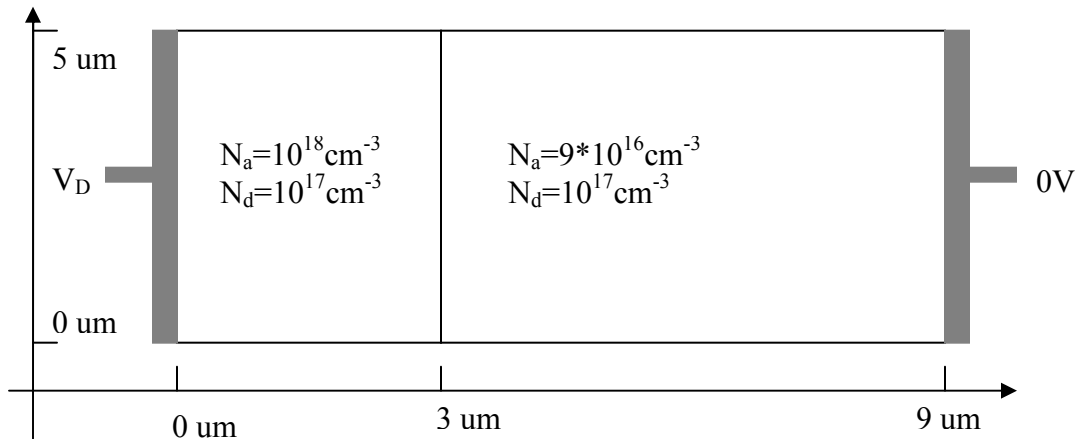

Problem 2

Consider the P region resistor below. The n substrate concentration is 10^{17} cm^{-3} . A P -region is implanted on top of the n background, with an acceptor concentration of $1.1 \times 10^{17} \text{ cm}^{-3}$. Assume $n_i = 10^{10} \text{ cm}^{-3}$.



- Find the majority carrier concentration for the n and p regions.
- Find the sheet resistance between the metal contacts. Use the mobility plot in your notes.
- Design a $1 \text{ K}\Omega$ resistor using the above manufacturing process. Show a top view of your resistor, and specify how many squares of the previous sheet resistance are required for your resistor.
- For what values of voltages on the metallic contacts would this device stop working like a P region resistor? Assume the n -Si is biased to 2V .

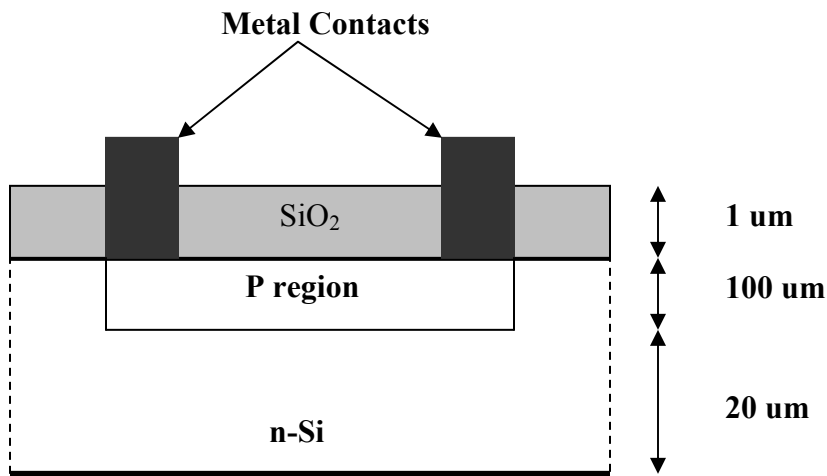

Problem 3


Consider the n-type silicon substrate below. The n background concentration is 10^{17} cm^{-3} . A P region is implanted on top of the n background, with an acceptor concentration of $1.1 \times 10^{17} \text{ cm}^{-3}$. A P^+ region is implanted on top of the P region with acceptors with the concentration of 10^{18} cm^{-3} . Assume $n_i = 10^{10} \text{ cm}^{-3}$.

- Find the majority carrier concentration for the n , p and p^+ regions.
- Find the sheet resistance for the P^+ region.
- Find the sheet resistance for the P region.
- What is the total sheet resistance?

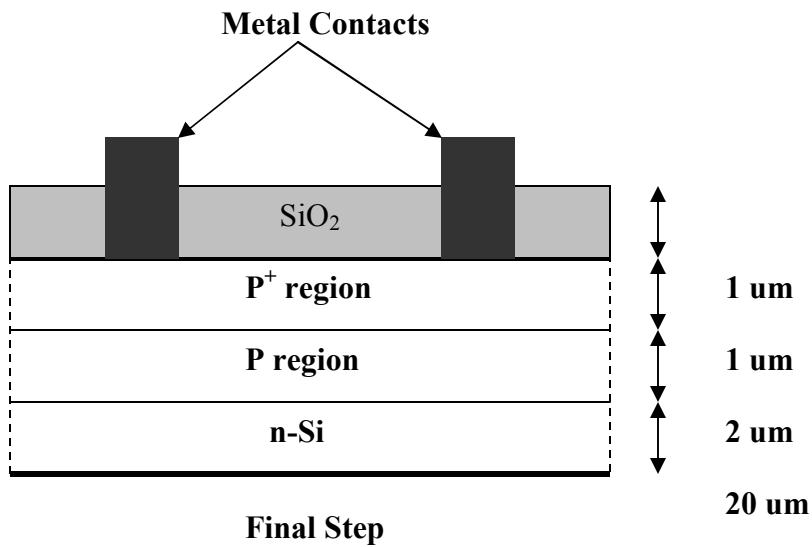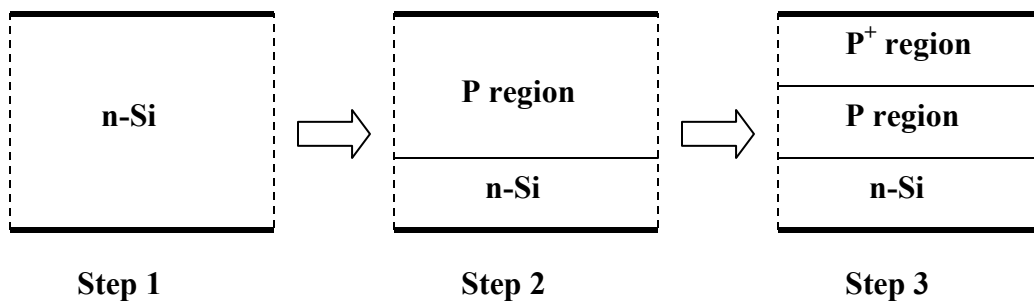


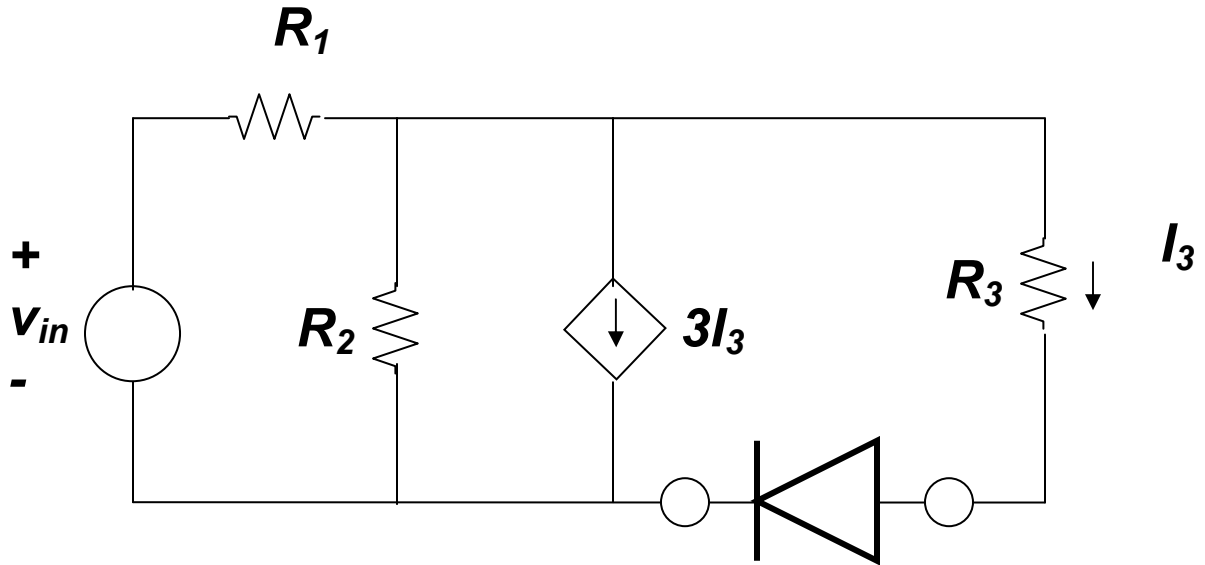Problem 4


$R_1 = 2K\Omega$, $R_2 = 2K\Omega$, $R_3 = 4K\Omega$, and $V_{in} = 4V$



- Draw the Thevenin equivalent circuit that the diode sees (i.e. the Thevenin equivalent for the two terminals of the diode).
- Specify the Thevenin voltage and Thevenin Resistance.
- Given the I-V characteristic shown below, find the Q points V_{diode} and I_{diode} .

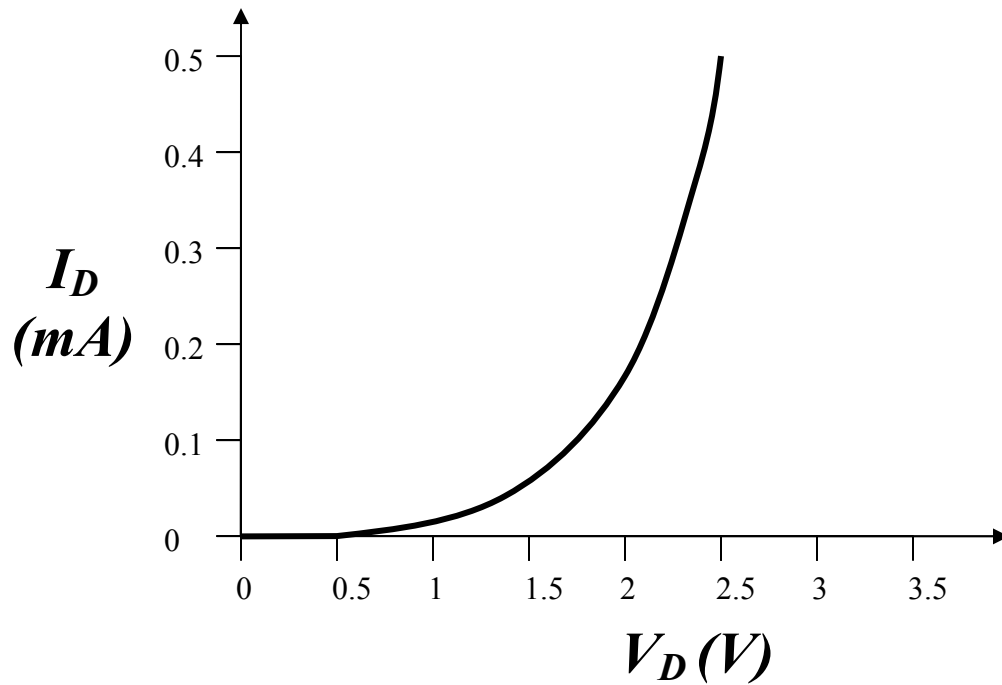


Problem 5

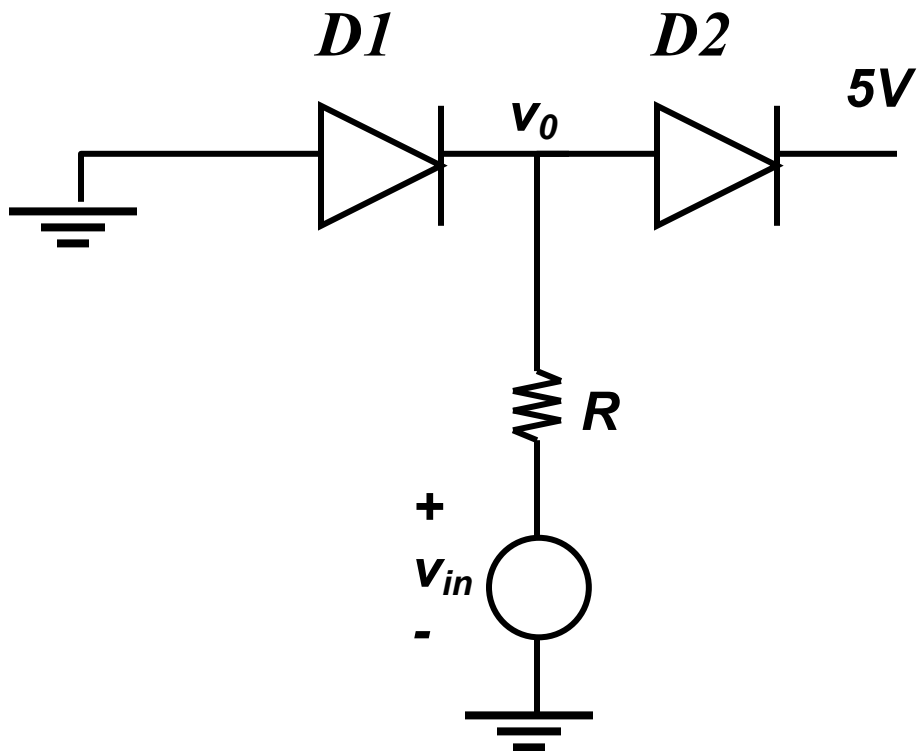

- a. $D1$ and $D2$ have built-in potential voltages of 0.7 Volts. Use the Ideal model for $D1$ and $D2$ to plot V_o vs. V_{in} . *Hint: Try some sample voltages.*

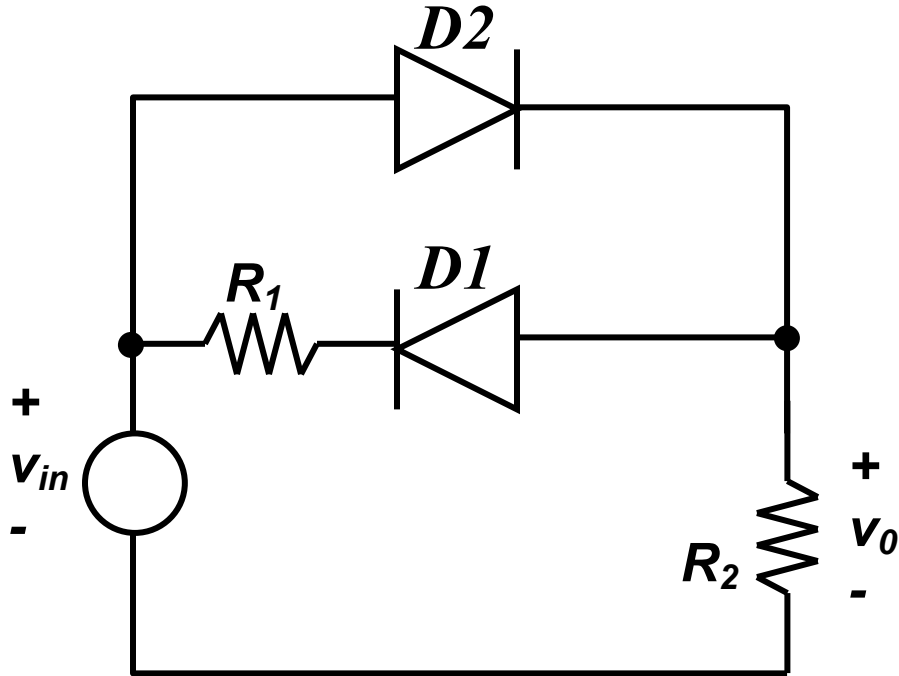Problem 6

Diodes D_1 and D_2 are p-n junctions with $N_A = 10^{18} \text{ cm}^{-3}$ and $N_D = 1.5 \times 10^{17} \text{ cm}^{-3}$ at room temperature. Assume $n_i(T) = 10^{10} \text{ cm}^{-3}$



- What is the built in potential of the diodes?
- If $R_1 = 5 \text{ K}\Omega$ and $R_2 = 10 \text{ K}\Omega$, plot V_o versus V_{in} . Use the large signal model for the diodes.