

test to HW 5 p1.

10.11

$$i_D = I_s [e^{v_D/nV_T} - 1]$$

$$\rightarrow I_s = \frac{i_D}{e^{v_D/nV_T} - 1} = \frac{0.2 \times 10^{-3}}{e^{0.6/(2 \times 0.026)} - 1} = 1.950 \times 10^{-9} \text{ A}$$

for $v_D = 0.65 \text{ V}$

$$i_D = 1.950 \times 10^{-9} [e^{0.65/(2 \times 0.026)} - 1] = \boxed{0.532 \text{ mA}}$$

for $v_D = 0.70 \text{ V}$

$$i_D = 1.950 \times 10^{-9} [e^{0.70/(2 \times 0.026)} - 1] = \boxed{1.369 \text{ mA}}$$

10.13

When the switch is open:

$$I_s = \frac{i_{D1}}{e^{v/nV_T} - 1} = \frac{10^{-3}}{e^{0.6/0.026} - 1} = 9.502 \times 10^{-14} \text{ A}$$

When the switch is closed

$$i_{D1} = i_{D2} = 0.5 \text{ mA}$$

$$v = nV_T \ln \left[\frac{i_D}{I_s} + 1 \right] = 0.026 \ln \left[\frac{0.5 \times 10^{-3}}{9.502 \times 10^{-14}} + 1 \right] = \boxed{582.0 \text{ mV}}$$

For $n=2$


$$I_s = \frac{10^{-3}}{e^{0.6/(2 \times 0.026)} - 1} = 9.748 \times 10^{-9} \text{ A}$$

$$v = 2 \times 0.026 \ln \left[\frac{0.5 \times 10^{-3}}{9.748 \times 10^{-9}} + 1 \right] = \boxed{1.163 \text{ V}}$$

10.16

Load line: $i_x = \frac{V_s}{R_s} - \frac{1}{R_s} v_x = 2 - \frac{1}{3} v_x$


Diode: $i_x = \frac{1}{8} v_x^2$

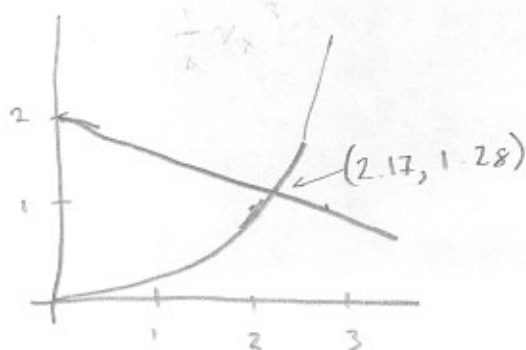


$$\boxed{i_x = 1.28 \text{ A}} \\ \boxed{v_x = 2.17 \text{ V}}$$

10.21

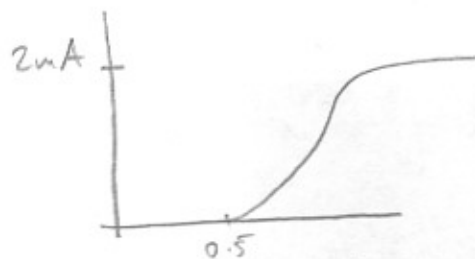(a) $v_a(i_a) = v(i_a) + v_x(i_a)$ (series \rightarrow same current, voltage adds)




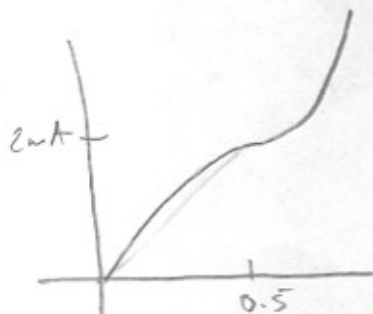(b) $i_b(v_b) = i(v_b) + i_x(v_b)$ (parallel \rightarrow same voltage, add current)



10.33


(a) D_1 on D_2 off

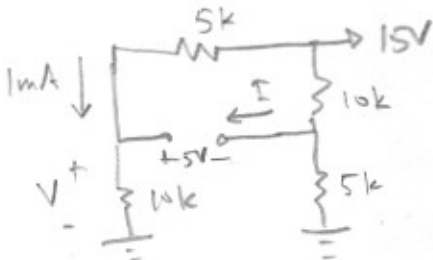

$$V = \frac{10}{10+5} 15 = 10V$$

$$I = 0A$$


(b) D_1 on D_2 off

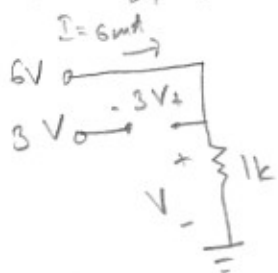

$$V = \frac{6mA}{1k} = 6V$$

$$I = \frac{6V}{1k} = 6mA$$

(c) Both on

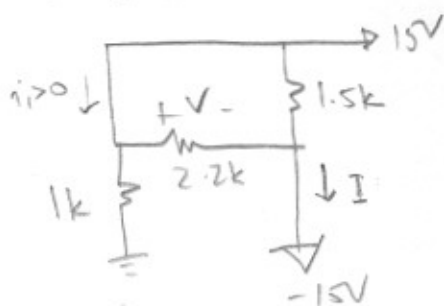


$$V = 30V$$

$$I = \frac{30V}{1.5k \parallel 2.2k} = 33.6mA$$

10.34


(a) on/on/off

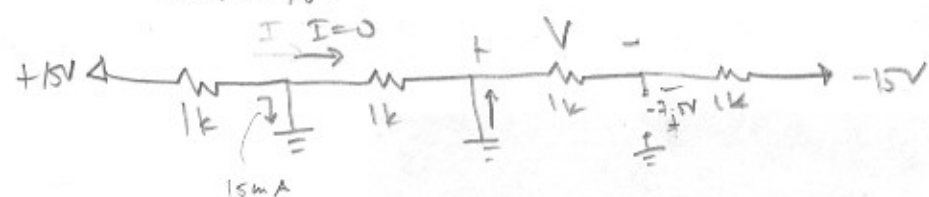

$$V = \frac{1}{2}(-15V) = \boxed{7.5V}$$

$$I = \frac{0V - 0V}{1k} = \boxed{0A}$$

(s)	V_{in}	D_1	D_2	D_3	D_4	V	I
	0	on	on	on	on	0	0
	2	on	on	on	on	2V	2mA
	6	off	on	on	off	5V	5mA
	10	off	on	on	off	5V	5mA

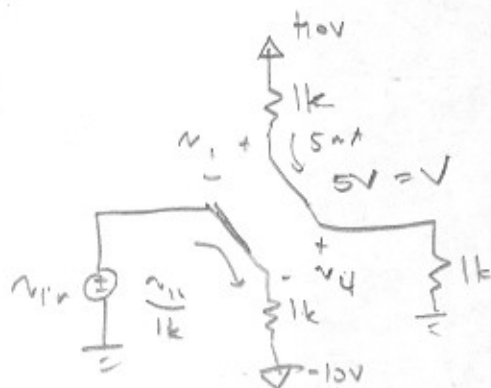


Need $V_1 < 0 \rightarrow V_{in} > 5V$

$$i_3 = \frac{V_{in}}{1k} > 0 \rightarrow V_{in} > 0$$

$$V_4 < 0 \rightarrow V_{in} > 5V$$


So for $V_{in} > 5V$ $V = 5V$

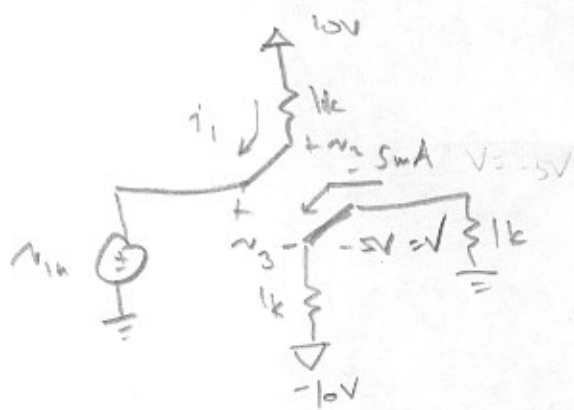

Need $V_1 > 0 \rightarrow V_{in} < 10V$

$$V_2 = V_3 < 0 \rightarrow V_{in} < -5V$$

So for $V_{in} < -5V$ $V = -5V$

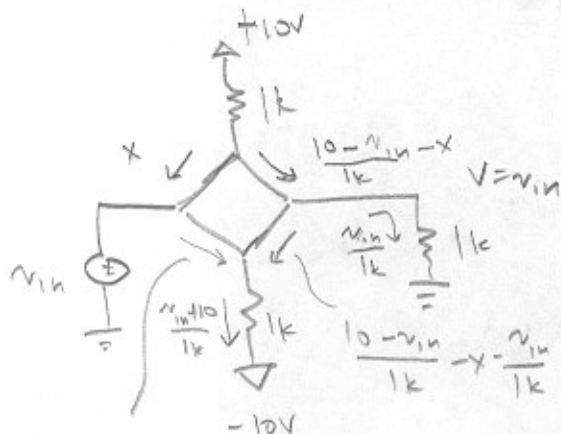

Need $x > 0$ (i)

$$\frac{10 - V_{in} - x}{1k} > 0 \rightarrow V_{in} < 10 - x \quad (ii)$$

$$\frac{V_{in} + 10}{1k} - \left(\frac{10 - V_{in} - x}{1k} - \frac{V_{in}}{1k} \right) > 0 \rightarrow x \geq \frac{V_{in}}{1k} \quad (iii)$$

$$\frac{10 - V_{in}}{1k} - x - \frac{V_{in}}{1k} > 0 \rightarrow x < \frac{10 - 2V_{in}}{1k} \quad (iv)$$

$$\frac{V_{in} + 10}{1k} - \left(\frac{10 - V_{in}}{1k} - x - \frac{V_{in}}{1k} \right)$$

By transitivity:


$$(i, ii) \quad 0 < 10 - v_{in} \rightarrow v_{in} < 10$$

$$(i, iv) \quad 0 < 10 - 2v_{in} \rightarrow v_{in} < 5$$

$$(iii, iv) \quad -3v_{in} < 10 - 2v_{in} \rightarrow v_{in} > -10$$


$$(ii, iii) \quad -3v_{in} < 10 - v_{in} \rightarrow v_{in} > -5$$
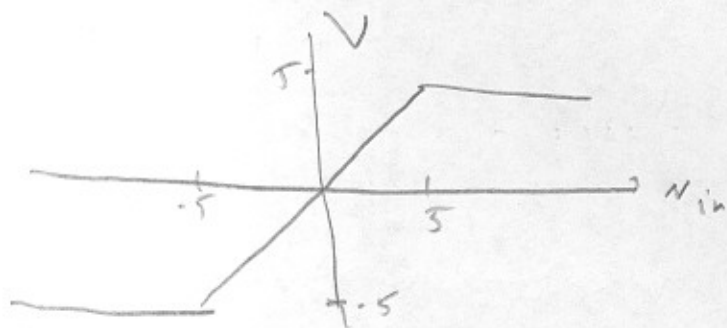
$$\text{So } V = v_{in} \text{ for } -5 < v_{in} < 5$$




10.35

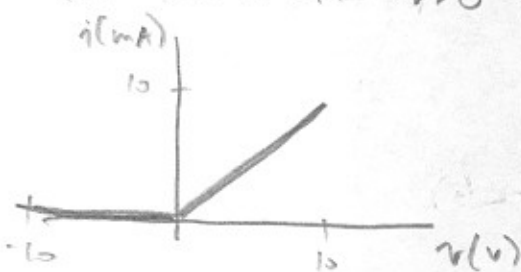
(a) $v < 0 \rightarrow \text{off}$ $v > 0 \rightarrow \text{on}$



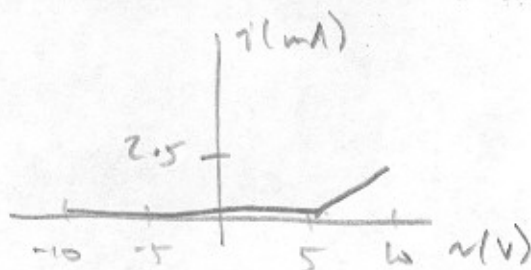
(b) $v > 5 \rightarrow \text{on}$ $v < 5 \rightarrow \text{off}$



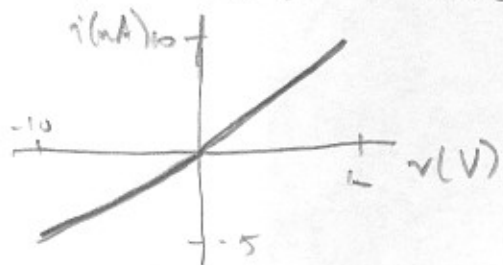(c) $v > 0 \rightarrow A \text{ on}$ $v < 0 \rightarrow B \text{ on}$



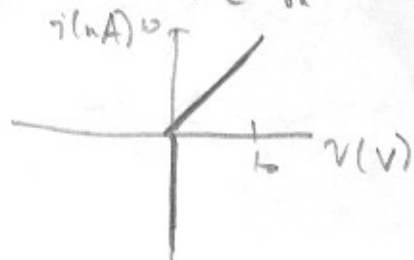(d) $v > 0 \rightarrow C \text{ on}$ $v < 0 \rightarrow D \text{ on}$



E2.4

E2.4

(a) $N_a > N_d \rightarrow$ holes

(b) $p_0 = N_a - N_d = 5 \times 10^{16} \text{ cm}^{-3}$

(c) $n_0 = \frac{n_i^2}{p_0} = 2 \times 10^3 \text{ cm}^{-3}$

E2.10

(a) $v_{dp} = \mu_p E = (150 \text{ cm}^2/\text{Vs})(2 \times 10^3 \text{ V/cm}) = 3 \times 10^5 \text{ cm/s}$

(b) $J_p^{dr} = q p v_{dp} = (1.6 \times 10^{-19} \text{ C})(10^{16} \text{ cm}^{-3})(3 \times 10^5 \text{ cm/s}) = 4.8 \times 10^4 \text{ A/cm}^2$

(c) $\Delta t = \frac{\Delta x}{v_{dp}} = \frac{1 \mu\text{m}}{3 \times 10^5 \text{ cm/s}} = 3.333 \times 10^{-10} \text{ s} = 333.3 \text{ ps}$

(d) $\# \text{ collisions} = \frac{\Delta t}{\tau_c} = \frac{333.3 \text{ ps}}{0.5 \text{ ps}} = 666.7$

E2.11

(a) $N_a > N_d \rightarrow$ p-type

(b) $p_0 = N_a - N_d = 2 \times 10^{14} \text{ cm}^{-3}$

(c) $E = \frac{v_{dp}}{\mu_p} = \frac{4 \times 10^6 \text{ cm/s}}{475 \text{ cm}^2/\text{Vs}} = 8.421 \times 10^3 \text{ V/cm}$

(d) $J_p^{dr} = q p v_{dp} = (1.6 \times 10^{-19} \text{ C})(2 \times 10^{14} \text{ cm}^{-3})(4 \times 10^6 \text{ cm/s})$
 $= 128 \text{ A/cm}^2$

P2.2

$N_d = 10^{16} \text{ cm}^{-3} + 2.5 \times 10^{15} \text{ cm}^{-3} = 1.25 \times 10^{16} \text{ cm}^{-3}$

$N_a = 1.15 \times 10^{16} \text{ cm}^{-3}$

$n_0 = N_d - N_a = 2 \times 10^{15} \text{ cm}^{-3}$

$p_0 = \frac{n_i^2}{n_0} = 5 \times 10^5 \text{ cm}^{-3}$

P2.5


P2.5

$$n_0 = \frac{N_A}{2} \left(1 + \sqrt{1 + 4 \left(\frac{n_i}{N_A} \right)^2} \right)$$

$$n_i = A T^{3/2} e^{-6608.7/T}$$

$$A = \frac{1.42 \times 10^9}{273^{3/2} e^{-6608.7/273}} = 1.026 \times 10^{16}$$
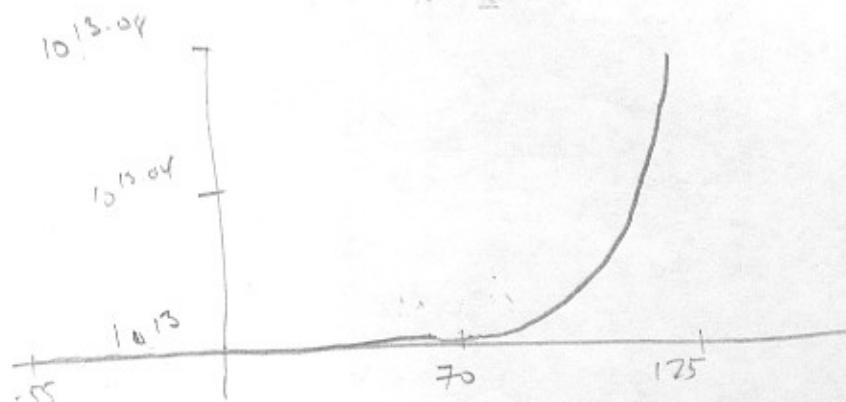
$$n_0 = \frac{10^{15}}{2} \left(1 + \sqrt{1 + 4 A^2 T^3 e^{-6608.7/T}} \right)$$



$$(b) \frac{p_0}{n_0} = \frac{n_i^2}{n_0^2} = 10^{-7} \rightarrow \frac{n_i}{n_0} = 10^{-3/2}$$

$$\frac{A T^{3/2} e^{-6608.7/T}}{\frac{10^{15}}{2} \left(1 + \sqrt{1 + 4 A^2 T^3 e^{-6608.7/T}} \right)} = 10^{-3/2}$$

$$\rightarrow T = 345 \text{ K}$$

P2.7

$$(a) E_x = \frac{2V}{24\mu\text{m}} = 8.333 \times 10^2 \text{ V/cm}$$

$$(b) v_{dn} = -\mu_n E_x = (1450 \text{ cm}^2/\text{Vs}) (8.333 \times 10^2 \text{ V/cm}) = -1.208 \times 10^6 \text{ cm/s}$$

$$v_{dp} = \mu_p E_x = (500 \text{ cm}^2/\text{Vs}) (8.333 \times 10^2 \text{ V/cm}) = 4.167 \times 10^4 \text{ cm/s}$$

$$(c) \Delta t = \frac{\Delta x}{v_{dn}} = \frac{24\mu\text{m}}{1.208 \times 10^6 \text{ cm/s}} = 1.987 \times 10^{-9} \text{ s}$$

$$(d) J_n^{dr} = -q n v_{dn} = (-1.6 \times 10^{-19} \text{ C}) (10^{13} \text{ cm}^{-3}) (-1.208 \times 10^6 \text{ cm/s}) = 1.933 \text{ A/cm}^2$$

$$J_p^{dr} = q p v_{dp} = (1.6 \times 10^{-19} \text{ C}) (10^7 \text{ cm}^{-3}) (4.167 \times 10^4 \text{ cm/s}) = 6.667 \times 10^{-8} \text{ A/cm}^2$$


$$\% \text{ error} = \left| \frac{J_p^{dr}}{J_n^{dr} + J_p^{dr}} \right| \times 100\% = 0.000003449\%$$

$$(e) \sigma = \frac{J}{E} = \frac{1.933}{833.3} = 2.32 \times 10^{-3} \Omega^{-1} \text{ cm}^{-1}$$

$$R = \frac{1}{\sigma} \frac{L}{Wt} = \left(\frac{1}{2.32 \times 10^{-3} \Omega^{-1} \text{ cm}^{-1}} \right) \frac{24 \times 10^{-4} \text{ cm}}{6 \times 10^{-4} \text{ cm} \times 2 \times 10^{-4} \text{ cm}} = 8.621 \text{ M}\Omega$$

P2.10

(a)

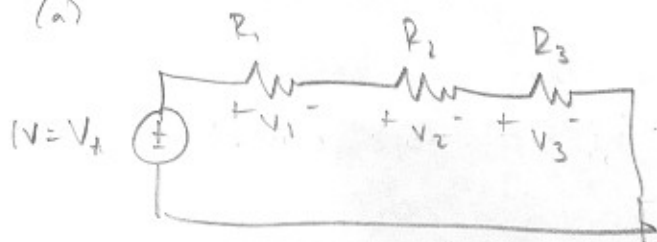

$$R_1 = \frac{L}{q\mu t W} = \frac{4 \times 10^{-4} \text{ m}}{(1.6 \times 10^{-19} \text{ C})(10^{15} \text{ cm}^{-3})(480 \text{ cm}^2/\text{Vs})(1 \times 10^{-4} \text{ cm})(2 \mu\text{m})} = 260.4 \text{ k}\Omega$$



$$R_2 = \frac{2 \mu\text{m}}{(1.6 \times 10^{-19} \text{ C})(2 \times 10^{14} \text{ cm}^{-3})(490 \text{ cm}^2/\text{Vs})(1 \times 10^{-4} \text{ cm})(2 \mu\text{m})} = 637.8 \text{ k}\Omega$$

$$R_3 = R_1 = 260.4 \text{ k}\Omega$$

$$I = \frac{V}{\sum R} = 0.8631 \mu\text{A}$$

$$V_1 = V_3 = 0.2248 \text{ V}$$

$$V_2 = 0.5505 \text{ V}$$

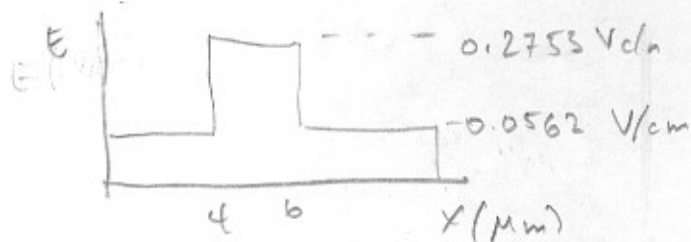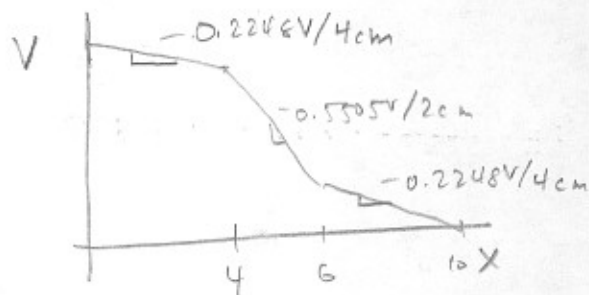


(b) $I_{\max} = J_{\max} Wt = q\mu v_{\max} Wt$
smallest μ because all regions must satisfy
 $= (1.6 \times 10^{-19} \text{ C})(2 \times 10^{14} \text{ cm}^{-3})(10^7 \text{ cm/s})(2 \times 10^{-4} \text{ cm})(10^{-4} \text{ cm}) = 6.4 \mu\text{A}$

(c) $V_{\max} = I_{\max} R_{\text{tot}} = 7.415 \text{ V}$


(d) $E_1 = E_3 = IR / \Delta X = (6.4 \mu\text{A})(260.4 \text{ k}\Omega) / 4 \mu\text{m} = 4.166 \text{ kV/cm}$

$$E_2 = (6.4 \mu\text{A})(637.8 \text{ k}\Omega) / 2 \mu\text{m} = 20.41 \text{ kV/cm}$$

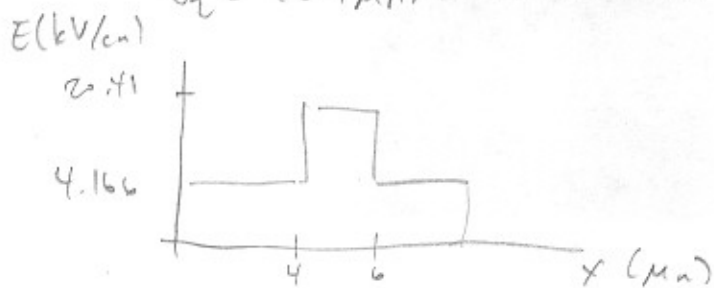

Problem 1

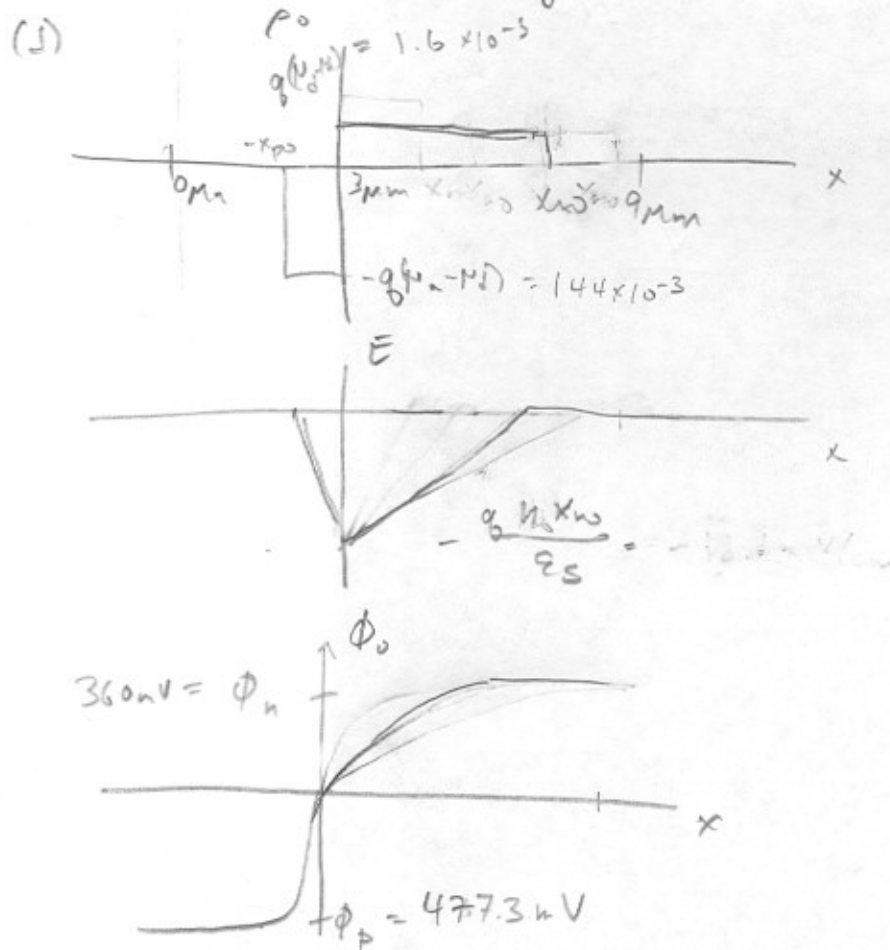- (a) The potential barrier is reduced and we get drift current
 (b) The potential barrier is increased so that we have no drift current and are dominated by diffusion current.
 (c) The acceptor doping is heavier \rightarrow holes are majority carrier, electrons are minority



$$x_{n0} = \sqrt{\frac{2\epsilon_s \phi_B}{q N_d} \left(\frac{N_a}{N_d + N_a} \right)} = 7.165 \mu$$

$$x_{p0} = \sqrt{\frac{2\epsilon_s \phi_B}{q N_a} \left(\frac{N_d}{N_d + N_a} \right)} = 1.187 \mu$$

$$\phi_B = 360 \text{ mV} + 477.3 \text{ mV} = 837.3 \text{ mV}$$

(e) $W_j = x_{n0} + x_{p0} = 8.352 \mu$

$$C = \frac{\epsilon_s W_j}{W_j} = \frac{(11.7 \times 8.85 \times 10^{-14}) (5 \times 10^{-4}) (1 \times 10^{-4})}{8.352 \times 10^{-4}} = 6.2 \times 10^{-17} \text{ F/cm}$$


Problem 2

(a) n: $n_i = N_d = 10^{17} \text{ cm}^{-3}$

p: $p_o = N_a - N_d = 1.1 \times 10^{17} - 1 \times 10^{17} = 1 \times 10^{16} \text{ cm}^{-3}$

(b) $R_D = \frac{1}{q_p \mu_p t} = \frac{1}{(1.6 \times 10^{-19})(10^{16})(275)(100 \times 10^{-4})} = 227.3 \Omega/\square$

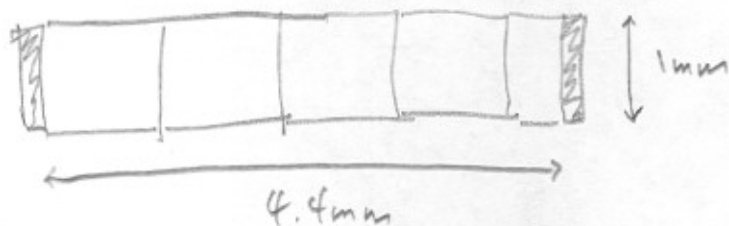(c) $\frac{1 \text{ k}\Omega}{227.3 \Omega/\square} = 4.4 \square$



(d) When we forward bias the pn junction

$\phi_B = 360 + 420 = 780 \text{ mV}$ (60 mV rule)

$V = 2V + 780 \text{ mV} = 2.78 \text{ V}$

Problem 3

(a) n: $n_i = N_d = 10^{17} \text{ cm}^{-3}$

p: $p_o = N_a - N_d = 1.1 \times 10^{17} - 10^{17} = 10^{16} \text{ cm}^{-3}$

p+: $p_o = N_a - N_d = 10^{18} + 1.1 \times 10^{17} - 10^{17} = 1.01 \times 10^{18} \text{ cm}^{-3}$


(b) $R_{Dp+} = \frac{1}{q p_o \mu_p t} = \frac{1}{(1.6 \times 10^{-19})(1.01 \times 10^{18})(175)(1 \times 10^{-4})} = 42.5 \Omega/\square$

(c) $R_{Dp} = \frac{1}{(1.6 \times 10^{-19})(1 \times 10^{16})(275)(2 \times 10^{-4})} = 11.36 \text{ k}\Omega/\square$


(d) $R_D = R_{Dp+} \parallel R_{Dp} = 398 \Omega/\square$

Problem 4

(a) V_{oc}

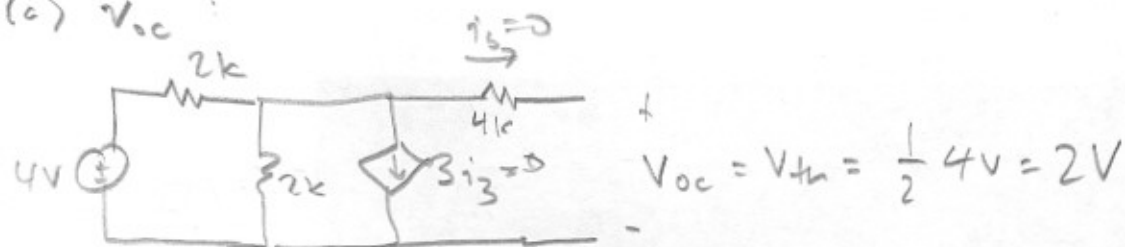

(b) Test current

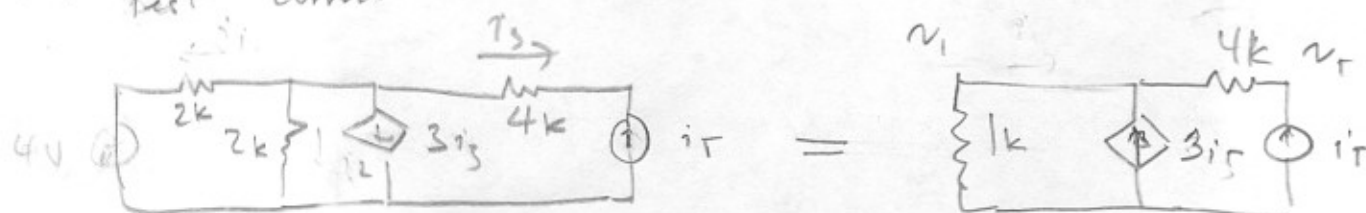

$$i_3 = -i_T$$

$$\frac{v_1}{1k} = 4i_T$$

$$\frac{v_T - v_1}{4k} = i_T$$

$$v_T - (4i_T)(1k) = i_T(4k)$$


$$v_T = 8k(i_T) \rightarrow R_{eq} = 8k$$

Plugging this load line, we get $V = 1.6V, I = 0.8mA$

Problem 5


on/on

→

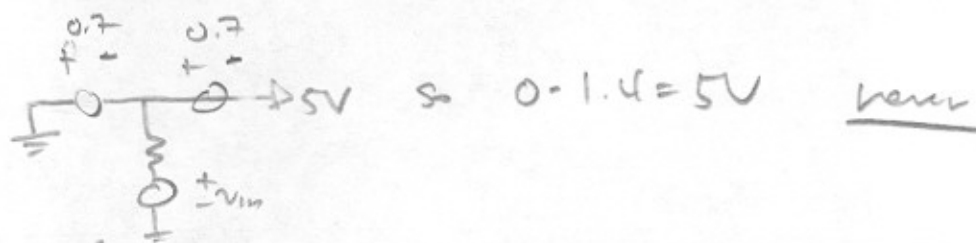


on/off

→

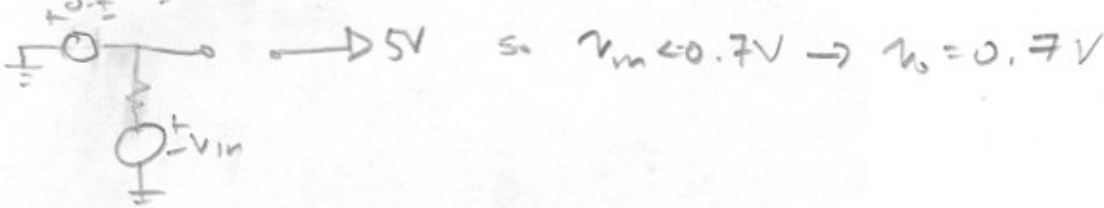


off/on

→

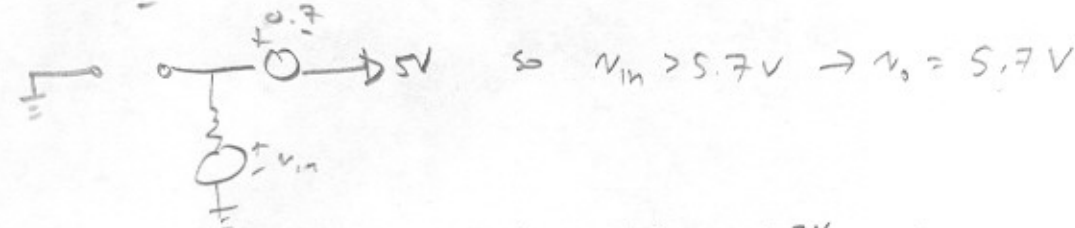


off/off

→

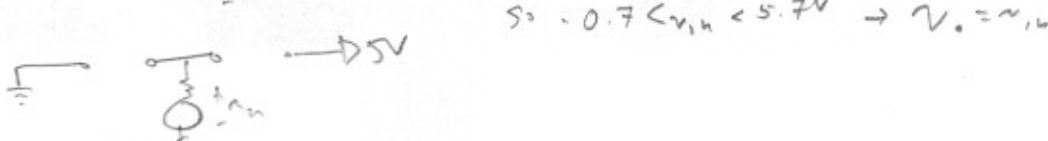

Problem 5 (cont'd)

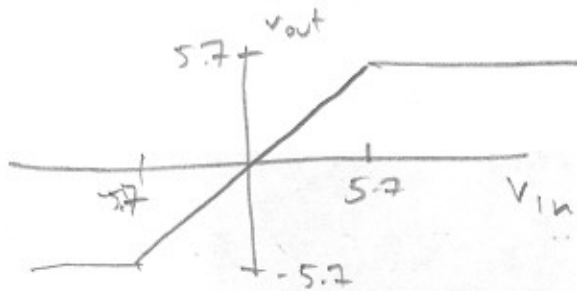


Problem 6

$$(a) \phi_B = 60 \text{ mV} \left[\log \left(\frac{10^{18}}{10^{10}} \right) + \log \left(\frac{1.5 \times 10^7}{10^{10}} \right) \right] = 910.6 \text{ mV}$$

(b) $n_1 D_1$ on:

$$v_o = \frac{2}{3} (v_{in} + 0.9106 \text{ V})$$

$$v_o > 0 \rightarrow v_{in} > -0.9106$$

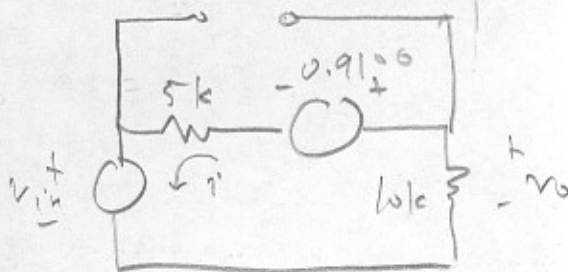

$n_2 D_2$ on:


$$v_{in} \leq 0.9106 \text{ V}$$

Then:

$$v_{in} - v_o \geq 0.9106$$

$$v_o \geq 0 \rightarrow v_{in} \geq 0.9106$$

$$v_o = v_{in} - 0.9106$$

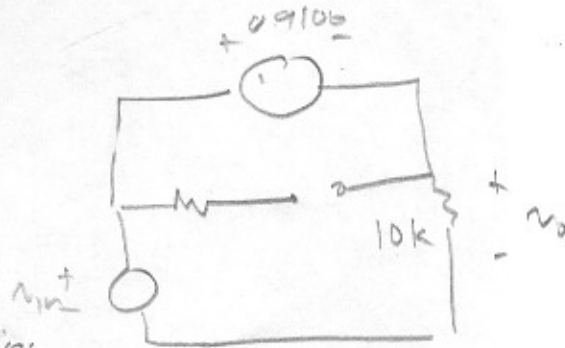

Both can't be on b/c $\rightarrow v_{in} \geq v_o$

$\therefore -0.9106 < v_{in} < 0.9106 \rightarrow$ both off $\rightarrow v_o = 0$

