

Find the solution

12.15

$$i_D = K(V_{GS} - V_T)^2$$

$$V_{GS} = V_T \pm \sqrt{\frac{i_D}{K}} = -2V \pm 2V = 0V, -4V$$


But 0V would not be solution, so  $V_{GS} = -4V$

12.24

$$V_{GS} = 7V + \sin 2000\pi t - 10V = -3V + \sin 2000\pi t$$

Because sin can range between 1V and -1V,
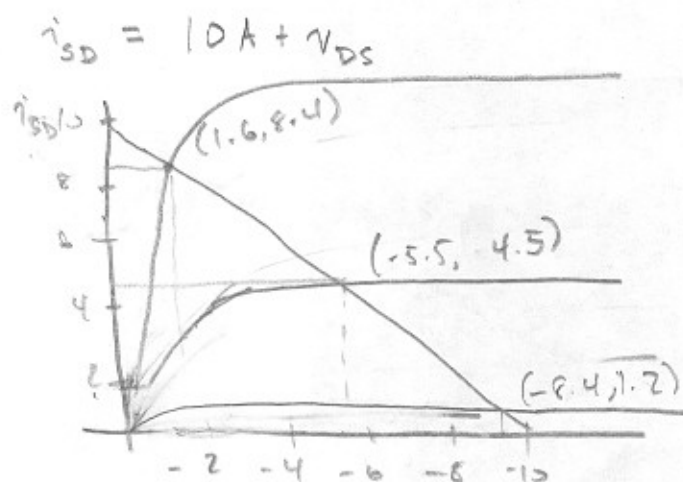
$$V_{GS\max} = -2V, V_{GS\min} = -4V \quad V_{GSQ} = -3V$$



$$V_{DSQ} = 1k I_{SD}$$

$$V_{D\max} = 8.4V$$

$$V_{D\min} = 1.2V$$

$$V_{DQ} = 4.5V$$

12.30

$$I_{DQ} = \frac{2k(20V - 8V - 2V)}{2k\Omega} = 5mA$$

$$R_S = 2V / I_{DQ} = 400\Omega$$

Assuming saturation ( $V_{DS} = 8V$ )

$$I_{DQ} = \frac{1}{2} 50 \times 10^{-6} \frac{600}{20} (V_{GS} - 1)^2 \rightarrow V_{GS} = 1.582, 3.582$$

↑  
saturation

(check  $V_{DS} > V_{GS} - V_T$ )

$$V_G = V_{GS} + 2V = 5.582V$$

$$V_G = 20V \frac{1M\Omega}{1M\Omega + R_1} \rightarrow R_1 = \frac{1M\Omega}{V_G/20V} - 1M\Omega = 2.583M\Omega$$

12.37

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(v_{GS} - V_T)v_{DS} - v_{DS}^2]$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = \mu_n C_{ox} \frac{W}{L} v_{DSQ}$$


12.40

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = 3e^{v_{GSQ}} = 3e = 8.155 \text{ mS}$$

$$\frac{1}{r_d} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = 0.02 v_{DSQ} = 0.2 \text{ mS} \rightarrow r_d = \frac{1}{0.2 \text{ mS}} = 5 \text{ k}\Omega$$

12.47

(a)

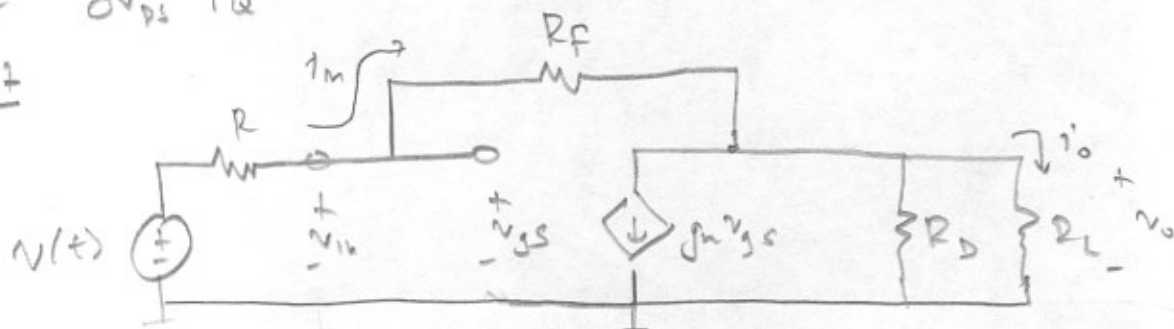


(b)

$$\text{KCL: } i_{in} = g_m v_{gs} + v_o \left( \frac{1}{R_D \parallel R_L} \right) \rightarrow v_o = (R_D \parallel R_L) (i_{in} - g_m v_{gs})$$

$$i_{in} = \frac{v_{in} - v_o}{R_f} \rightarrow v_o = (R_D \parallel R_L) \left( \frac{v_{in} - v_o}{R_f} - g_m v_{gs} \right)$$

$$\text{Solving: } A_v = \frac{v_o}{v_{in}} = \frac{(R_D \parallel R_L) - g_m (R_D \parallel R_L) R_f}{(R_D \parallel R_L) + R_f}$$

$$R_m = \frac{v_{in}}{i_{in}} = \frac{R_f}{1 - A_v}$$

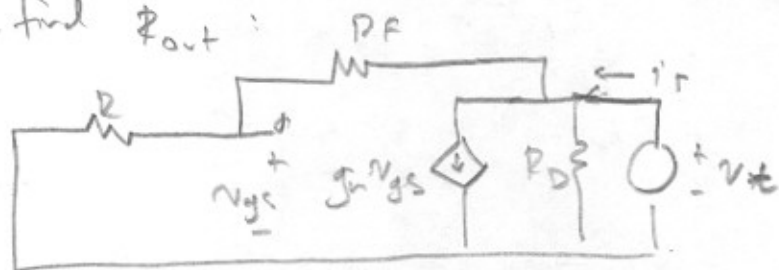To find  $R_{out}$ :


$$v_g = v_t \frac{R}{R + R_f} \quad (\text{voltage divider})$$

$$\text{KCL: } i_t = \frac{v_t}{R_D \parallel (R + R_f)} + g_m v_{gs} = v_t \left( \frac{1}{R_D \parallel (R + R_f)} + \frac{g_m R}{R + R_f} \right)$$

$$R_{out} = \frac{v_t}{i_t} = \frac{1}{\frac{1}{R_D \parallel (R + R_f)} + \frac{g_m R}{R + R_f}}$$

2.47 (cont'd)

(c) Dc.

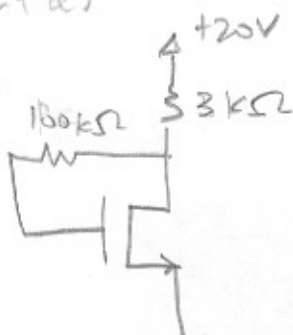

Since there is no current into the gate:  $V_{gs} = V_{ds}$

Thus  $V_{ds} > V_{gs} - V_T \rightarrow$  saturation

$$I_{DQ} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)^2$$

Load line:  $I_{DQ} = (20V - V_{ds}) / 3k\Omega$

Solving:  $V_{DSe} = 7.08, 2.59$   
 $\uparrow < V_T$

$$I_{DQ} = K(V_{DSe} - V_T)^2 = 4.31 \text{ mA}$$

$$g_m = \left. \frac{\partial i_D}{\partial V_{gs}} \right|_Q = \frac{\partial}{\partial V_{gs}} K(V_{gs} - V_T)^2 \bigg|_Q = 2K(V_{DSe} - V_T) = 4.16 \text{ mS}$$

$V_{gs} = V_{ds}$

(d)  $A_v = -9.37$

$R_{in} = 9.64k\Omega$

$R_o = 414\Omega$

(e)  $v_o(t) = A_v v_{in}(t) = A_v \frac{R_{in}}{R + R_{in}} v(t) = -0.164 \sin(2000\pi t)$

(f) inverting ( $A_v < 0$ )

2.51

Assuming saturation:

$$I_{DQ} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)^2$$

$$\rightarrow V_{gs} = V_T + \sqrt{\frac{2I_{DQ}L}{\mu_n C_{ox}W}} = 3.23 \text{ V}$$

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 10 \text{ V}$$

$$V_G = V_{gs} + R_S I_{DQ} \rightarrow R_S = \frac{V_G - V_{gs}}{I_{DQ}} = \boxed{3.382k\Omega}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{DQ}} = 1.789 \text{ mS}$$

$$A_v = \frac{v_o}{v_{in}} = \frac{g_m (R_L \parallel R_S \parallel r_d)}{1 + g_m (R_L \parallel R_S \parallel r_d)} = \boxed{0.6922}$$

12.51 cont'd

$$R_{in} = R_1 || R_2 = 666.7 \text{ k}\Omega$$


$$R_0 = \frac{1}{g_m + \frac{1}{R_S} + \frac{1}{R_D}} = 386.9 \Omega$$

P2.1

$$(a) V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 3V$$

$$(b) V_{GS} = V_G - I_{DS} R_S$$

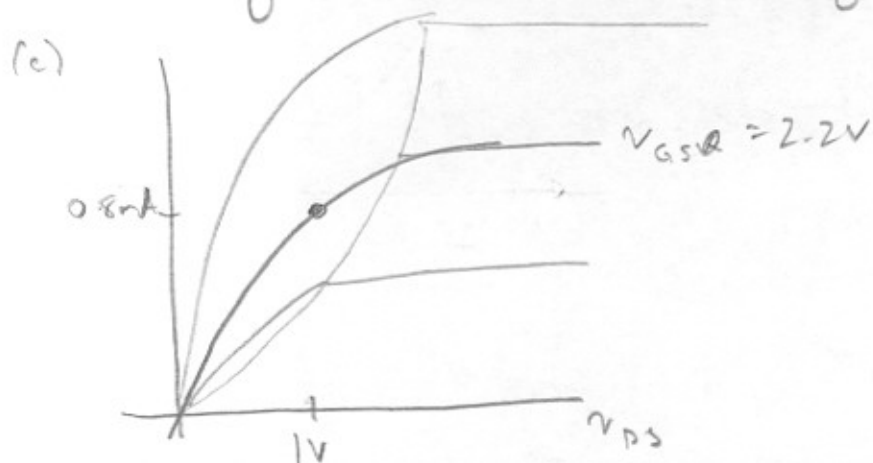Plotting the load line, we get  $V_{GS} = 2.2V$   $I_{DS} = 0.8 \text{ mA}$




$$(d) V_{DSQ} = V_{DD} - I_{DSQ} (R_D + R_S) = 1V$$

$$(e) N_0$$

$$(f) V_0 = V_{DD} - I_{DS} R_D = 1.8V$$

P2.2

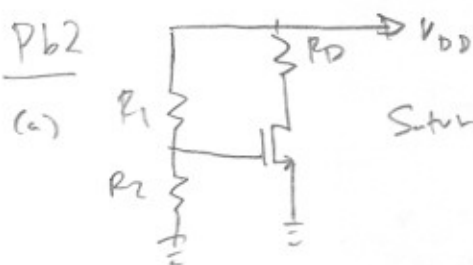


$$V_{GSQ} = V_{DD} \frac{R_2}{R_1 + R_2} = 3V$$

Solution:

$$I_{DSQ} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GSQ} - V_T)^2 = 4 \text{ mA}$$

$$V_{DSQ} = V_{DD} - I_{DSQ} R_D = 7V$$



Pt 2 (cont'd)  
(b)

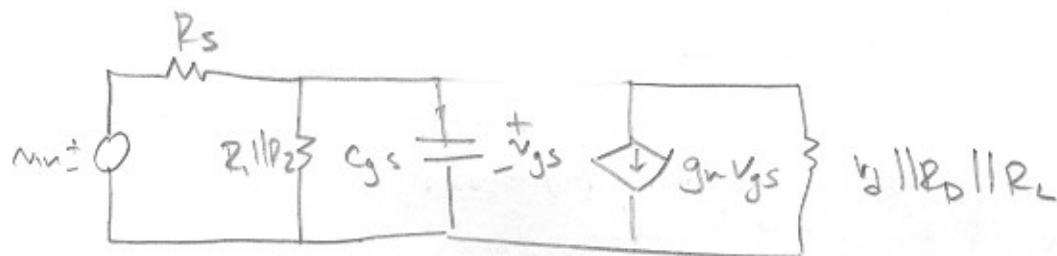

$$\frac{v_g}{v_{in}} = \frac{R_1 || R_2 || \frac{1}{j\omega C_{gs}}}{R_s + R_1 || R_2 || \frac{1}{j\omega C_{gs}}} = \frac{R_G}{R_G + R_s + j\omega R_G R_s C_{gs}} = \frac{8 \times 10^5}{8.1 \times 10^5 + j\omega / 25000}$$


$$(c) \frac{v_o}{v_{in}} = -g_m v_{gs} (R_d || R_L) = \frac{5.818 \times 10^6}{8.1 \times 10^5 + j\omega / 25000}$$

$$= 7.183 \frac{1}{1 + j\omega / 2\pi \cdot 3.223 \text{ MHz}}$$

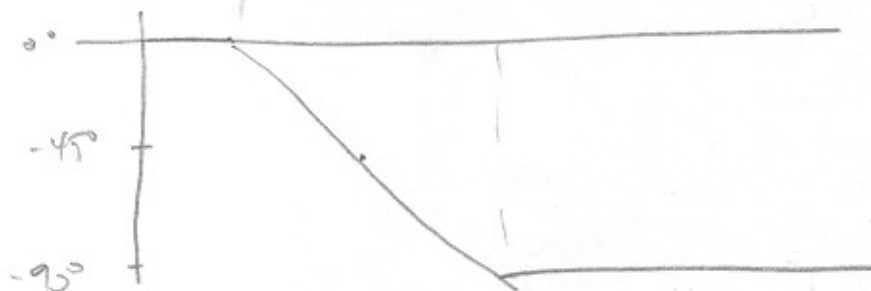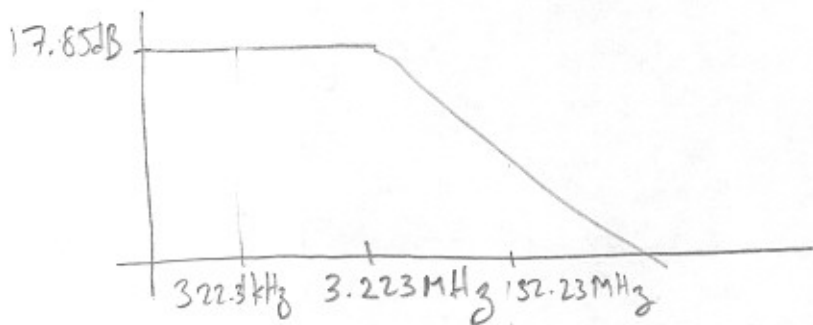

Pt 3

(a)

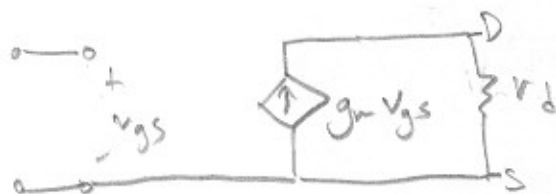


$$g_m = \frac{\partial i_{SD}}{\partial v_{GS}} = \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_T)$$

$$g_m^2 = 2\mu_n C_{ox} \frac{W}{L} I_{SD}$$

$$\rightarrow g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{SD}}$$
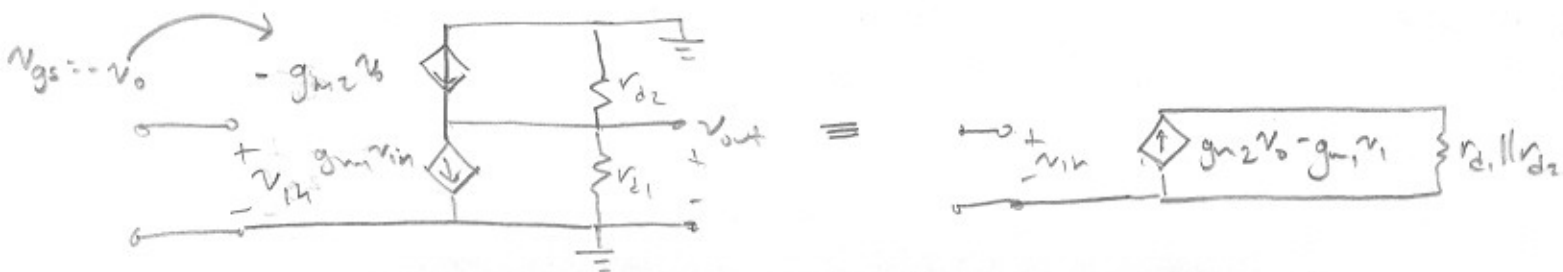
$$\frac{1}{r_d} = \frac{\partial i_{SD}}{\partial v_{DS}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_T)^2 \lambda = \lambda I_{SD} \rightarrow r_d = \frac{1}{\lambda I_{SD}}$$



(c)

$$\frac{v_o}{r_{d1} || r_{d2}} = (-g_{m2}v_o - g_{m1}v_{in}) r_{d1} || r_{d2}$$

$$\rightarrow \left| \frac{v_o}{v_{in}} = -g_{m1} (r_{d1} || r_{d2} || \frac{1}{g_{m2}}) \right|$$

Pb 4

$$\frac{V_1}{V_{in}} = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \quad (\text{HPF})$$

$$V_{out} = \frac{-G_m V_1}{\frac{1}{R_2} + j\omega C_2} = -\frac{G_m V_1 R_2}{1 + j\omega R_2 C_2} \rightarrow \frac{V_{out}}{V_1} = -G_m R_2 \frac{1}{1 + j\omega R_2 C_2}$$

$$\frac{V_{out}}{V_{in}} = -G_m R_2 \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \frac{1}{1 + j\omega R_2 C_2} = -10 \frac{j\omega/1000}{(1 + j\omega/1000)(1 + j\omega/1000)}$$

