 



DC analysis:

DC Bias Pt:
input load line


$$V_{IN} = V_{DD} - I_{IN} \cdot R_{IN}$$



output Bias pt:

 


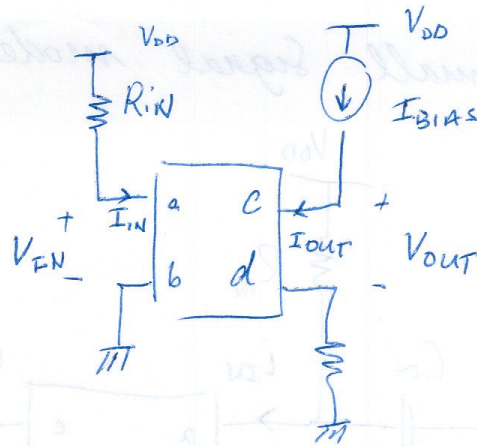So we have I_{INQ} , V_{INQ} , I_{OUTQ} , V_{OUTQ} .
let's construct a SSM.







Small signal model example:

1

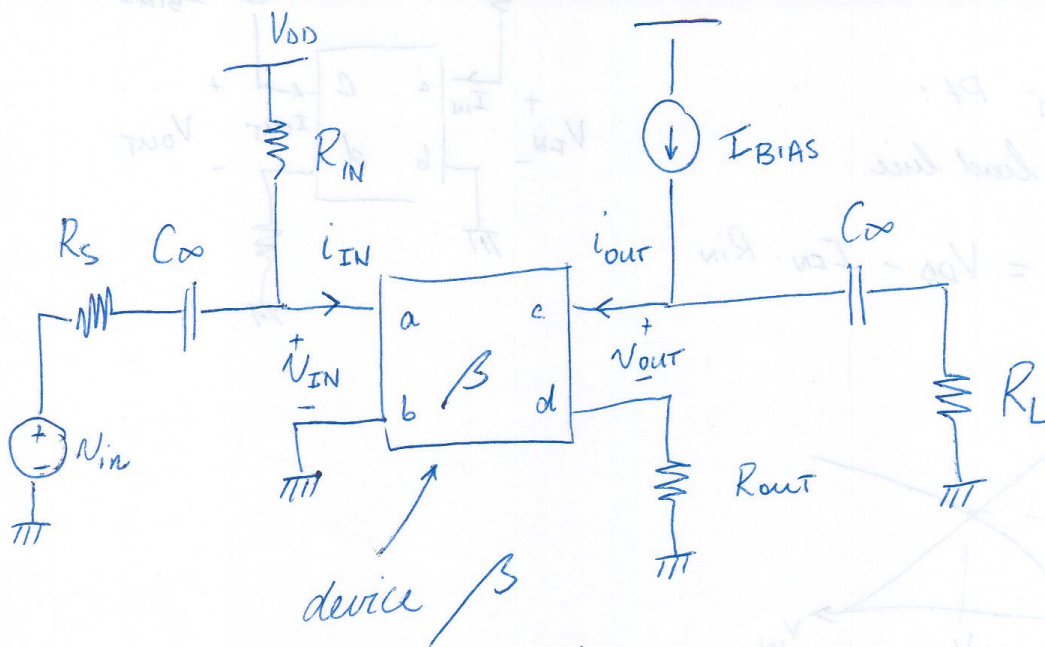

Device β characteristics:

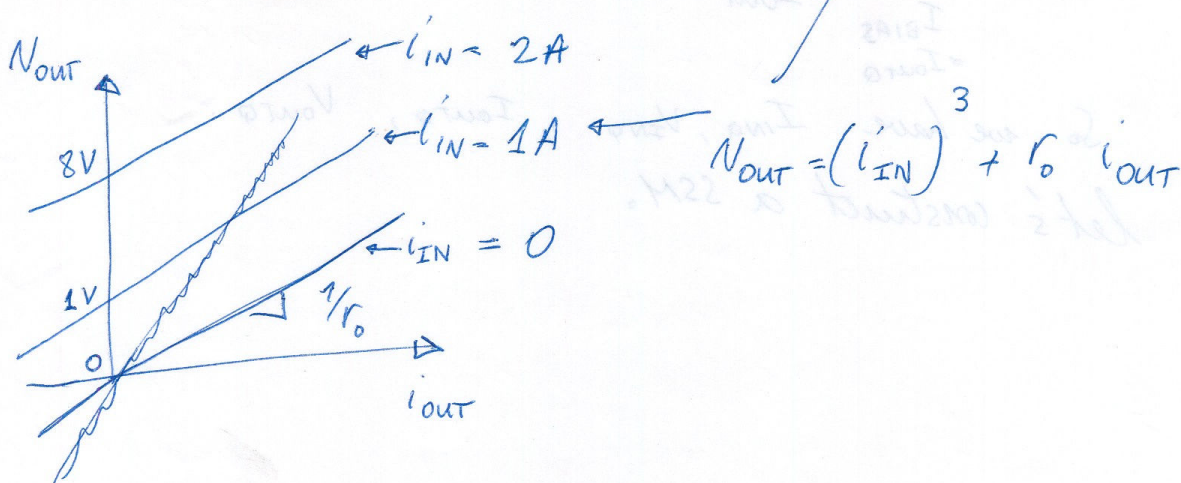  

 

$$i_{in} = \frac{\partial i_{IN}}{\partial V_{IN}} \bigg|_{V_{INQ}, I_{INQ}} \cdot V_{in} \quad (2)$$

We can model:


$$r_{in} = \frac{1}{\frac{\partial i_{IN}}{\partial V_{IN}} \bigg|_{V_{INQ}, I_{INQ}}}$$

$$\Rightarrow V_{in} = r_{in} \cdot i_{in}$$

$$\Rightarrow \frac{\partial (\sqrt{V_{IN}})}{\partial V_{IN}} = \frac{1}{2} \frac{1}{\sqrt{V_{IN}}} \bigg|_{V_{INQ}}$$

$$\Rightarrow i_{in} = \frac{1}{2} \frac{1}{\sqrt{V_{INQ}}} \cdot V_{in}$$


around V_{INQ}

 

$$v_{out} = \frac{\partial V_{OUT}}{\partial i_{IN}} \bigg|_{I_{INQ}, V_{OUTQ}} \cdot i_{in}$$

$$\frac{\partial V_{OUT}}{\partial i_{IN}} = 3 i_{IN}^2 \bigg|_{I_{INQ}}$$

 
$$\Rightarrow v_{out} = \underbrace{3 \cdot I_{INQ}^2}_{r_m} \cdot i_{in}$$




$$v_{out} = \frac{\partial V_{OUT}}{\partial i_{OUT}} \bigg|_{Q_{pt}} \cdot i_{out}$$

$$\Rightarrow v_{out} = r_o \cdot i_{out}$$

So the total model looks like this:

 

SSM of entire CKT:

 


$$\text{Find } \frac{V_o}{V_i} : \quad \frac{i_{in}}{V_i} = \frac{1}{r_{in}} \cdot \frac{R_{IN} \parallel r_{in}}{R_{IN} \parallel r_{in} + R_s}$$

$$\frac{V_o}{i_{in}} = \frac{r_m \cdot R_L}{R_L + R_{out} + r_o}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1}{r_{in}} \cdot \frac{R_{IN} \parallel r_{in}}{R_{IN} \parallel r_{in} + R_s} \cdot \frac{r_m \cdot R_L}{R_L + R_{out} + r_o}$$

CMOS logic

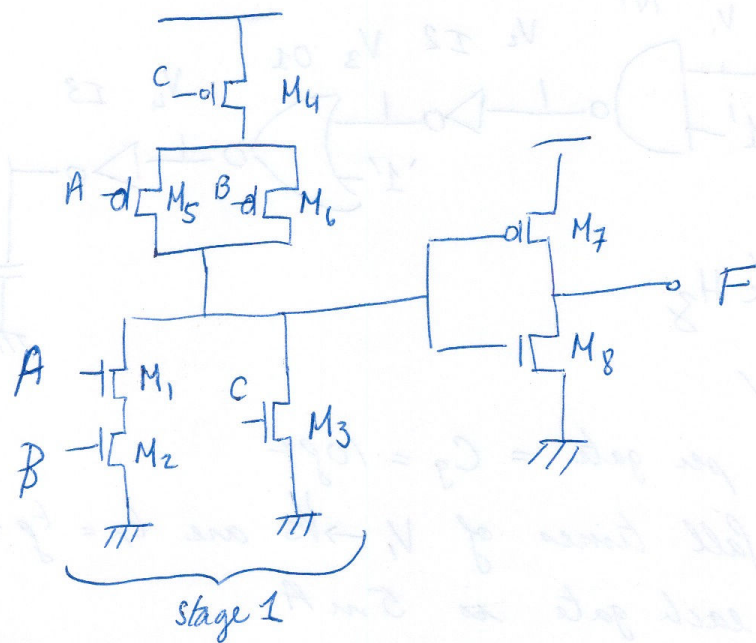a) Implement $F = A \cdot B + C$ using transistors



b) $\mu_n = 3\mu_p$

Suppose $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 2\left(\frac{W}{L}\right)_3$

and $\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_4 = 2\left(\frac{W}{L}\right)_1$

find t_{PHL}/t_{PLH} of stage 1 when


ABC goes from 100 \rightarrow 111 and back.

PDN $\left(\frac{W}{L}\right)_{eq} = \cancel{\left(\frac{W}{L}\right)_1} \times 2$

PUN $\left(\frac{W}{L}\right)_{eq} = \frac{1}{2}\left(\frac{W}{L}\right)_4 = \cancel{\left(\frac{W}{L}\right)_1} = \left(\frac{W}{L}\right)_3 \times 2$

But $\mu_p = \frac{1}{3}\mu_n \Rightarrow \frac{t_{PHL}}{t_{PLH}} = \frac{1}{3}$

CMOS Power Dissipation: 20M

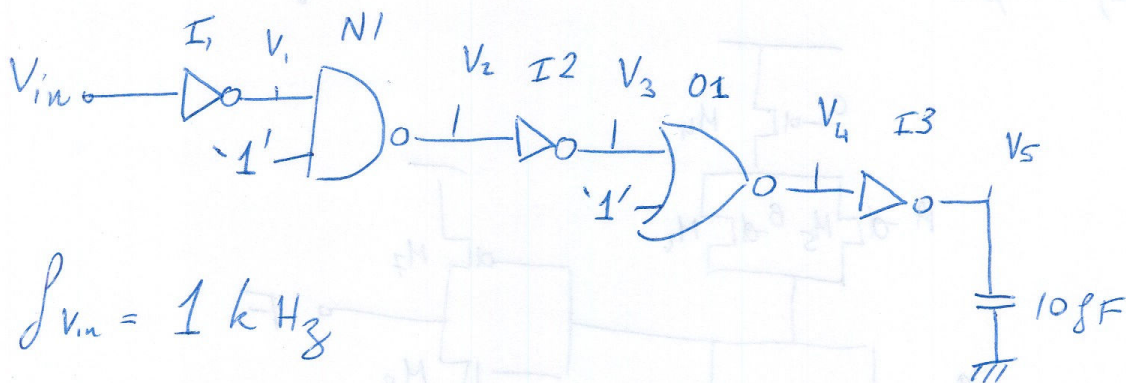

$$f_{V_{in}} = 1 \text{ kHz}$$

$$V_{DD} = 5V$$

$$\text{Capacitance per gate} = C_g = 10 \text{ pF}$$

$$\text{Rise and fall times of } V_1 \rightarrow V_5 \text{ are } t_r = t_f = 10 \text{ ps}$$

$$I_{sc} \text{ for each gate is } 5 \text{ mA}$$

$$I_{leakage} \text{ for each path to ground is } 1 \text{ nA}$$

Find the total power consumption of this Design:

Dynamic power:

① Do not include power needed to charge V_{in} since this will be accounted for in the block driving this one.

$$\text{② only } V_1, V_2, V_3 \text{ toggle} \Rightarrow C_{eff} = 3 \times 2 \times 10 \text{ pF} = 60 \text{ pF}$$

$$\text{③ } P_{dyn} = C_{eff} \cdot V_{DD}^2 \cdot f_{V_{in}}$$

Short-Circuit Power:

$$E_{sc} = 3 \cdot V_{DD} \cdot I_{sc} \cdot t_r \Rightarrow P_{sc} = 3 \cdot V_{DD} \cdot I_{sc} \cdot f_{V_{in}}$$

↑
only 3 gates switch.

Leakage Power:

$$P = 5 \cdot I_{leakage} \cdot V_{DD}$$

↑
since all 5 gates leak.