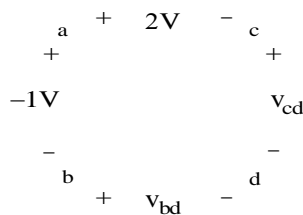


Announcements

- Sections begin this week
 - Cancelled Sections: Th 12-2.
- Labs begin this week. Attend your only second lab slot this week.
 - Cancelled labs: ThF 2-5. Please check your Lab section.
- Homework #1 online
 - Due next Monday at 6pm

Review

Find v_{ab} , v_{ca} , v_{cb}



Note that the labeling convention has nothing to do with whether or not v is positive or negative.

Lecture #2

OUTLINE

- Circuit Elements
- Circuit element I - V characteristics
- Construction of a circuit model
- Kirchhoff's laws – a closer look

Reading

(Chapter 1, begin Ch. 2)

Circuit Elements

- 5 ideal basic circuit elements:
 - ☐ voltage source
 - ☐ current source
 - ☐ resistor
 - ☐ inductor
 - ☐ capacitor
- } **active elements**, capable of generating electric energy
- } **passive elements**, incapable of generating electric energy
- Many practical systems can be modeled with just sources and resistors
 - The basic analytical techniques for solving circuits with inductors and capacitors are similar to those for resistive circuits

Electrical Sources

- An **electrical source** is a device that is capable of converting non-electric energy to electric energy and *vice versa*.

Examples:




- battery: chemical \longleftrightarrow electric
- dynamo (generator/motor): mechanical \longleftrightarrow electric
(Ex. gasoline-powered generator, Bonneville dam)

→ Electrical sources can either deliver or absorb power

Ideal Voltage Source

- Circuit element that maintains a prescribed voltage across its terminals, **regardless of the current flowing in those terminals**.
 - Voltage is known, but current is determined by the circuit to which the source is connected.
- The voltage can be either **independent** or **dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.




Device symbols:

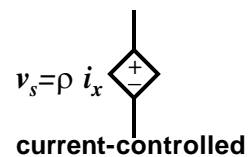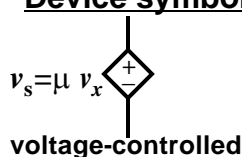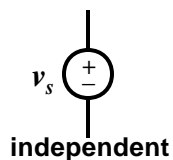

Ideal Current Source

- Circuit element that maintains a prescribed current through its terminals, **regardless of the voltage across those terminals**.
 - Current is known, but voltage is determined by the circuit to which the source is connected.
- The current can be either **independent** or **dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.

Device symbols:

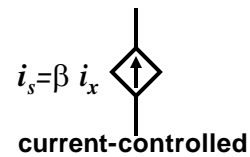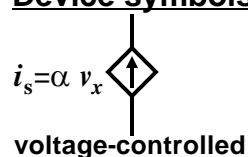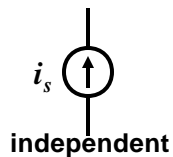

Electrical Resistance

- **Resistance:** the ratio of voltage drop and current. The circuit element used to model this behavior is the **resistor**.

Circuit symbol:



Units: Volts per Ampere ohms (Ω)

- The current flowing in the resistor is proportional to the voltage across the resistor:

$$v = i R \quad (\text{Ohm's Law})$$

where v = voltage (V), i = current (A), and R = resistance (Ω)



Georg Simon Ohm
1789-1854

Electrical Conductance

- **Conductance** is the reciprocal of resistance.

Symbol: G

Units: siemens (S)

Example:

Consider an $8\ \Omega$ resistor. *What is its conductance?*



Werner von Siemens
1816-1892

Short Circuit and Open Circuit

Wire (“short circuit”):

- $R = 0 \rightarrow$ **no voltage difference exists**
(all points on the wire are at the same potential)
- Current can flow, as determined by the circuit

Air (“open circuit”):

- $R = \infty \rightarrow$ **no current flows**
- Voltage difference can exist,
as determined by the circuit


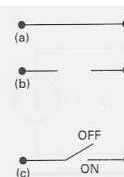


Figure 2.10 Circuit symbols. (a) Short circuit. (b) Open circuit. (c) Switch.



Current vs. Voltage (I - V) Characteristic

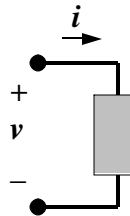- Voltage sources, current sources, and resistors can be described by plotting the current (i) as a function of the voltage (v)



Passive? Active?

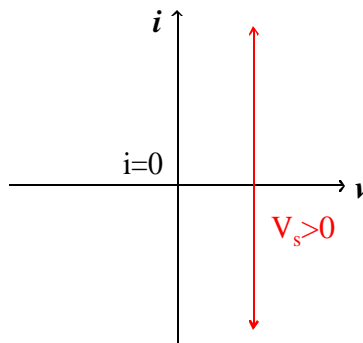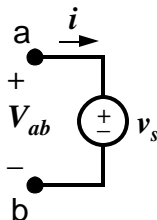I - V Characteristic of an Ideal Voltage Source




1. Plot the I - V characteristic for $v_s > 0$. For what values of i does the source absorb power? For what values of i does the source release power?

$V_s > 0 \rightarrow i < 0$ release power; $i > 0$ absorb power

What is the I - V characteristic for an ideal wire?

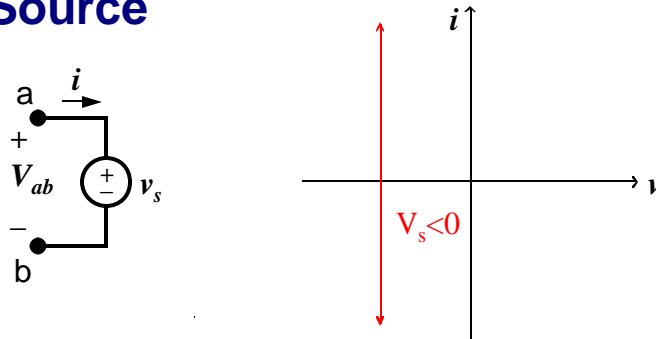
I-V Characteristic of an Ideal Voltage Source



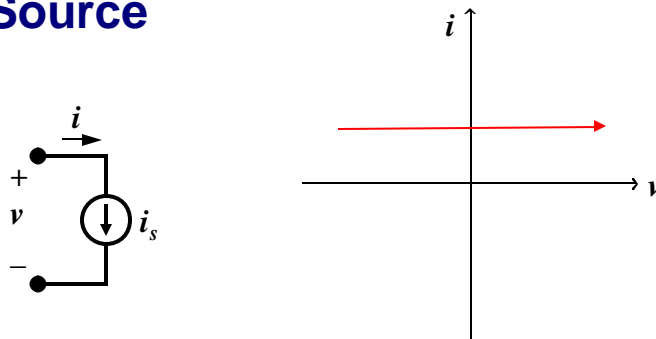2. Plot the I - V characteristic for $v_s < 0$. For what values of i does the source absorb power? For what values of i does the source release power?

$V_s < 0 \rightarrow i > 0$ release power; $i < 0$ absorb power



I-V Characteristic of an Ideal Current Source



1. Plot the I - V characteristic for $i_s > 0$. For what values of v does the source absorb power? For what values of v does the source release power?

$V > 0$ absorb power; $V < 0$ release power

I-V Characteristic of Ideal Resistor

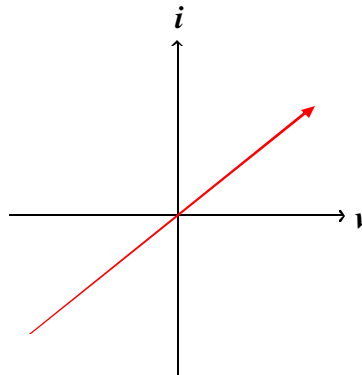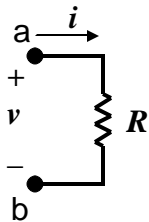

1. Plot the I - V characteristic for $R = 1 \text{ k}\Omega$. What is the slope?

“Lumped Element” Circuit Modeling



(Model = representation of a real system which simplifies analysis)

- In circuit analysis, important characteristics are grouped together in “lumps” (separate circuit elements) connected by perfect conductors (“wires”)
- An electrical system can be modeled by an **electric circuit** (combination of paths, each containing 1 or more **circuit elements**).

Construction of a Circuit Model

- The electrical behavior of each physical component is of primary interest.
- We need to account for undesired as well as desired electrical effects.
- Simplifying assumptions should be made wherever reasonable.

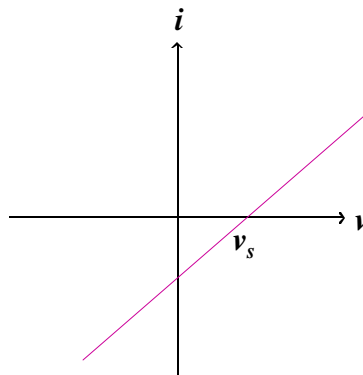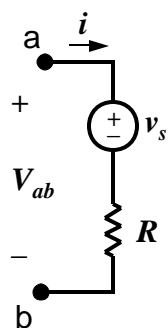
I-V Characteristic of a real Voltage Source



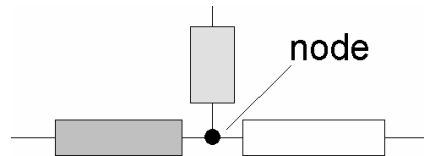
1. What is the I - V characteristic for an real current source?
2. What is the I - V characteristic for an ideal wire?

Terminology: Nodes and Branches

Node: A point where two or more circuit elements are connected




Branch: A path that connects two nodes

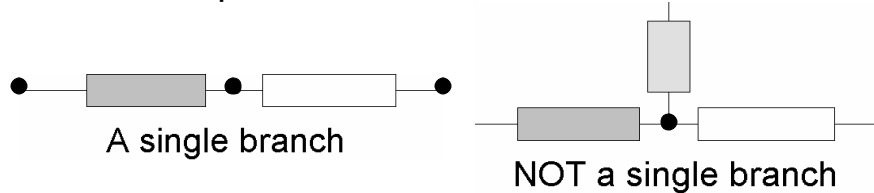

Notation: Node and Branch Voltages


- Use one node as the reference (the “common” or “ground” node) – label it with a symbol
- The voltage drop from node **x** to the reference node is called the **node voltage** v_x .
- The voltage across a circuit element is defined as the difference between the node voltages at its terminals

Example:

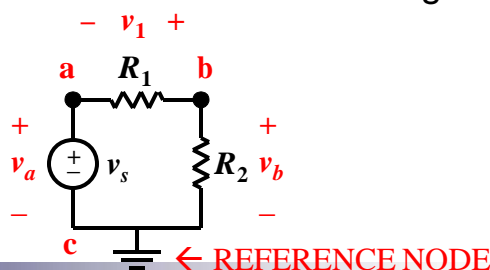

Circuit Loops

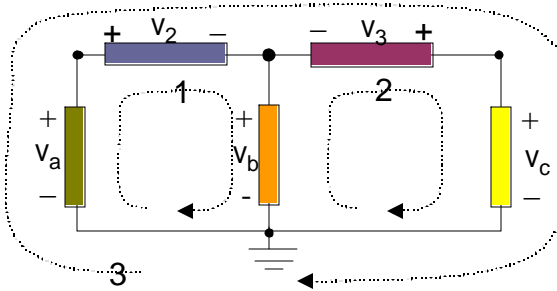- A **loop** is formed by tracing a closed path in a circuit through selected basic circuit elements without passing through any intermediate node more than once. Below are marked loops 1, 2 and 3:



Kirchhoff's Laws


- **Kirchhoff's Current Law (KCL):**
 - The algebraic sum of all the **currents** entering any **node** in a circuit equals zero.
- **Kirchhoff's Voltage Law (KVL):**
 - The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.



Gustav Robert Kirchhoff
1824-1887

Using Kirchhoff's Current Law (KCL)

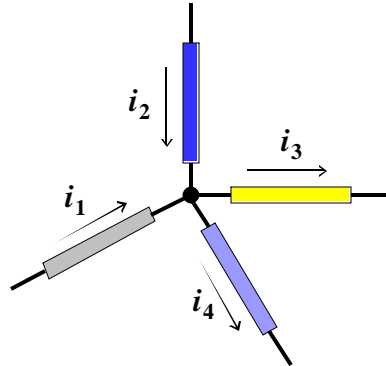Consider a node connecting several branches:



- Use **reference directions** to determine whether currents are “entering” or “leaving” the node — **with no concern about actual current directions**

Formulations of Kirchhoff's Current Law

(Charge stored in node is zero.)

Formulation 1:

Sum of currents entering node
= sum of currents leaving node

Formulation 2:

Algebraic sum of currents entering node = 0

- Currents leaving are included with a minus sign.


Formulation 3:

Algebraic sum of currents leaving node = 0

- Currents entering are included with a minus sign.

A Major Implication of KCL

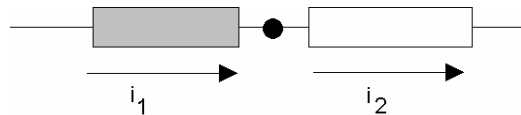
- KCL tells us that **all of the elements in a single branch carry the same current.**
- We say these elements are connected ***in series***.



Current entering node = Current leaving node

$$i_1 = i_2$$

KCL Example

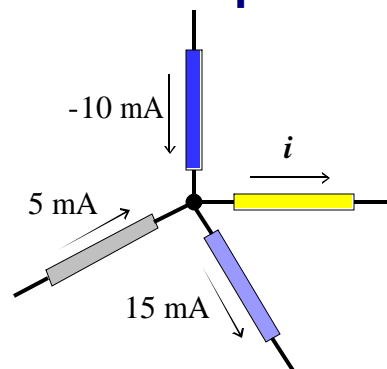

Currents entering the node:


Currents leaving the node:

KCL:



Generalization of KCL

- The sum of currents entering/leaving a **closed surface** is zero. Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

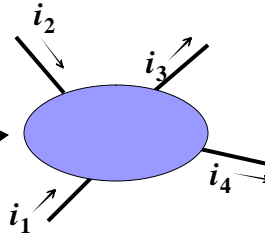This could be a big chunk of a circuit, *e.g.* a “black box”




Generalized KCL Examples

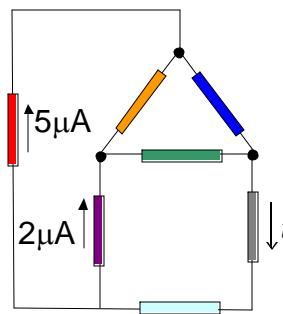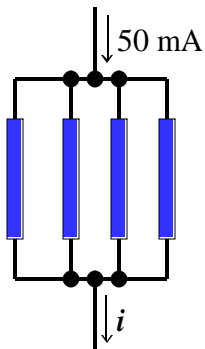

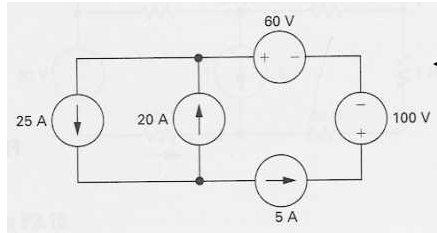
Examples

■ Are these interconnections permissible?




This circuit connection is NOT permissible. It violates the KCL.

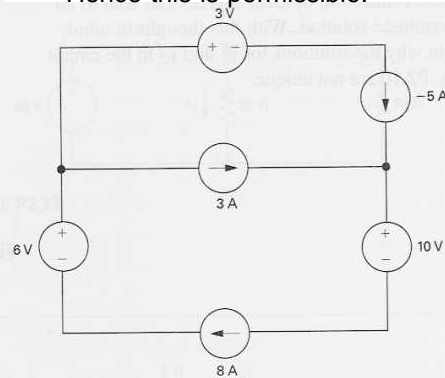This circuit connection is permissible. This is because the current sources can sustain any voltage across; Hence this is permissible.




Using Kirchhoff's Voltage Law (KVL)

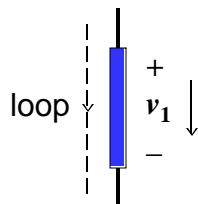Consider a branch which forms part of a loop:



Moving from + to -
We add V_1

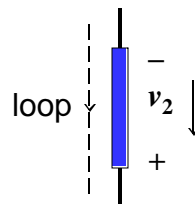

Moving from - to +
We subtract V_1

- Use **reference polarities** to determine whether a voltage is dropped
- **No concern about actual voltage polarities**

Formulations of Kirchhoff's Voltage Law

(Conservation of energy)

Formulation 1:

Sum of voltage drops around loop
= sum of voltage rises around loop

Formulation 2:

Algebraic sum of voltage drops around loop = 0

- Voltage rises are included with a minus sign.

(Handy trick: Look at the first sign you encounter on each element when tracing the loop.)


Formulation 3:

Algebraic sum of voltage rises around loop = 0

- Voltage drops are included with a minus sign.

A Major Implication of KVL

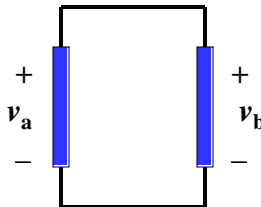- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel.**




Applying KVL in the clockwise direction,
starting at the top:

$$v_b - v_a = 0 \rightarrow v_b = v_a$$

KVL Example

Three closed paths:

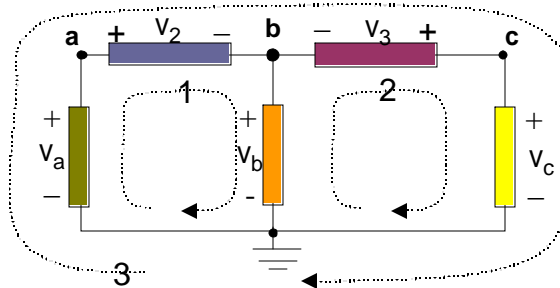

Path 1:


Path 2:

Path 3:

An Underlying Assumption of KVL

- No time-varying magnetic flux through the loop
Otherwise, there would be an induced voltage (Faraday's Law)
- Note: Antennas are designed to “pick up” electromagnetic waves; “regular circuits” often do so undesirably.

Avoid these loops!

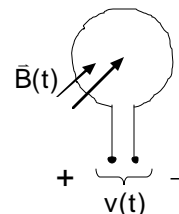

How do we deal with antennas (EECS 117A)?

Include a voltage source as the circuit representation of the induced voltage or “noise”.


(Use a **lumped model** rather than a distributed (wave) model.)

Tips for KCL, KVL

- Find one formulation which works for you and stick with it.
- I suggest:
 - KCL
 - Algebraic sum of currents leaving node = 0
 - Currents entering are included with a minus sign.
 - KVL
 - Algebraic sum of voltage drops around loop = 0
 - Voltage rises are included with a minus sign.


Equivalent Resistance

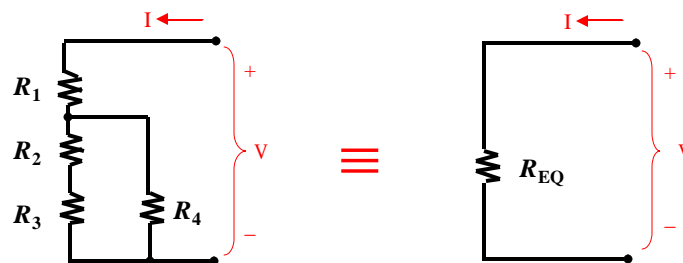- Arrangements of several resistors can be lumped into one equivalent resistance:



Resistors in Series

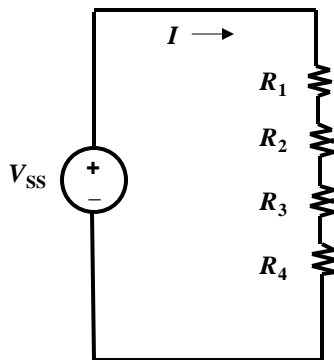Consider a circuit with multiple resistors connected in series.
Find their equivalent resistance.




- KCL tells us that the same current (I) flows through every resistor
- KVL tells us:


Equivalent resistance of series resistors is the sum of resistances

Voltage Divider
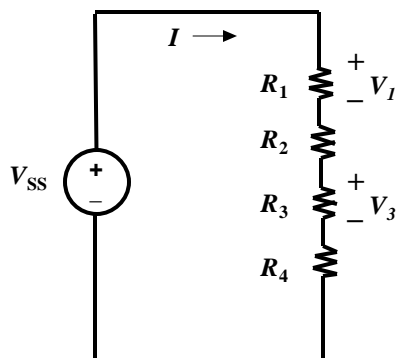
$$I = V_{SS} / (R_1 + R_2 + R_3 + R_4) \dots$$




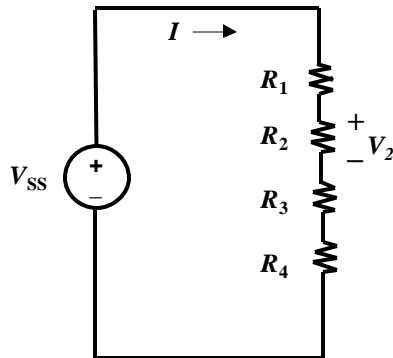When can the Voltage Divider Formula be Used?



$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

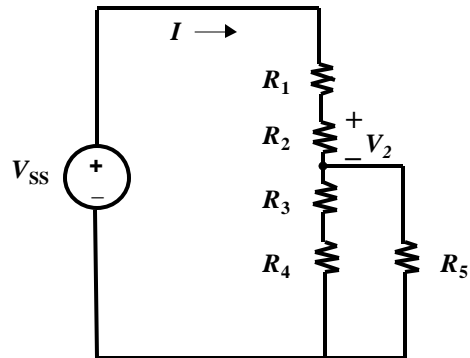Correct, if nothing else
is connected to nodes




$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

Why? What is V_2 ?

Resistors in Parallel

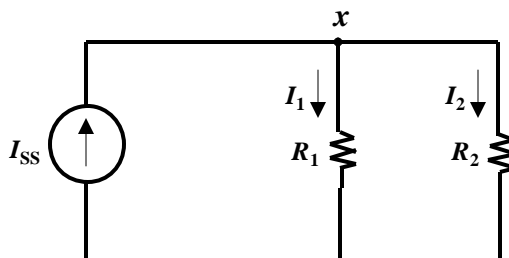
Consider a circuit with two resistors connected in parallel.
Find their equivalent resistance.



- KVL tells us that the same voltage is dropped across each resistor
- KCL tells us:

**Equivalent
conductance of
parallel resistors is the
sum of conductances**


Current Divider

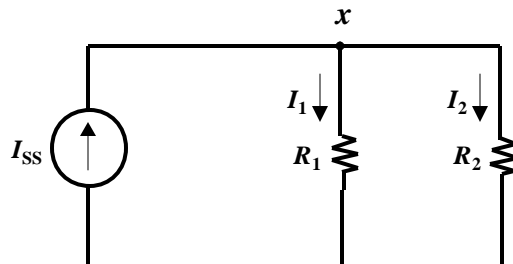

$$V_x = I_1 R_1 = I_2 R_2 \dots$$

Generalized Current Divider Formula

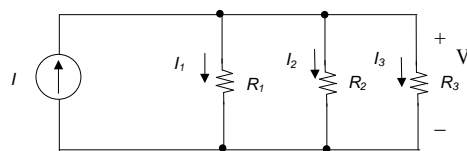Consider a current divider circuit with >2 resistors in parallel:



$$V = \frac{I}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2}\right) + \left(\frac{1}{R_3}\right)}$$

$$I_3 = \frac{V}{R_3} = I \left[\frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3} \right]$$

Example: Power Absorbed by a Resistor


$$p = vi = (iR)i = i^2R$$

$$p = vi = v(v/R) = v^2/R$$

Note that $p > 0$ always, for a resistor \rightarrow a resistor dissipates electric energy

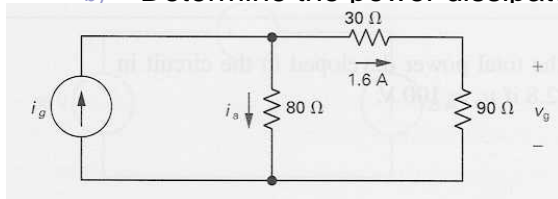Example:

- Calculate the voltage v_g and current i_a .
- Determine the power dissipated in the 80Ω resistor.



EE40 Summer 2006: Lecture 2

Instructor: Octavian Florescu

43

Summary

- An **ideal voltage source** maintains a prescribed voltage regardless of the current in the device.
- An **ideal current source** maintains a prescribed current regardless of the voltage across the device.
- A **resistor** constrains its voltage and current to be proportional to each other:

$$v = iR \quad (\text{Ohm's law})$$

EE40 Summer 2006: Lecture 2

Instructor: Octavian Florescu

44

Summary (cont'd)

- **Kirchhoff's current law (KCL)** states that the algebraic sum of all currents at any node in a circuit equals zero.
- **Kirchhoff's voltage law (KVL)** states that the algebraic sum of all voltages around any closed path in a circuit equals zero.
- **Resistors in Series** – Voltage Divider
- **Conductances in Parallel** – Current Divider