

Lecture #6

OUTLINE


■ Chap 5

- Phasors
- Complex Impedances

Reading

Chap 5.1-5.4

Complex Numbers

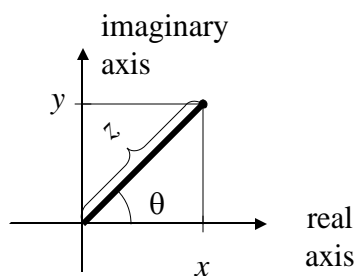

- x is the real part
- y is the imaginary part
- z is the magnitude
- θ is the phase

More Complex Numbers

- Polar Coordinates: $\mathbf{A} = z \angle \theta$
- Rectangular Coordinates: $\mathbf{A} = x + jy$

$$x = z \cos \theta$$

$$y = z \sin \theta$$

$$z = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

Summary of Phasors

- Phasor (frequency domain) is a complex number:

$$\mathbf{X} = z \angle \theta = x + jy$$

- Sinusoid is a time function:

$$x(t) = z \cos (\omega t + \theta)$$

Examples

Find the time domain representations of

$$\mathbf{X} = -1 + j2$$

$$\mathbf{V} = 104\text{V} - j60\text{V}$$

$$\mathbf{A} = -1\text{mA} - j3\text{mA}$$

Arithmetic With Complex Numbers

- To compute phasor voltages and currents, we need to be able to perform computation with complex numbers.

- ☐ Addition
- ☐ Subtraction
- ☐ Multiplication
- ☐ Division

Addition


- Addition is most easily performed in rectangular coordinates:

$$\mathbf{A} = x + jy$$

$$\mathbf{B} = z + jw$$

$$\mathbf{A} + \mathbf{B} = (x + z) + j(y + w)$$

Addition

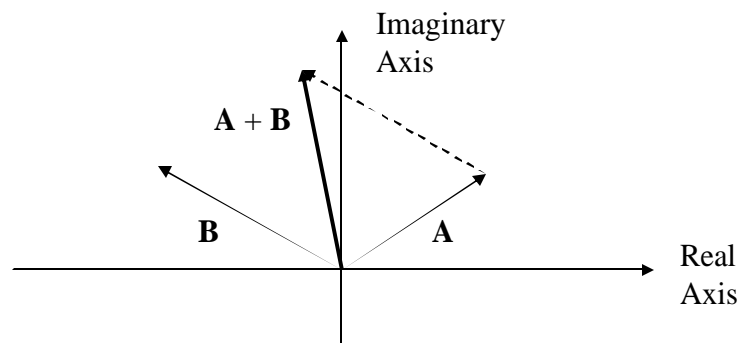

Subtraction


- Subtraction is most easily performed in rectangular coordinates:

$$\mathbf{A} = x + jy$$

$$\mathbf{B} = z + jw$$

$$\mathbf{A} - \mathbf{B} = (x - z) + j(y - w)$$

Subtraction

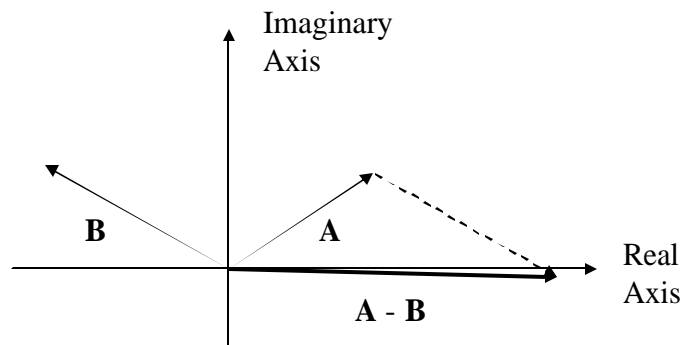

Multiplication


- Multiplication is most easily performed in polar coordinates:

$$\mathbf{A} = A_M \angle \theta$$

$$\mathbf{B} = B_M \angle \phi$$

$$\mathbf{A} \times \mathbf{B} = (A_M \times B_M) \angle (\theta + \phi)$$

Multiplication

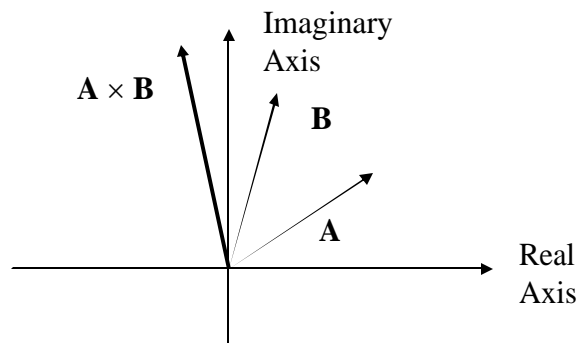

Division


- Division is most easily performed in polar coordinates:

$$\mathbf{A} = A_M \angle \theta$$

$$\mathbf{B} = B_M \angle \phi$$

$$\mathbf{A} / \mathbf{B} = (A_M / B_M) \angle (\theta - \phi)$$

Division

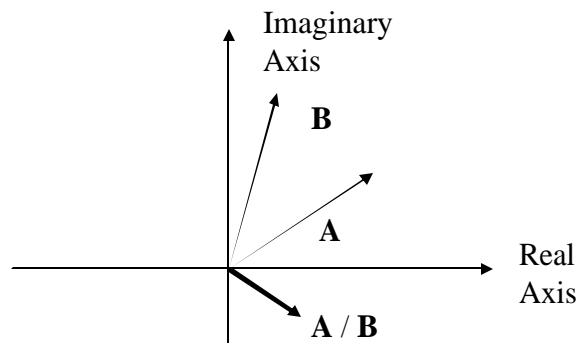

Phasors and Complex Exponentials

- A sinusoid can be described using a complex exponential:

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

So,

$$v(t) = V_M \cos (\omega t + \theta) = \text{Re}[e^{j(\omega t + \theta)}]$$

- The phasor of $v(t)$ is given by:

$$\mathbf{V} = V_M \angle \theta$$

Complex Exponentials

- We represent a real-valued sinusoid as the real part of a complex exponential.
- Complex exponentials provide the link between time functions and phasors.
- Complex exponentials make solving for AC steady state an algebraic problem.

Complex Exponentials

- A complex number $A = z \angle \theta$ can be represented as

$$A = z \angle \theta = z e^{j\theta} = z \cos \theta + j z \sin \theta$$

**DO NOT CONFUSE A SINE FUNCTION
WITH A COMPLEX NUMBER!**

- A What do you get when you multiply A and $e^{j\omega t}$ and find the real part?

Complex Exponentials

$$A e^{j\omega t} = z e^{j\theta} e^{j\omega t} = z e^{j(\omega t + \theta)}$$

$$z e^{j(\omega t + \theta)} = z \cos (\omega t + \theta) + j z \sin (\omega t + \theta)$$

$$\text{Re}[A e^{j\omega t}] = z \cos (\omega t + \theta)$$

Sinusoids, Complex Exponentials, and Phasors

- Sinusoid:

$$z \cos(\omega t + \theta)$$

- Complex exponential:

$$Ae^{j\omega t} = z e^{j(\omega t + \theta)}$$


- Phasor:

$$\mathbf{V} = z \angle \theta$$

Phasor Relationships for Circuit Elements

- Phasors allow us to express current-voltage relationships for inductors and capacitors much like we express the current-voltage relationship for a resistor.
- A complex exponential is the mathematical tool needed to obtain this relationship.

I-V Relationship for a Capacitor

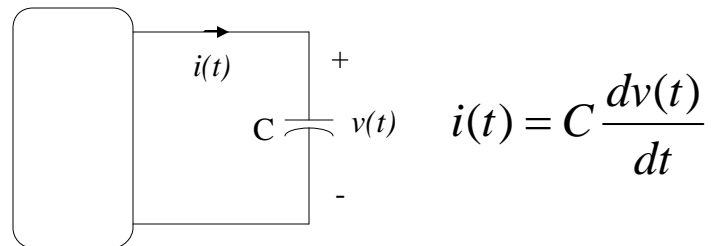

Suppose that $v(t)$ is a sinusoid:

$$v(t) = V_M \cos(\omega t + \theta)$$

Find $i(t)$.

Computing the Current

$$i(t) = C \frac{dv(t)}{dt} = -CV_M \omega \sin(\omega t + \theta)$$

$$i(t) = \text{Re}[j\omega CV_M e^{j\omega t + j\theta}] = \text{Re}[j\omega C v(t)]$$

We can write:

$$i(t) = \text{Re}\left[\frac{1}{Z_C} v(t)\right] \quad \text{where } Z_C = 1/j\omega C$$

Phasor Relationship

- Represent $v(t)$ and $i(t)$ as phasors:

$$\mathbf{V} = V_M \angle \theta$$

$$\mathbf{I} = j\omega C \mathbf{V}$$

- The derivative in the relationship between $v(t)$ and $i(t)$ becomes a multiplication by $j\omega$ in the relationship between \mathbf{V} and \mathbf{I} .


Example

$$v(t) = 120V \cos(377t + 30^\circ)$$

$$C = 2\mu\text{F}$$

- What is \mathbf{V} ?
- What is \mathbf{I} ?
- What is $i(t)$?

I-V Relationship for an Inductor

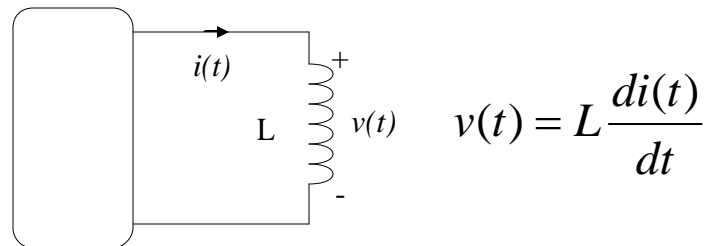

$$\mathbf{V} = j\omega L \mathbf{I}$$

$$\mathbf{Z}_L = j\omega L$$

Example

$$i(t) = 1\mu\text{A} \cos(2\pi 9.15 \cdot 10^7 t + 30^\circ)$$

$$L = 1\mu\text{H}$$

- What is \mathbf{I} ?
- What is \mathbf{V} ?
- What is $v(t)$?

Resistor I-V relationship

$v_R = i_R R$ $\mathbf{V}_R = \mathbf{I}_R R$ where R is the resistance in ohms,
 \mathbf{V}_R = phasor voltage, \mathbf{I}_R = phasor current
(boldface indicates complex quantity)

Capacitor I-V relationship

$i_C = C dv_C/dt$ Phasor current \mathbf{I}_C = phasor voltage \mathbf{V}_C /
capacitive impedance \mathbf{Z}_C : $\rightarrow \mathbf{I}_C = \mathbf{V}_C / \mathbf{Z}_C$
where $\mathbf{Z}_C = 1/j\omega C$, $j = (-1)^{1/2}$ and boldface
indicates complex quantity

Inductor I-V relationship

$v_L = L di_L/dt$ Phasor voltage \mathbf{V}_L = phasor current \mathbf{I}_L /
inductive impedance \mathbf{Z}_L : $\rightarrow \mathbf{V}_L = \mathbf{I}_L \mathbf{Z}_L$
where $\mathbf{Z}_L = j\omega L$, $j = (-1)^{1/2}$ and boldface
indicates complex quantity

Phasor Diagrams

- A phasor diagram is just a graph of several phasors on the complex plane (using real and imaginary axes).
- A phasor diagram helps to visualize the relationships between currents and voltages.

Impedance

- AC steady-state analysis using phasors allows us to express the relationship between current and voltage using a formula that looks like Ohm's law:


$$\mathbf{V} = \mathbf{I} \mathbf{Z}$$

- \mathbf{Z} is called *impedance*.

Some Thoughts on Impedance

- Impedance depends on the frequency ω .
- Impedance is (often) a complex number.
- Impedance allows us to use the same solution techniques for AC steady state as we use for DC steady state.

Example: Single Loop Circuit

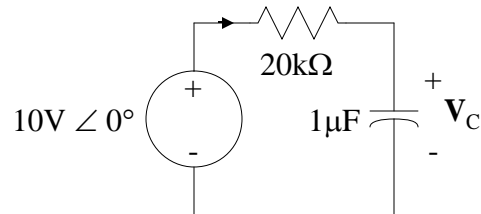

$$\omega = 377$$

Find V_C


How do we find V_C ?

First compute impedances for resistor and capacitor:

$$Z_R = 20k\Omega = 20k\Omega \angle 0^\circ$$

$$Z_C = 1/j(377 \text{ } 1\mu F) = 2.65k\Omega \angle -90^\circ$$

Impedance Example

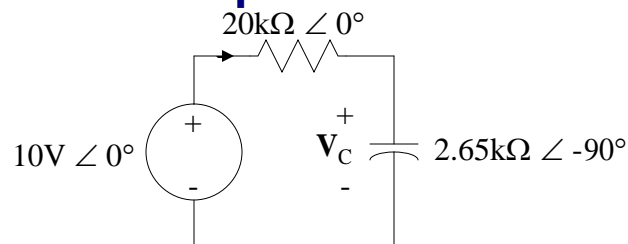


Now use the voltage divider to find V_C :

$$V_C = 10V \angle 0^\circ \left(\frac{2.65k\Omega \angle -90^\circ}{2.65k\Omega \angle -90^\circ + 20k\Omega \angle 0^\circ} \right)$$

$$V_C = 1.31V \angle -82.4^\circ$$


What happens when ω changes?

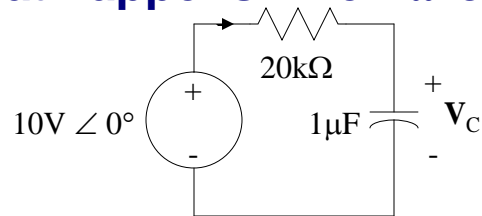


$$\omega = 10$$

Find V_C

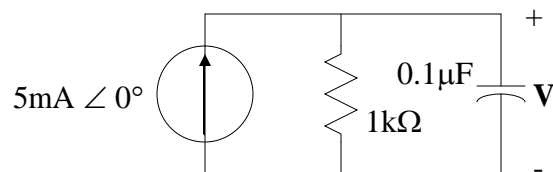
Low Pass Filter: A Single Node-pair Circuit



Find $v(t)$ for $\omega = 2\pi 3000$

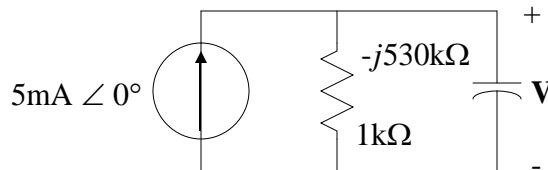

Find the Equivalent Impedance

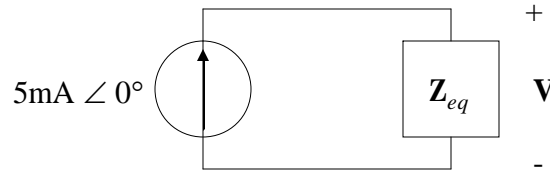

$$\mathbf{Z}_{eq} = \frac{1000(-j530)}{1000 - j530} = \frac{10^3 \angle 0^\circ \times 530 \angle -90^\circ}{1132 \angle -27.9^\circ}$$


$$\mathbf{Z}_{eq} = 468.2\Omega \angle -62.1^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 468.2\Omega \angle -62.1^\circ$$


$$\mathbf{V} = 2.34\text{V} \angle -62.1^\circ$$

$$v(t) = 2.34\text{V} \cos(2\pi 3000t - 62.1^\circ)$$


Change the Frequency

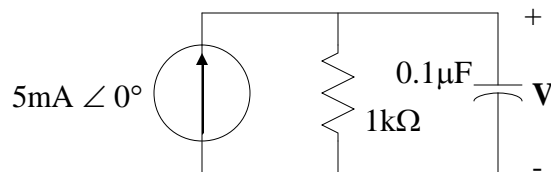

Find $v(t)$ for $\omega = 2\pi 455000$

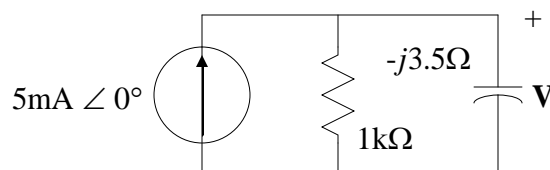

Find an Equivalent Impedance

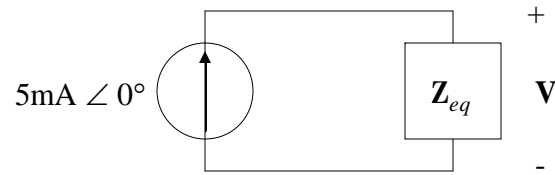

$$\mathbf{Z}_{eq} = \frac{1000(-j3.5)}{1000 - j3.5} = \frac{10^3 \angle 0^\circ \times 3.5 \angle -90^\circ}{1000 \angle -0.2^\circ}$$

$$\mathbf{Z}_{eq} = 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = 17.5\text{mV} \angle -89.8^\circ$$

$$v(t) = 17.5\text{mV} \cos(2\pi 455000t - 89.8^\circ)$$