

Midterm 1 Announcements

■ Midterm 1:

- 12-1:30pm on Tuesday, July 18th in Dwinelle 145.

- Material covered in HW1-3


■ HW3 due on Monday at 6pm

■ Attend only your second lab slot next week

■ Extended office hours

- All day Monday: (10am-12pm and 2-5pm)

Review: Second-Order Filter Circuits

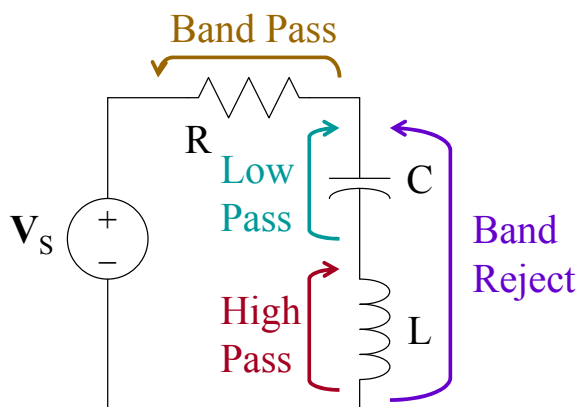

$$\mathbf{Z} = R + 1/j\omega C + j\omega L$$

$$\mathbf{H}_{\text{BP}} = R / \mathbf{Z}$$

$$\mathbf{H}_{\text{LP}} = (1/j\omega C) / \mathbf{Z}$$

$$\mathbf{H}_{\text{HP}} = j\omega L / \mathbf{Z}$$

$$\mathbf{H}_{\text{BR}} = \mathbf{H}_{\text{LP}} + \mathbf{H}_{\text{HP}}$$



Lecture #9

OUTLINE

- The operational amplifier (“op amp”)
- Ideal op amp
- Feedback
- Unity-gain voltage follower circuit
- Summing, difference, integrator, differentiator, active filter

Reading

Ch. 14




The Operational Amplifier

- The ***operational amplifier*** (“***op amp***”) is a basic building block used in analog circuits.
 - Its behavior is modeled using a dependent source.
 - When combined with resistors, capacitors, and inductors, it can perform various useful functions:
 - **amplification/scaling** of an input signal
 - **sign changing** (inversion) of an input signal
 - **addition** of multiple input signals
 - **subtraction** of one input signal from another
 - **integration** (over time) of an input signal
 - **differentiation** (with respect to time) of an input signal
 - **analog filtering**
 - **nonlinear functions** like exponential, log, sqrt, etc


Op Amp Terminals

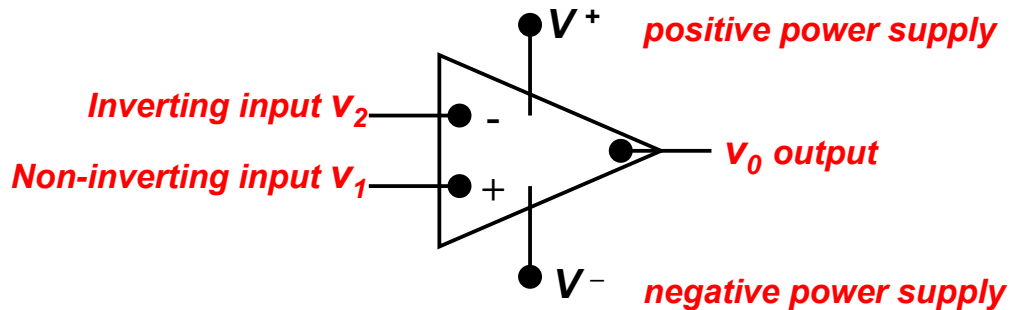- 3 signal terminals: 2 inputs and 1 output
- IC op amps have 2 additional terminals for DC power supplies
- Common-mode signal = $(v_1 + v_2)/2$
- Differential signal = $v_1 - v_2$



Op Amp Terminal Voltages and Currents

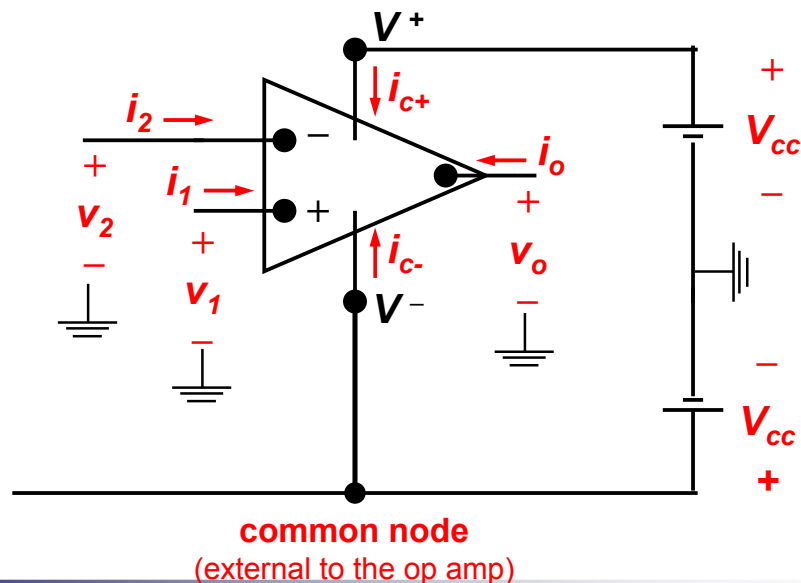- All voltages are referenced to a common node.
- Current reference directions are into the op amp.



Model

- A is differential gain or open loop gain

- Ideal op amp

$$A \rightarrow \infty$$

$$R_i \rightarrow \infty$$

$$R_o = 0$$


- Common mode gain = 0

$$v_{cm} = \frac{(v_1 + v_2)}{2}, v_d = v_1 - v_2$$

$$v_o = A_{cm} v_{cm} + A_d v_d$$

$$\text{Since } v_o = A(v_1 - v_2), A_{cm} = 0$$

- Circuit Model

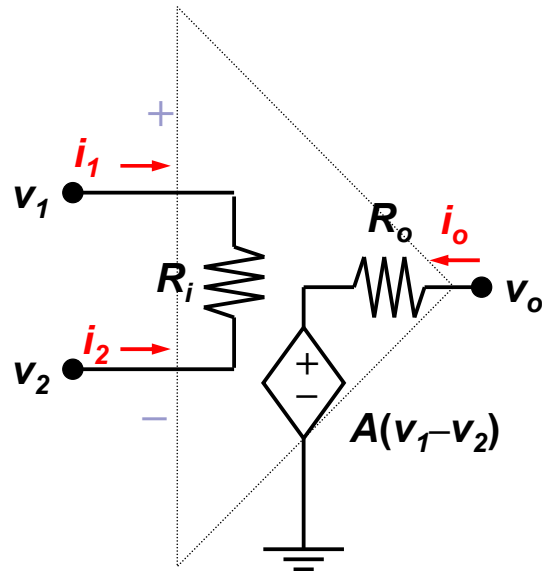


Model and Feedback

- Negative feedback

- connecting the output port to the negative input (port 2)

- Positive feedback

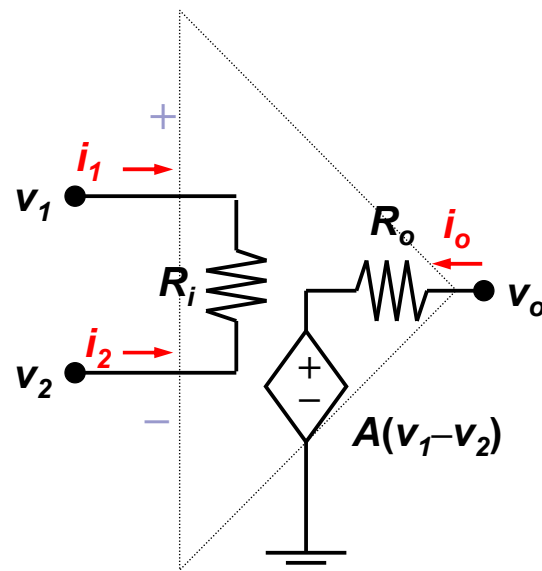- connecting the output port to the positive input (port 1)



Note on negative feedback

$$V_{out} = A\varepsilon$$

$$\varepsilon = V_{in} - FV_{out}$$


$$V_{out} = A(V_{in} - FV_{out})$$

$$V_{out}(1 + AF) = AV_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A}{1 + AF} \cong \frac{1}{F}$$

$$\varepsilon = \frac{V_{out}}{A}$$
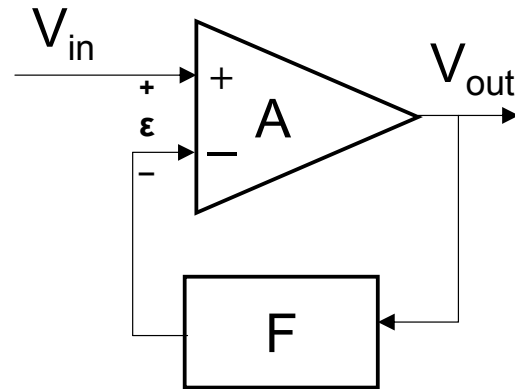
$$\Rightarrow \frac{\varepsilon}{V_{in}} = \frac{1}{1 + AF} \cong 0$$




When A is very large

Summing-Point Constraint

- Check if under negative feedback
 - Small v_i result in large v_o
 - Output v_o is connected to the inverting input to reduce v_i
 - Resulting in $v_i=0$
- Summing-point constraint
 - $v_1 = v_2$
 - $i_1 = i_2 = 0$
- Virtual short circuit
 - Not only voltage drop is 0 (which is short circuit), input current is 0
 - This is different from short circuit, hence called “virtual” short circuit.

Op Amp Voltage Transfer Characteristic

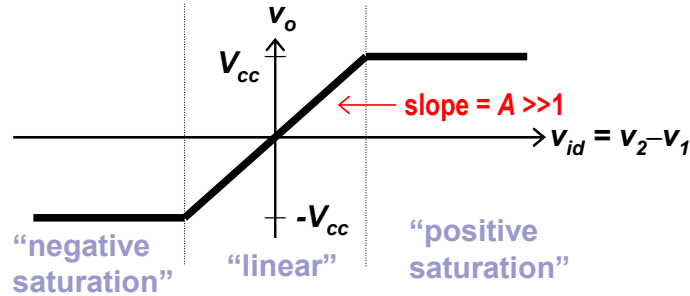The op amp is a differentiating amplifier:




- In the linear region, $v_o = A (v_2 - v_1) = A v_{id}$
 - A is the open-loop gain
- Typically, $V_{cc} \leq 20 \text{ V}$ and $A > 10^4$
 - linear range: $-2 \text{ mV} \leq v_{id} = (v_2 - v_1) \leq 2 \text{ mV}$
- Thus, for an op amp to operate in the linear region,
 - $v_2 \cong v_1$
 - There is a "virtual short" between the input terminals.)


Achieving a "Virtual Short"

- Recall the voltage transfer characteristic of an op amp:

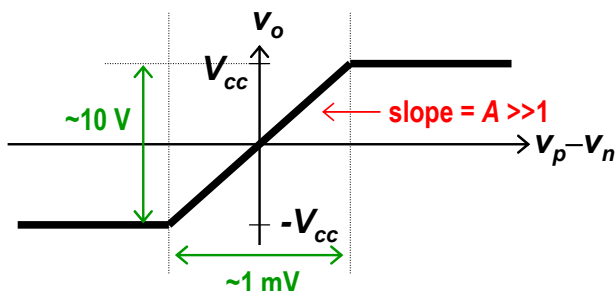Plotted using different scales for v_o and $v_p - v_n$



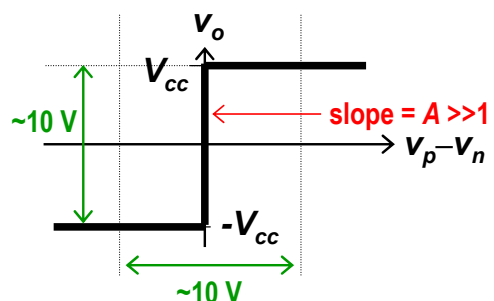Plotted using similar scales for v_o and $v_p - v_n$




Q: How does a circuit maintain a virtual short at the input of an op amp, to ensure operation in the linear region?

A: By using **negative feedback**. A signal is fed back from the output to the inverting input terminal, effecting a **stable** circuit connection. Operation in the **linear region** enforces the virtual short circuit.

Inverting Amplifier

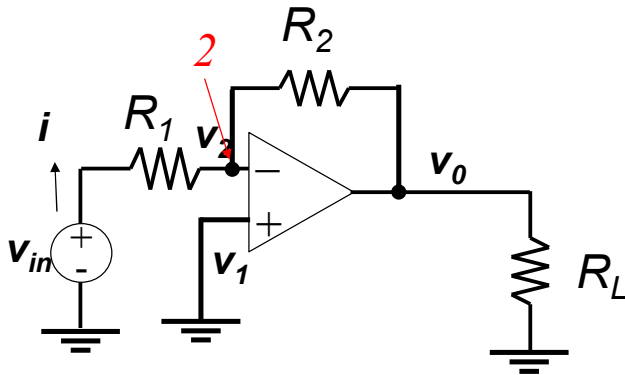- Negative feedback → checked
- Use summing-point constraint



$$\text{Closed loop gain} = A_v = \frac{v_o}{v_{in}}$$

$$v_1 = v_2 = 0, i_1 = i_2 = 0$$

Use KCL At Node 2.

$$i = \frac{(v_{in} - v_2)}{R_1} = \frac{(v_{out} - v_2)}{R_2}$$


$$v_o = -\frac{R_2 v_o}{R_1}$$

$$\text{Input impedance} = \frac{v_{in}}{i} = R_1$$

Ideal voltage source – independent of load resistor

Non-Inverting Amplifier

- Ideal voltage amplifier

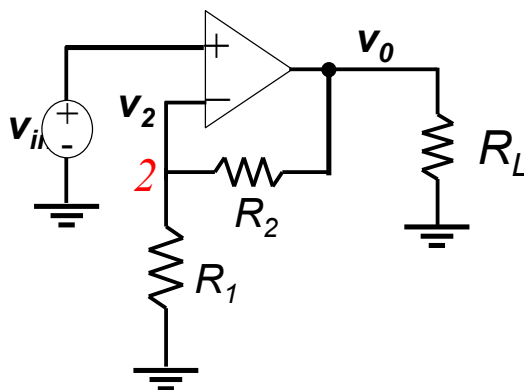

$$\text{Closed loop gain} = A_v = \frac{v_o}{v_{in}}$$

$$v_1 = v_2 = v_{in}, i_1 = i_2 = 0$$


Use KCL At Node 2.

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1}$$

$$\text{Input impedance} = \frac{v_{in}}{i} \rightarrow \infty$$

Voltage Follower

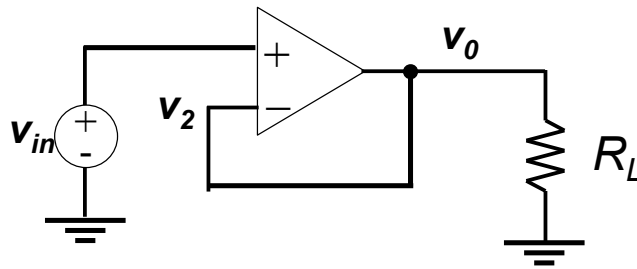


$$R_2 = 0$$

$$R_1 \rightarrow \infty$$

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1} = 1 + \frac{R_2}{R_1} = 1$$

Example 1

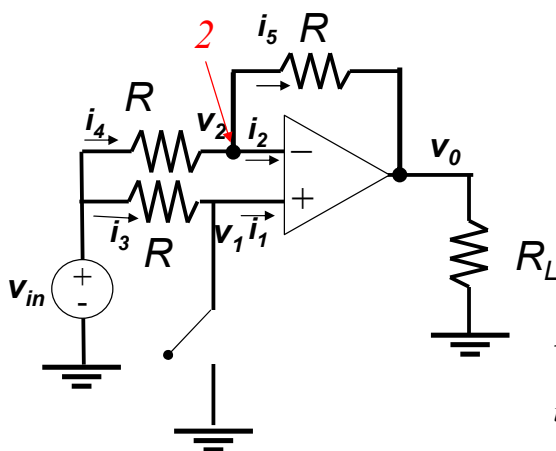

■ Switch is open

$$v_1 = v_2, i_1 = 0 \rightarrow i_3 = 0$$

$$i_3 = \frac{(v_{in} - v_1)}{R} \rightarrow v_1 = v_2 = v_{in} \rightarrow i_4 = 0 \rightarrow i_5 = 0$$

$$i_5 = \frac{(v_o - v_2)}{R} \rightarrow v_o = v_2 = v_{in}$$

$$A = \frac{v_o}{v_{in}} = 1, R_{in} \rightarrow \infty$$

■ Switch is closed

$$v_1 = v_2 = 0, i_1 = 0 \rightarrow i_3 = 0$$

$$i_4 = \frac{(v_{in} - v_2)}{R} = i_5 = -\frac{(v_o - v_2)}{R}$$

$$v_o = -v_{in}$$

$$A = \frac{v_o}{v_{in}} = -1, R_{in} = R/2$$




Example 2

- Design a variable gain amplifier
 - Must have 3 gain settings that can be selected by switches
 - $A = 10, 1, 0.1$
 - The input resistance is $1\text{M}\Omega$



Example 2

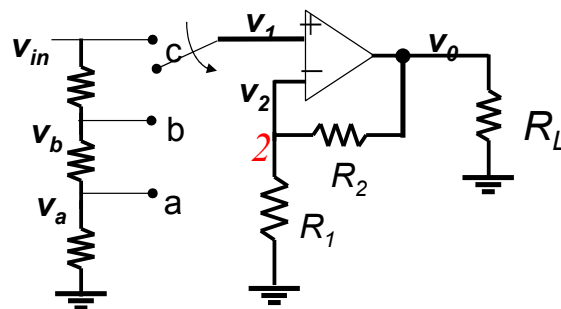

$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_1$$

$$v_1 = v_{in} \text{ Switch at } c$$

$$v_1 = \frac{R_a + R_b}{R_a + R_b + R_c} v_{in} \text{ Switch at } b$$

$$v_1 = \frac{R_a}{R_a + R_b + R_c} v_{in} \text{ Switch at } a$$

Example 2 (cont'd)

$$R_{in} = R_a + R_b + R_c = 1M\Omega$$

$$\text{Max } A_v = 10 = \left(1 + \frac{R_2}{R_1}\right) \text{ Switch at } c$$


$$A_v = 1 = \frac{R_a + R_b}{R_a + R_b + R_c} \left(1 + \frac{R_2}{R_1}\right) \text{ Switch at } b \therefore \frac{R_a + R_b}{R_a + R_b + R_c} = 0.1$$

$$A_v = 0.1 = \frac{R_a}{R_a + R_b + R_c} \left(1 + \frac{R_2}{R_1}\right) \text{ Switch at } a \therefore \frac{R_a}{R_a + R_b + R_c} = 0.01$$

$$\therefore R_a = 10k\Omega, R_b = 90k\Omega, R_c = 900k\Omega$$


$$R_2 = 9R_1$$

Summing Amplifier

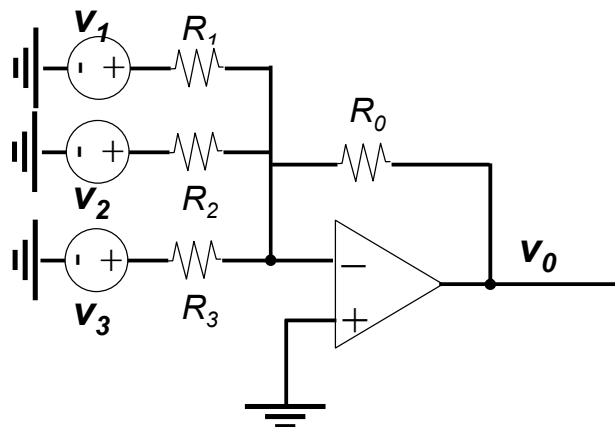





Difference Amplifier

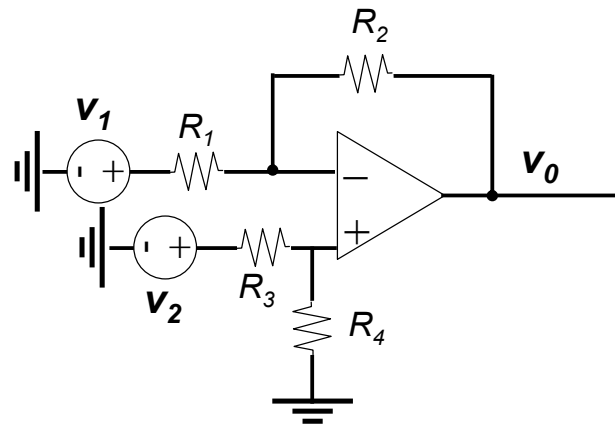


Integrator

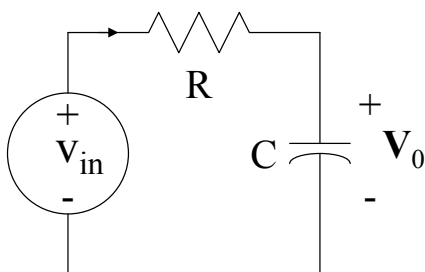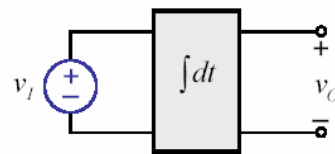- Want $v_o = K \int v_{in} dt$
- What is the difference between:




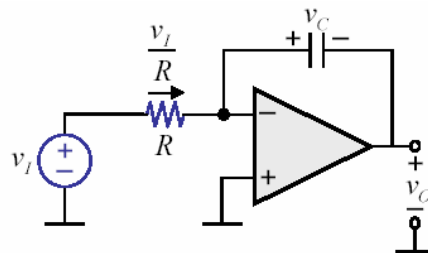
$$v_o \approx \frac{1}{RC} \int_{-\infty}^t v_i dt$$



$$v_o = -\frac{1}{C} \int_{-\infty}^t \frac{v_i}{R} dt$$

Differentiator


■ Want

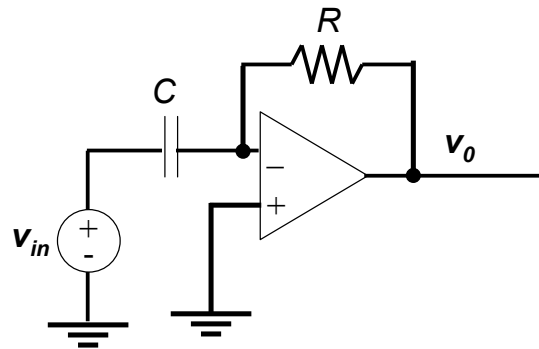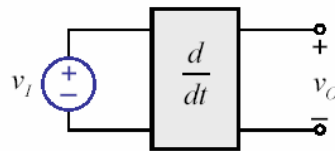

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

“Weighted-adder D/A converter”

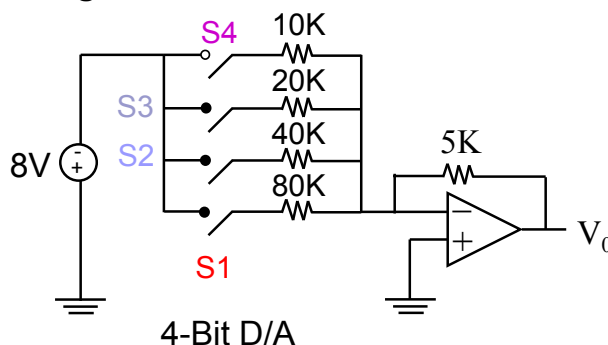


(Transistors are used as electronic switches)

S1 closed if LSB = 1
S2 " if next bit = 1
S3 " if " " = 1
S4 " if MSB = 1

Binary number	Analog output (volts)
0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
1 1 0 1	6.5
1 1 1 0	7
1 1 1 1	7.5
↑ ↑	
MSB LSB	




Characteristic of 4-Bit DAC

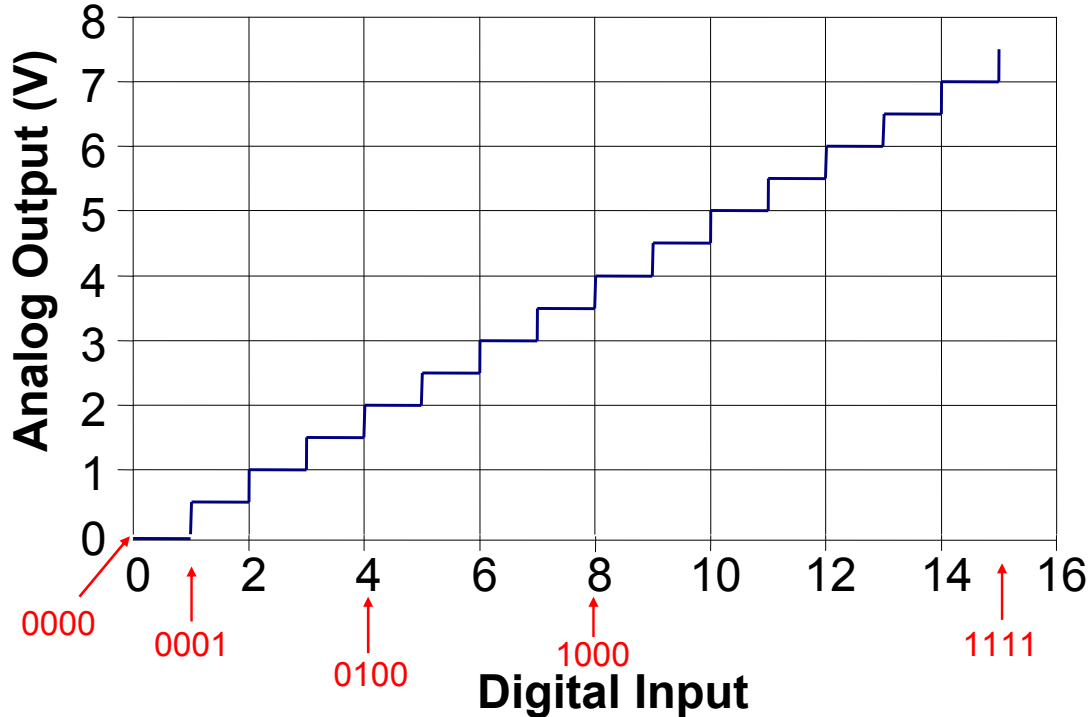

Active Filter

- Contain few components
- Transfer function that is insensitive to component tolerance
- Easily adjusted
- Require a small spread of components values
- Allow a wide range of useful transfer functions

Active Filter Example

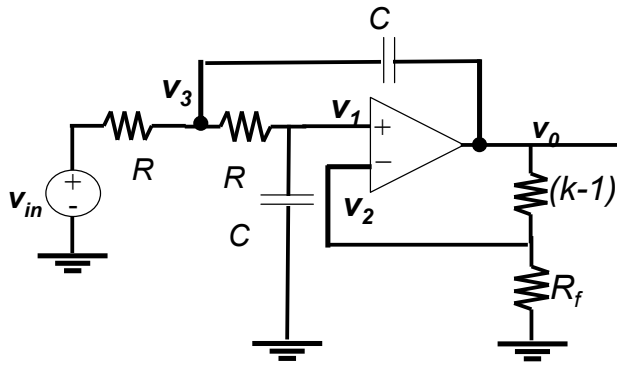

$$v_1 = v_2 = \frac{v_o}{k}$$

$$\text{Use KCL At Node A} \Rightarrow \frac{(v_3 - v_1)}{R} = j\omega C v_1$$

$$\text{Use KCL At Node B} \Rightarrow \frac{(v_{in} - v_3)}{R} = j\omega C(v_3 - v_o) + \frac{(v_3 - v_1)}{R}$$

$$\frac{v_o}{v_{in}} = \frac{k}{1 - \omega^2 R^2 C^2 + j\omega RC(3-k)}$$

$$\text{Let } \omega_B = 1/RC$$

$$|H(\omega)| = \left| \frac{v_o}{v_{in}} \right| = \frac{k}{\sqrt{\left(1 - \frac{\omega^2}{\omega_B^2}\right)^2 + \frac{\omega^2}{\omega_B^2}(3-k)^2}}$$


$$\omega = 0, |H(\omega)| = k \text{ DC gain}$$

$$\omega = \omega_B, |H(\omega)| = \frac{k}{3-k}$$

$$\omega \gg \omega_B, |H(\omega)| = \frac{k}{\left(\frac{\omega^2}{\omega_B^2}\right)} \propto \omega^{-2}$$

$20 \log |H(\omega)|$ decays at a rate of 40dB/decade

Cascaded Active Filter Example

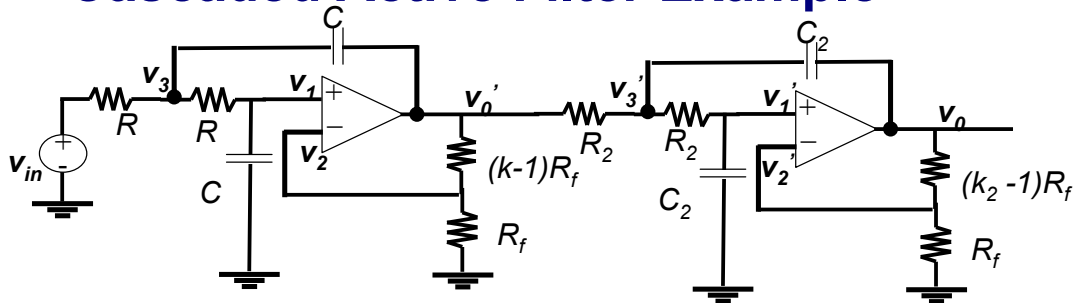

$$\frac{v_o}{v_{in}} = \frac{k_2}{1 - \omega^2 R_2^2 C_2^2 + j\omega R_2 C_2(3-k_2)} \cdot \frac{k}{1 - \omega^2 R^2 C^2 + j\omega RC(3-k)}$$

$$\text{Let } \omega_B = 1/RC, \omega_{B2} = 1/R_2 C_2$$

$$|H(\omega)| = \left| \frac{v_o}{v_{in}} \right| = \frac{k_2}{\sqrt{\left(1 - \frac{\omega^2}{\omega_{B2}^2}\right)^2 + \frac{\omega^2}{\omega_{B2}^2}(3-k_2)^2}} \cdot \frac{k}{\sqrt{\left(1 - \frac{\omega^2}{\omega_B^2}\right)^2 + \frac{\omega^2}{\omega_B^2}(3-k)^2}}$$

$$\omega = 0, |H(\omega)| = k_2 k \text{ DC gain}$$

$$\omega = \omega_B, |H(\omega)| = \frac{k_2 k}{3-k_2-k}$$

$$\omega \gg \omega_B, |H(\omega)| = \frac{k_2 k}{\left(\frac{\omega^4}{\omega_{B2}^2 \omega_B^2}\right)} \propto \omega^{-4}$$

$20 \log |H(\omega)|$ decays at a rate of 80dB/decade